

CMPE 314 Midterm Exam 2


(April 5, 2012)

Problem 1 (15 points)

Describe the structure and operation of a pnp bipolar transistor. What are the biasing conditions (show relevant voltage connections in the structure figure) for cut-off, forward-active mode, and saturation mode?

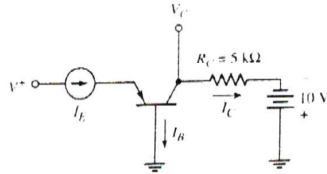
Problem 2 (25 points)

For the transistor circuit shown has properties $\beta=80$, $V_{EB(on)}=0.7$ V and $V_{EC(sat)}=0.2$ V. The bias current source has $I_E=2.2$ mA and $V^+=5$ V. Determine V_C and the power dissipated in the transistor. Is the transistor biased in the forward-active mode. Why or why not?



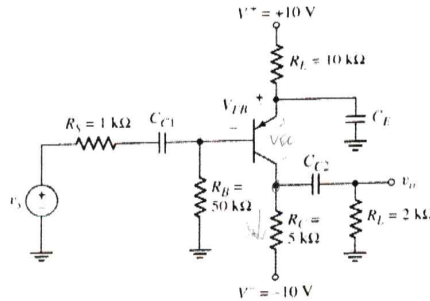
Problem 3 (35 points)

- Derive the equations to determine I_{CQ} and V_{CEQ} . Find the DC load-line slope. What are the roles of R_E and C_E ?
- Assume finite V_A . Draw the small-signal circuit with the hybrid- π model for the transistor. How to determine the hybrid- π model parameters? Find the AC load-line slope and the maximum symmetric output voltage swing. (Work with equations for Problem 3)



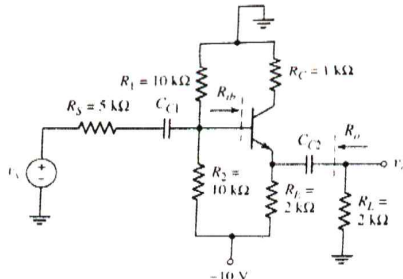Problem 4 (25 points)


- Assume $V_A = \infty$. Draw the small-signal circuit, including the hybrid- π model.
- Find the equivalent input resistance R_{ib} and the small-signal voltage gain. Comment on the type of amplifier configuration and its main features. (Work with equations for Problem 4)



CMPE 314 Midterm Exam II
Solutions

Spring 2012

P1

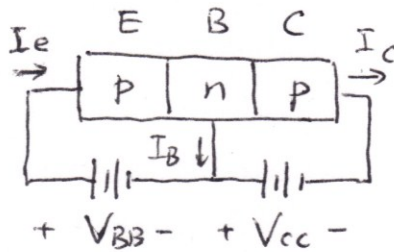

In forward-active mode

$V_{BB} > V_{EB(on)}$ forward biased

$V_{CB} < 0$ reverse biased


Holes injected from emitter into base and diffused to BC-junction, swept by the BC-junction space-charge field into collector

$V_{EB} < V_{EB(on)} \approx 0.7V$, BJT is in cut-off

$V_{EC} < V_{EC(sat)} \approx 0.2V$, BJT is in saturation.

$$\begin{array}{ccccc} I_E & = & I_C & + & I_B \\ \downarrow & & \downarrow & & \downarrow \\ \text{from holes} & & \text{holes} & & \text{electrons} \end{array}$$

P2

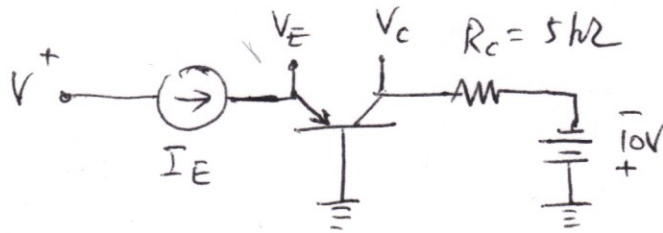

$$I_E = 2.2 \text{ mA}$$

$$R_C = 5 \text{ k}\Omega$$

If BJT is in the forward-active mode

$$I_C = \frac{\beta}{1+\beta} = \frac{80}{81} \times 2.2 \text{ mA} = 2.173 \text{ mA}$$

$$V_{R_C} = R_C I_C = 5 \text{ k}\Omega \times 2.173 \text{ mA} = 10.865 \text{ V}$$

$$V_E = -10 + R_C I_C = 0.865 \text{ V}$$

$$V_E = 0.7 \text{ V}$$

$$V_{EC} = V_E - V_C = 0.7 - 0.865 = -0.165 \text{ V} < V_{EC}(\text{sat})$$

BJT is in saturation.

$$V_C = V_{EC} - V_{EC}(\text{sat}) = 0.7 - 0.2 = 0.5 \text{ V}$$

$$I_C = \frac{V_C - (-10 \text{ V})}{5 \text{ k}\Omega} = 2.1 \text{ mA}$$

$$I_B = I_E - I_C = 2.2 - 2.1 = 0.1 \text{ mA}$$

$$P_d = V_{EB} I_B + V_{EC} I_C = 0.07 + 0.42 = 0.49 \text{ mW}$$

P3


$$(a) \begin{cases} V^+ = I_E R_E + V_{EB(on)} + I_B R_B \\ V^+ - V^- = I_E R_E + V_{EC} + I_C R_C \\ I_C = \beta I_B, I_E = (1 + \beta) I_B = \frac{1 + \beta}{\beta} I_C \end{cases}$$

$$\text{DC loadline slope} = - \frac{1}{R_C + \frac{1 + \beta}{\beta} R_E}$$

R_E is used to stabilize the Q-pt.

C_E is used to short R_E to increase the AC loadline slope

(b)

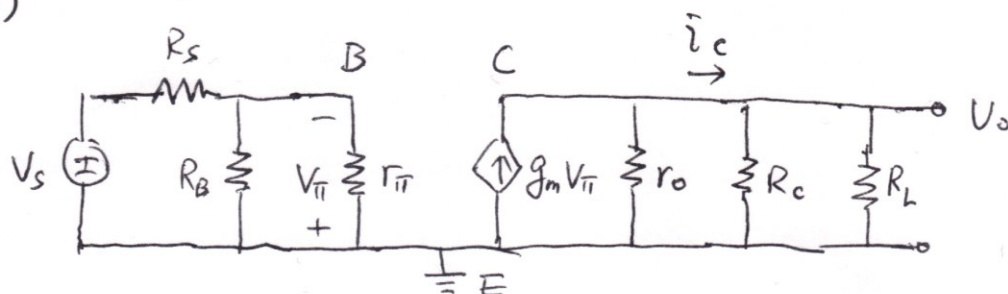

$$g_m = \frac{I_{CQ}}{V_T} \quad r_{\pi} = \frac{V_T}{I_{BQ}} \quad r_o = \frac{V_A}{I_{CQ}} \quad V_T = \frac{k_B T}{e}$$

$$V_o = -V_{ec} = i_c (R_C \parallel R_L)$$


$$\text{AC loadline slope} = - \frac{1}{R_C \parallel R_L}$$

Maximum symmetric swing of i_c : $|\Delta i_c| = 2 I_{CQ}$

Maximum symmetric swing of V_o : $|\Delta V_o| = |\Delta i_c| (R_C \parallel R_L)$

P4

(a)

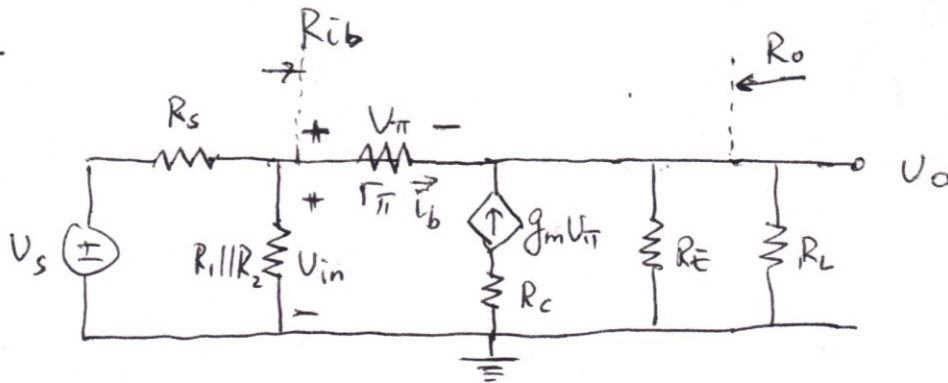

(b)

$$V_{in} = V_{\pi} + V_o$$

$$= i_b r_{\pi} + (1 + \beta) i_b R_E \parallel R_L$$

$$V_{\pi} = \beta i_b$$

$$g_m V_{\pi} = \beta i_b$$

$$R_{ib} \equiv \frac{V_{in}}{i_b} = r_{\pi} + (1 + \beta) R_E \parallel R_L$$

$$V_o = (1 + \beta) i_b (R_E \parallel R_L) = \frac{(1 + \beta) (R_E \parallel R_L)}{R_{ib}} V_{in}$$

$$V_{in} = V_s \frac{R_1 \parallel R_2 \parallel R_{ib}}{R_s + R_1 \parallel R_2 \parallel R_{ib}}$$

$$A_v = \frac{V_o}{V_s} = \frac{(1 + \beta) (R_E \parallel R_L)}{R_{ib}} \cdot \frac{R_1 \parallel R_2 \parallel R_{ib}}{R_s + R_1 \parallel R_2 \parallel R_{ib}}$$

It is an emitter-follower circuit.

$$A_v \approx +1$$

$$A_i > 1$$

R_o is small