

CMPE 212

Principles of Digital Design

Lecture 10

Reduction of Combinational Logic

February 24, 2016

www.csee.umbc.edu/~younis/CMPE212/CMPE212.htm



Lecture's Overview

Previous Lecture:

- ➔ Logic Synthesis
(Definition, Procedure)
- ➔ Gate Type Conversion
(Role of DeMorgan Theorem, Bubble matching)
- ➔ Popular Cell Library
(AND-OR, AND-OR-INVERT, OR-AND, OR_AND_INVERT)
- ➔ Technology Mapping
(Splitting forest to trees, Fan-in constraints, Factoring)

This Lecture

- ➔ Simplification of Switching Functions using K-map



Design Optimization

- ❑ Quality of combinational circuit design is measured using following metrics:
 - Gate counts: fewer gates require smaller area and cost less
 - Propagation delay: time for the output to become available after applying input. This time depends on transistor-level gate implementation
 - Gate fan-in: large gate fan-in can lead to increased gate counts and propagation delay (by using multi-level of gates)
 - Gate fan-out: large gate fan-out may mandate logic replication
- ❑ In many cases the canonical sum-of-products or product-of-sums forms are not minimal in terms of their number and size
- ❑ Since a smaller Boolean equation translates to a lower gate input count in the target circuit, reduction of the equation is an important consideration when circuit complexity is an issue
- ❑ Three methods for reducing Boolean equations are considered:
 - Algebraic reduction
 - Karnaugh map (K-map) reduction
 - Tabular reduction (Quine-McCluskey)

Karnaugh Maps

- ❑ Karnaugh maps (K-map) is a graphical technique to visualize minterms along with variables that are common to them
- ❑ Variables common to multiple minterms are candidates for elimination
- ❑ The basis of K-maps is the Venn diagram representation for visualizing concepts in set theory
- ❑ Each distinct region in the “Universe” represents a minterm
- ❑ Example: Majority Function

$$F = BC + AC + AB$$

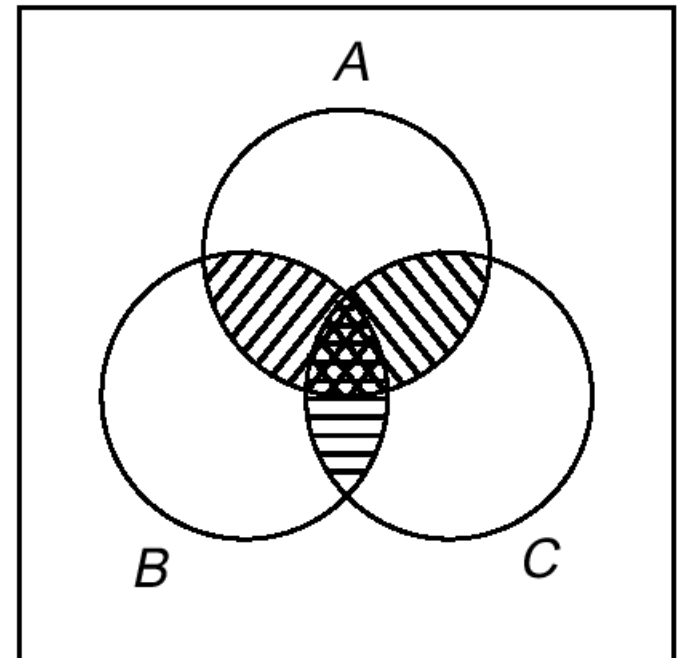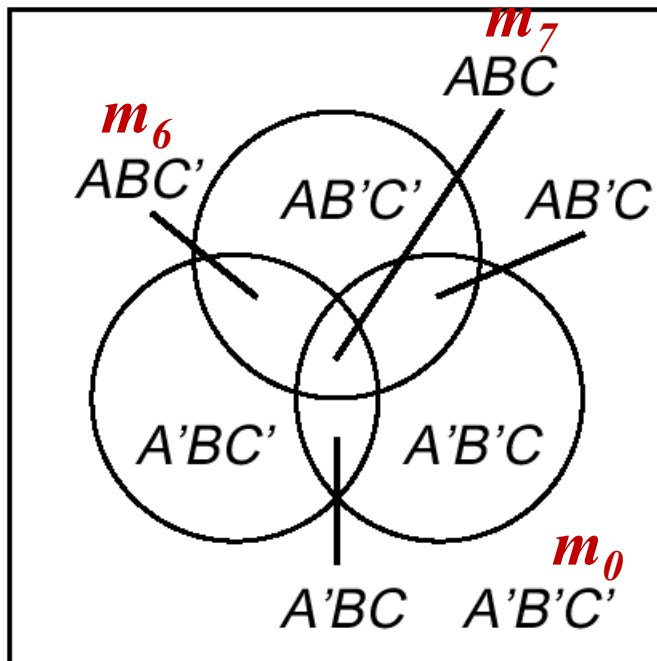


Forming K-Map


Minterm Index	A	B	C	F
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

Minterm adjacency matches the K-map


$$F = BC + AB + AC$$

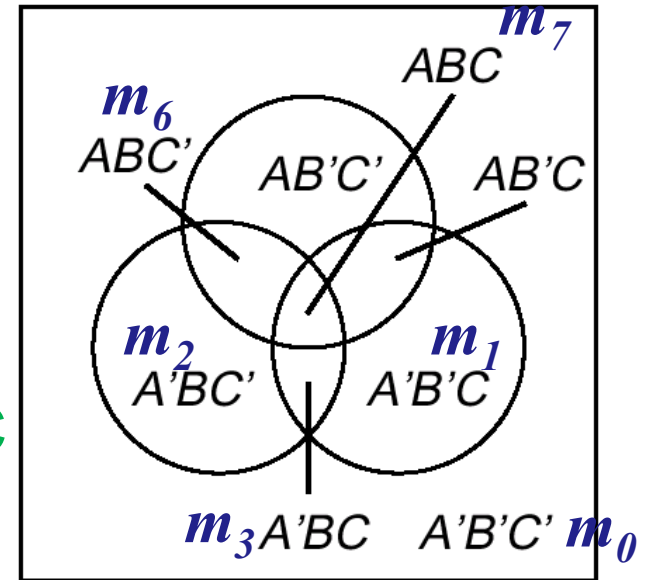

$\begin{matrix} AB \\ C \end{matrix}$	00	01	11	10
0			1	
1		1	1	1

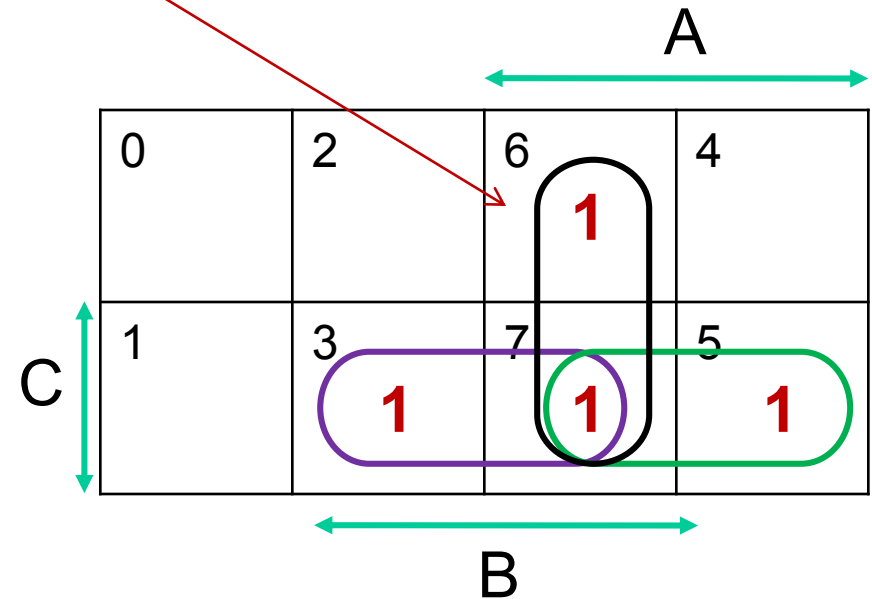

Understanding Minimization

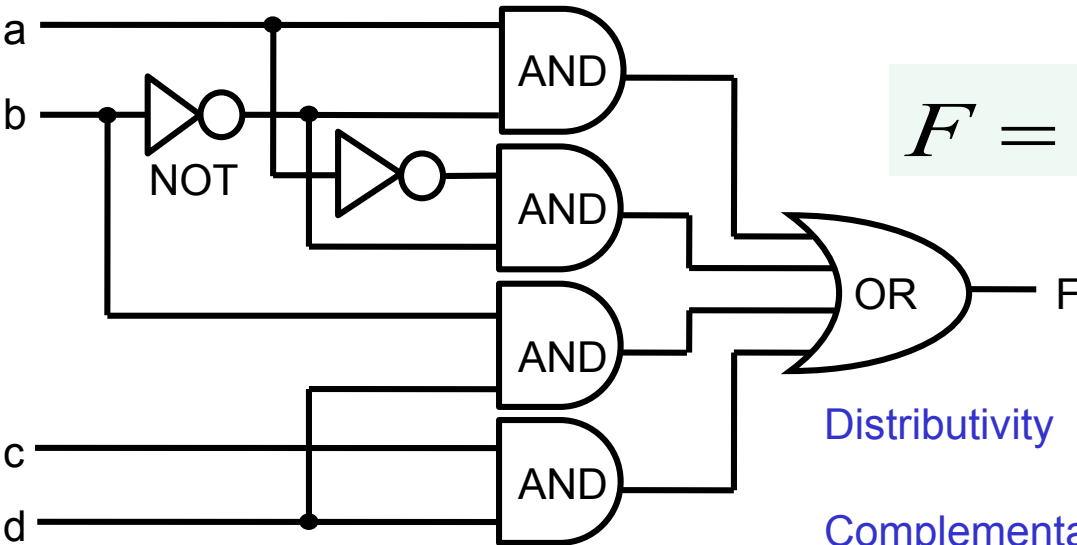

$$F = a\bar{b} + \bar{a}\bar{b} + bd + cd$$

Distributivity

$$F = a\bar{b} + \bar{a}\bar{b} + bd + cd$$

Complementation

$$= \bar{b}(a + \bar{a}) + bd + cd$$

Identity

$$= \bar{b}1 + bd + cd$$

Complementation

$$= \bar{b}(c + \bar{c}) + bd + cd$$

Distributivity

$$= bd + \bar{b}c + cd + \bar{b}\bar{c}$$

Consensus theorem

$$= bd + \bar{b}c + \bar{b}\bar{c}$$


Distributivity

$$= bd + \bar{b}(c + \bar{c})$$


Complement, identity

$$= bd + \bar{b}$$


$$F = bd + \bar{b}$$

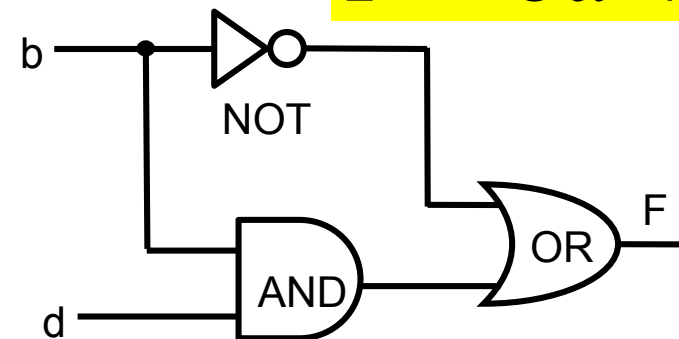


Understanding Minimization

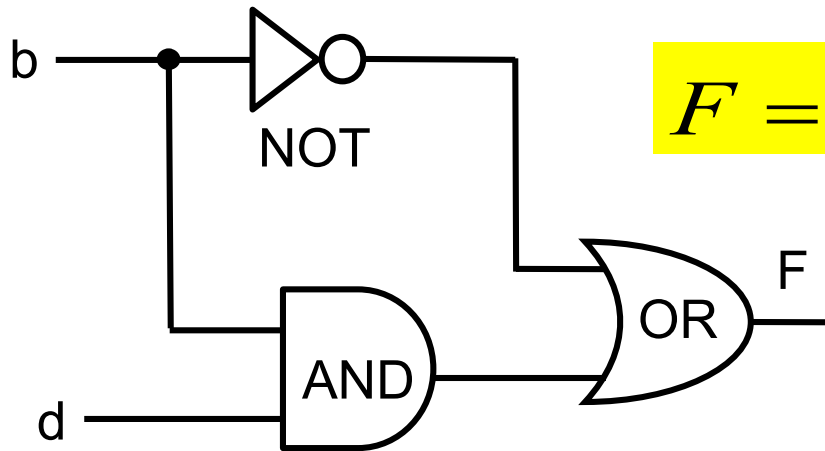


$$F = bd + \bar{b}$$

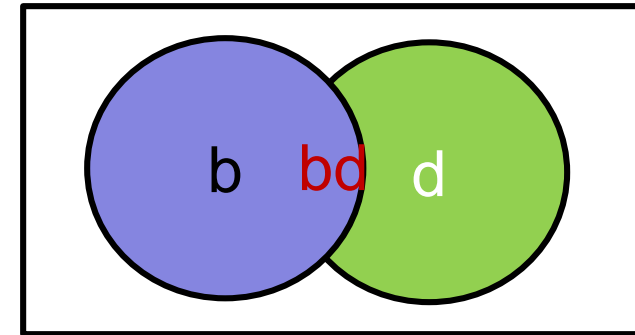

Absorption theorem

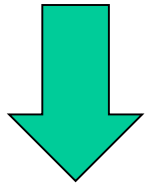
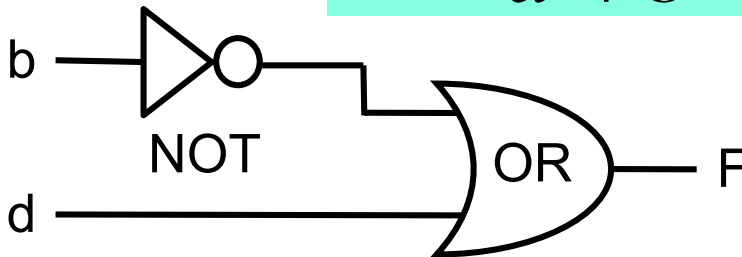
$$\begin{aligned} F &= bd + \bar{b} \\ &= d + \bar{b} \end{aligned}$$



Logic minimization means:


- Minimize gates, i.e., # products in SOP or # sums in POS
- Minimize literals (reduce gate inputs)

Product, Implicant or Cube


- Any set of literals ANDed together
- Minterm is a special case where all variables are present (largest product) and often called 0-implicant or 0-cube

Cubes (Implicants) of 4 Variables

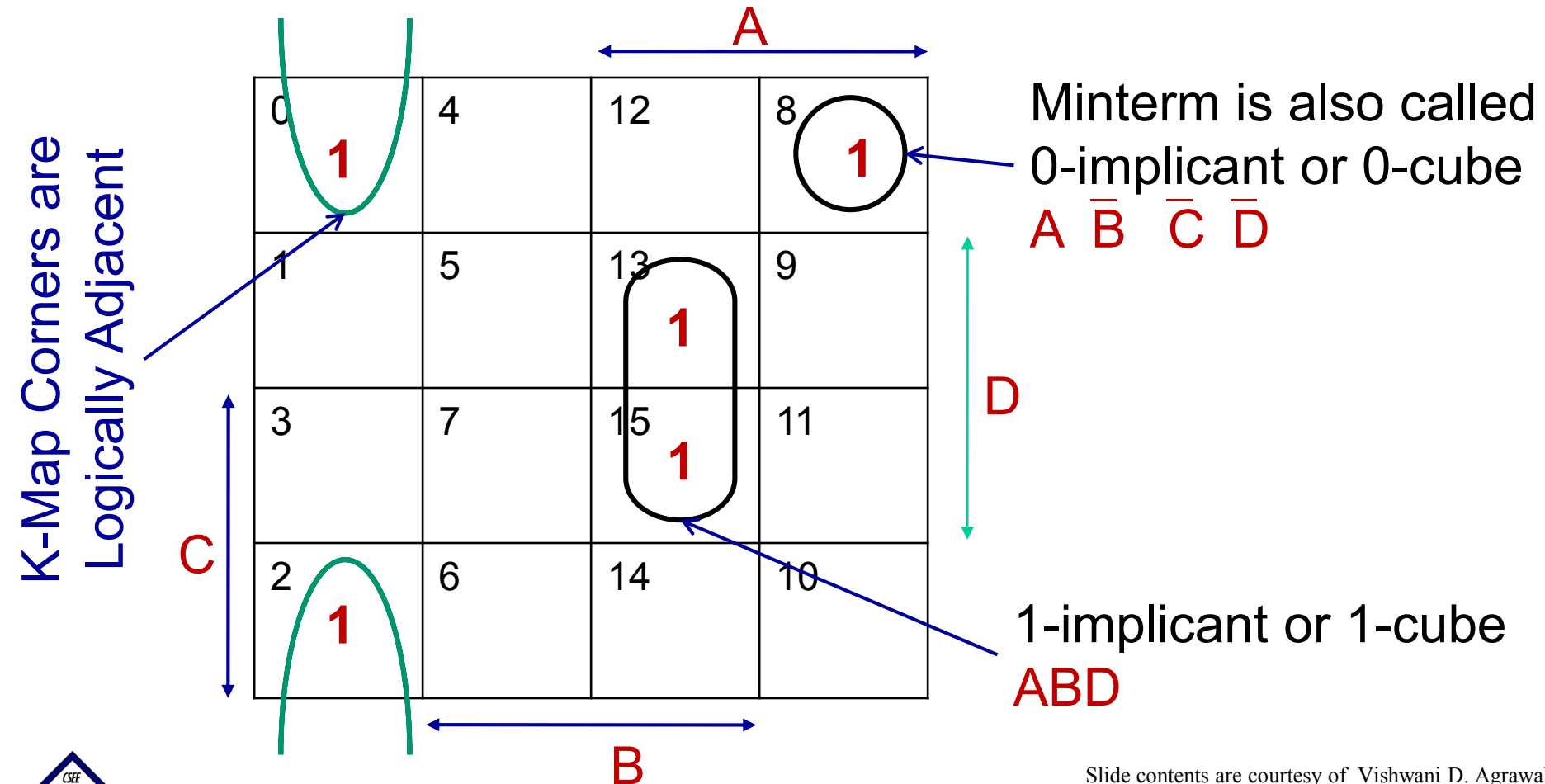- A 1-implicant (1-cube) is a product with one variable eliminated:
 - Obtained by combining two adjacent 0-cubes
 - $ABCD + ABC \bar{D} = ABC(D + \bar{D}) = ABC$




Growing Cubes, Reducing Products

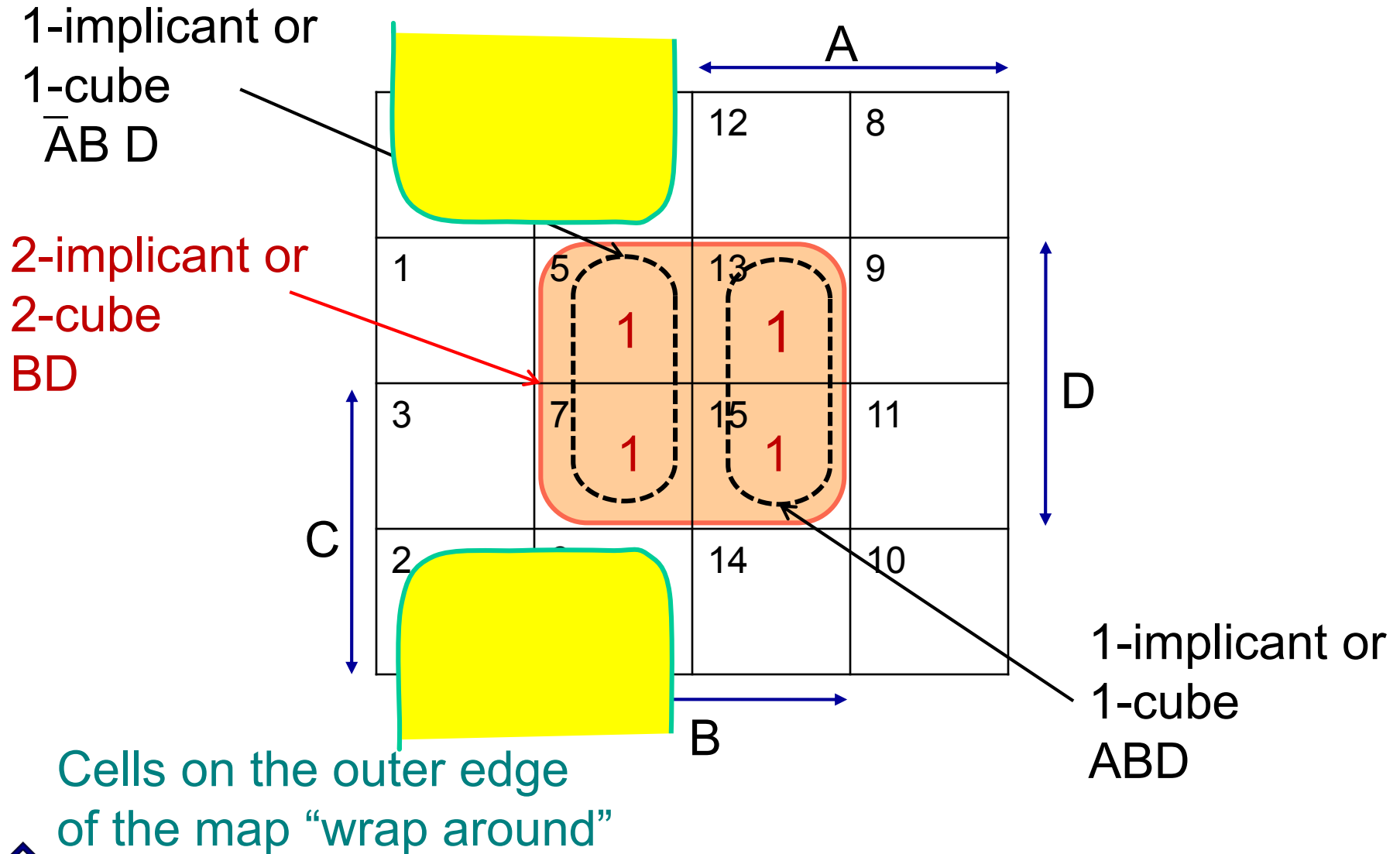

Largest Cubes or Smallest Products

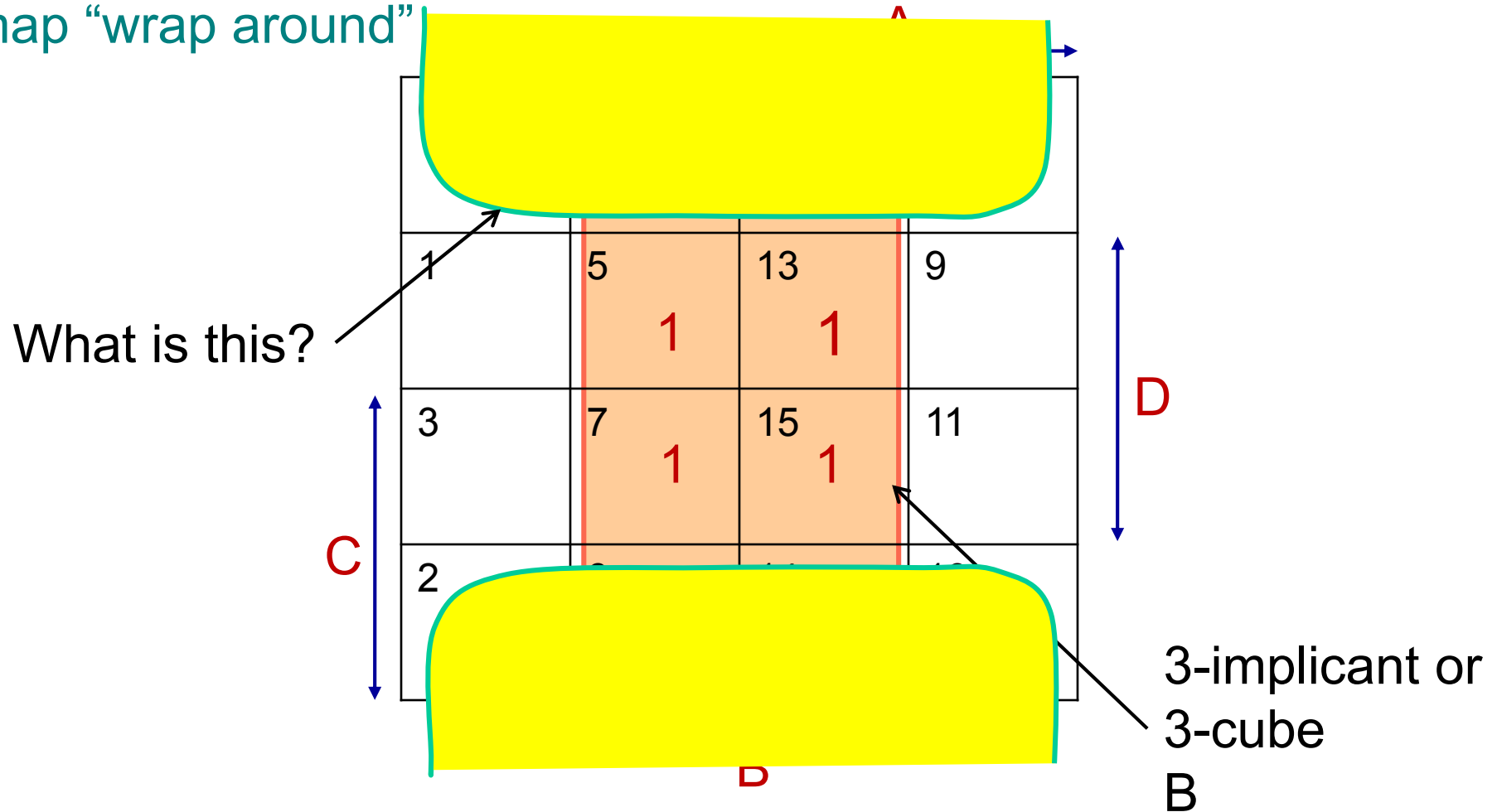Cells on the outer edge of the map “wrap around”




Implicants of a Function

- Minterms, products, cubes that imply the function

Implication and Covering


- A larger cube covers a smaller cube if all minterms of the smaller cube are included in the larger cube.
- A smaller cube implies (or subsumes) a larger cube if all minterms of the smaller cube are included in the larger cube.
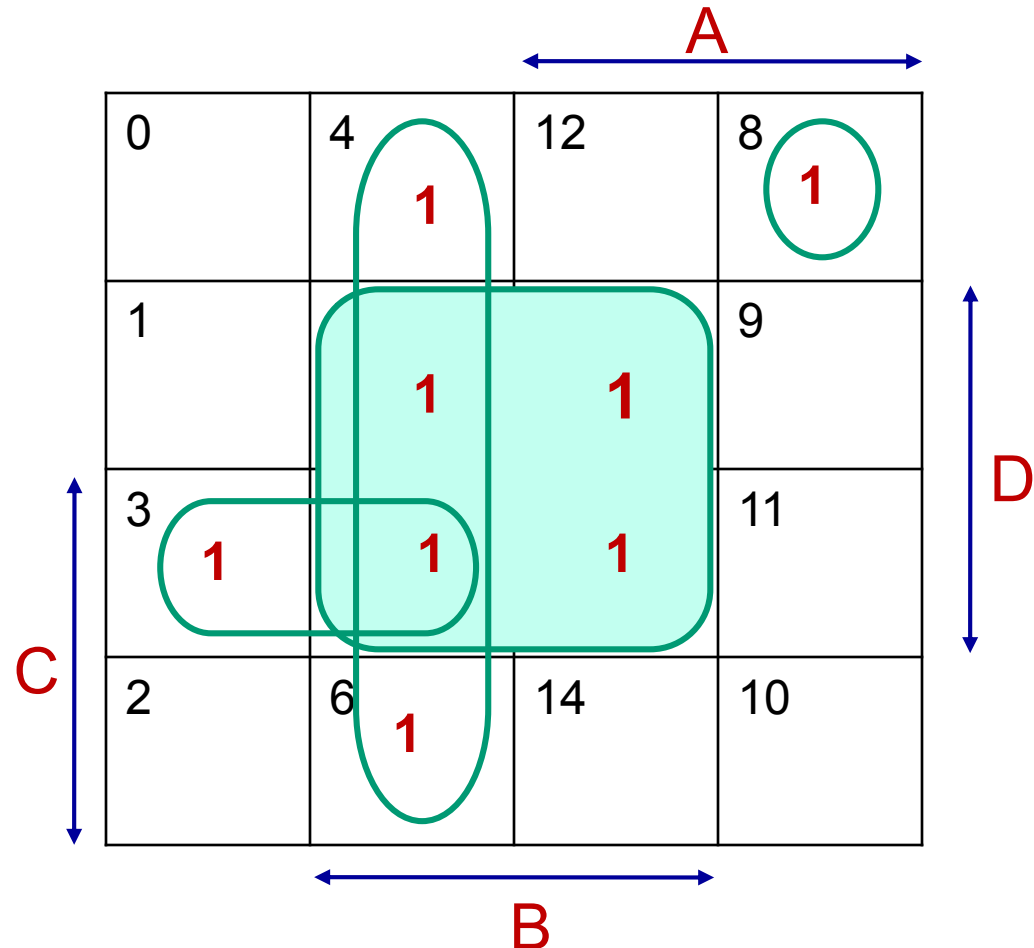
$$F = \overline{A}B + BD + \overline{A}CD + \overline{A}\overline{B}\overline{C}\overline{D}$$





Prime Implicant (PI)

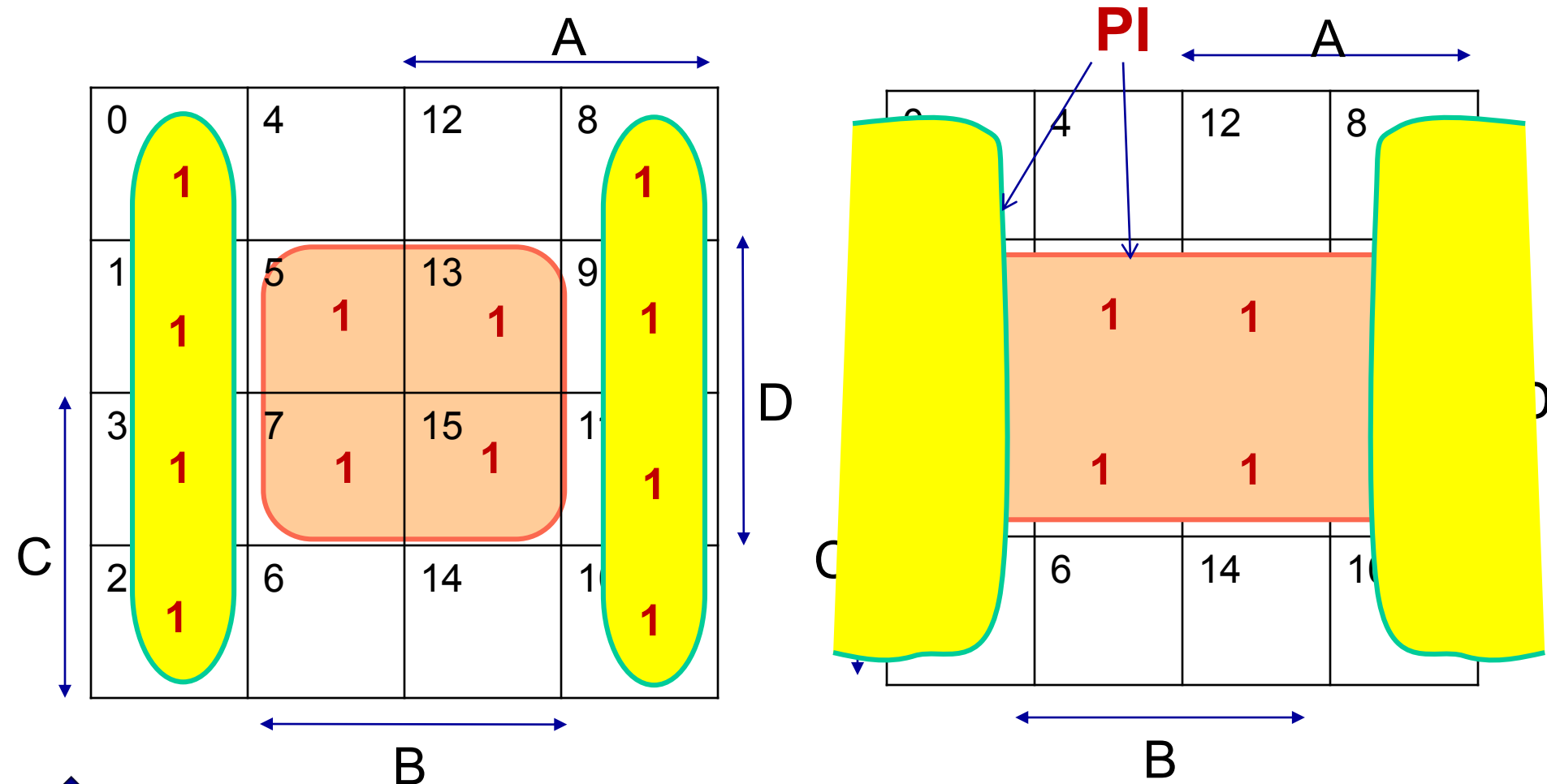- A cube or implicant of a function that cannot grow larger by expanding into other cubes




Type of Prime Implicants

- ❑ If among the minterms subsuming a prime implicant (PI), there is at least one minterm that is covered by this and only this PI, then the PI is called an essential prime implicant (EPI)
- ❑ If each minterm subsuming a prime implicant (PI) is also covered by other essential prime implicants, then that PI is called a redundant prime implicant (RPI)
- ❑ A prime implicant (PI) that is neither EPI nor RPI is called a selective prime implicant (SPI); SPIs occur in pairs.

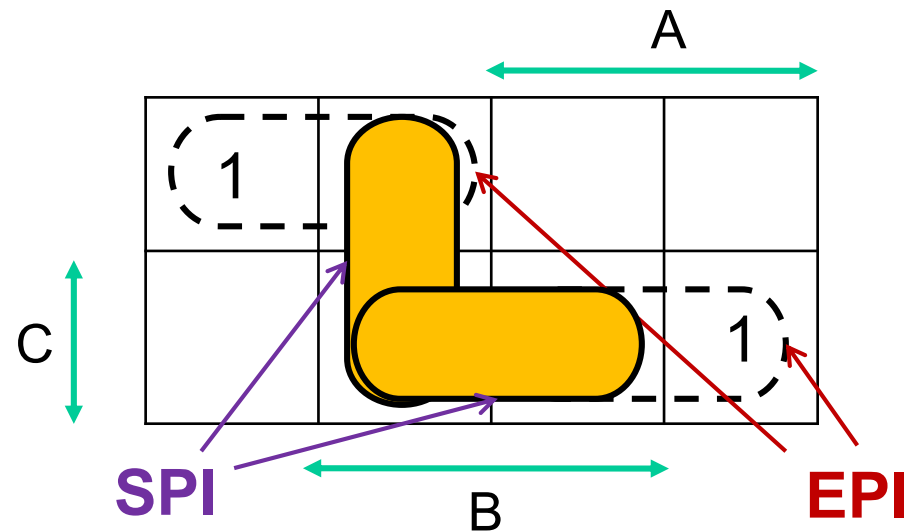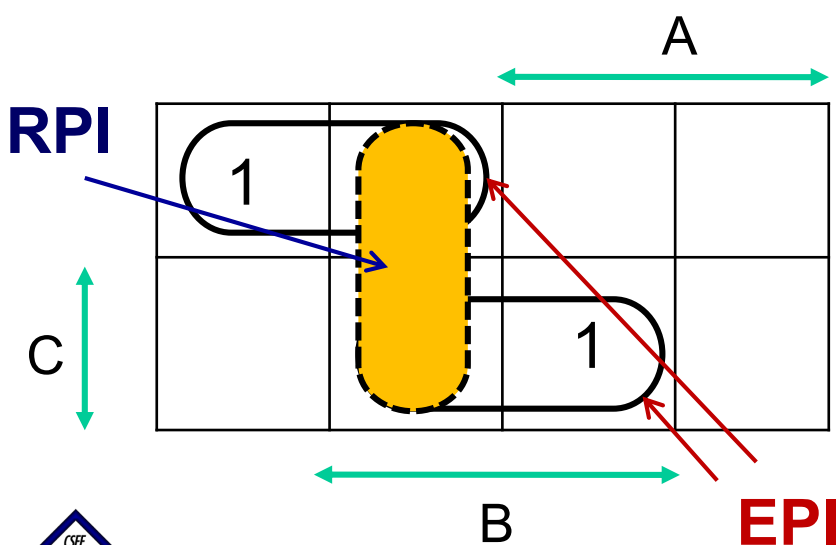

Minimum Sum of Products (MSOP)

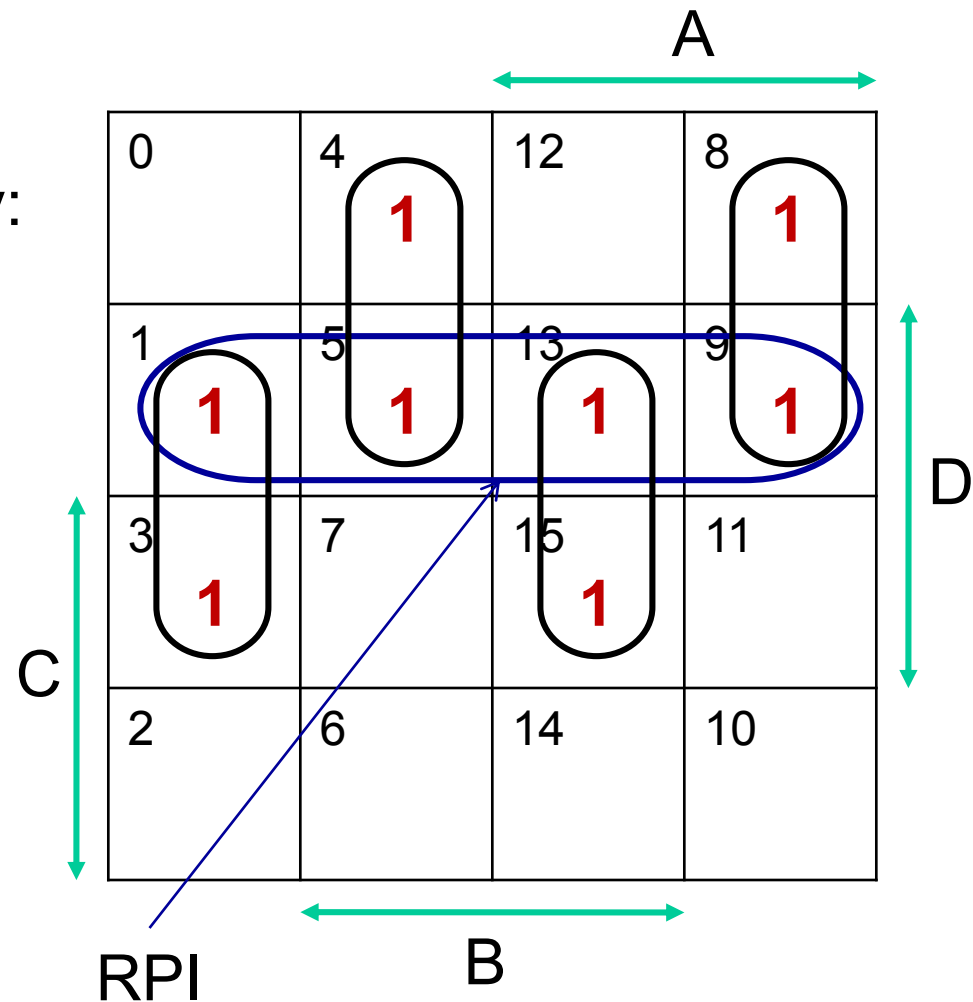- ❑ Identify all prime implicants (by letting implicants grow)
- ❑ Construct MSOP with PIs only:
 - Cover all minterms
 - Use only essential prime implicants (EPI)
 - Use no redundant prime implicant (RPI)
 - Use cheapest selective prime implicants (SPI), e.g. choose EPI in ascending order, starting from 0-implicant, then 1-implicant, 2-implicant, . . .



Example: $F = \sum m(1, 3, 4, 5, 8, 9, 13, 15)$


$$F = \bar{A} \bar{B} D + \bar{A} B \bar{C} + A B D + A \bar{B} \bar{C}$$

Example

$$F = \sum m(1, 3, 5, 7, 8, 10, 12, 13, 14)$$

MSOP:

$$F = \bar{A}D + A\bar{D} + AB\bar{C}$$

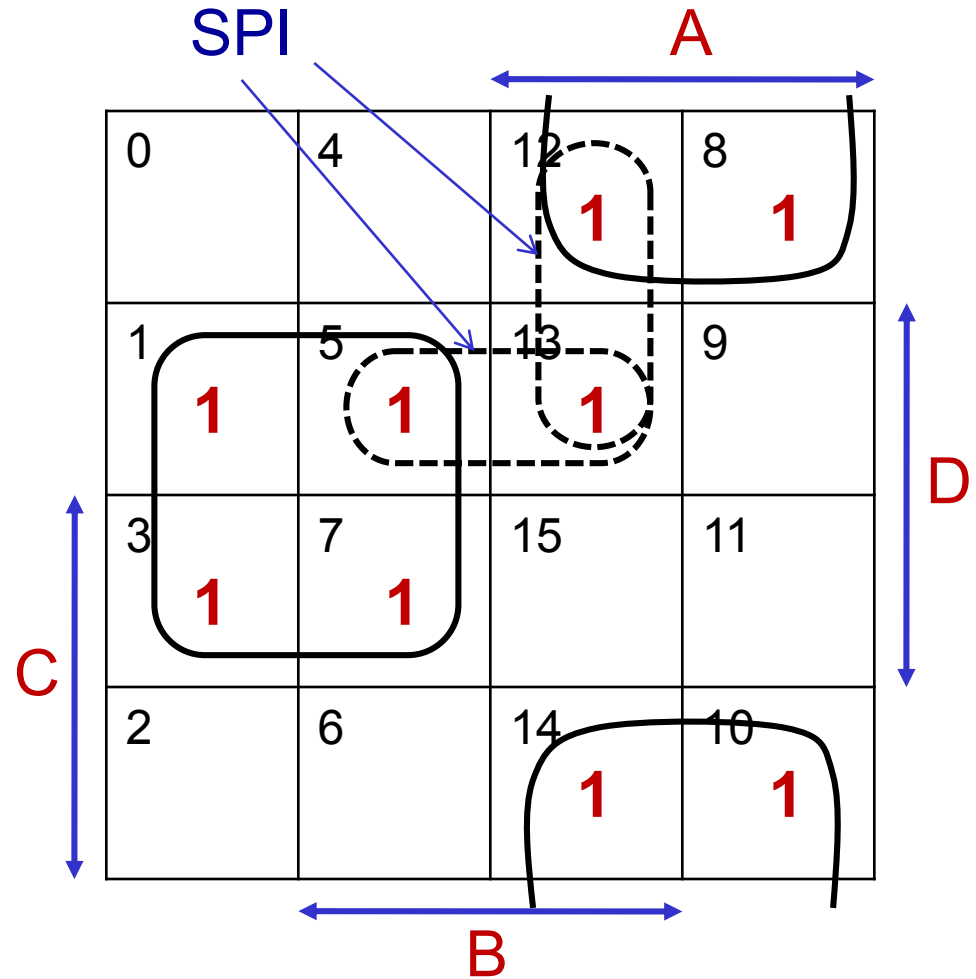

Growing Implicants to PI

- $$\begin{aligned}
 F &= AB + \bar{C}D + \bar{A}BCD \\
 &= AB + \bar{A}BCD + BCD + \bar{C}D \\
 &= AB + BCD + \bar{C}D \\
 &= AB + BCD + \bar{C}D + BD \\
 &= AB + \bar{C}D + BD
 \end{aligned}$$




initial implicants

consensus th.

absorption th.

consensus th.

absorption th.

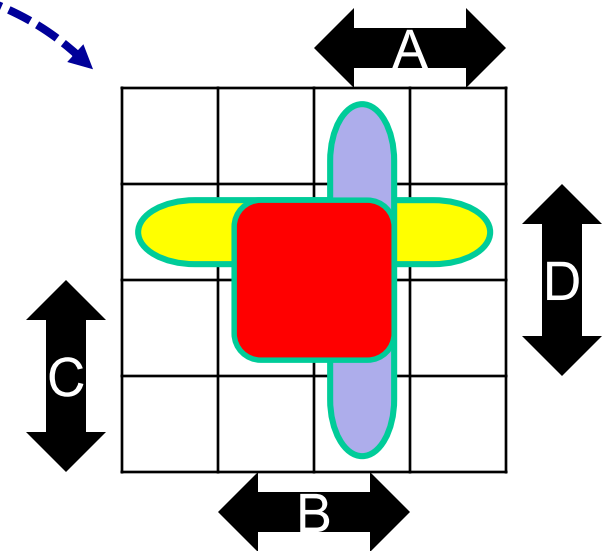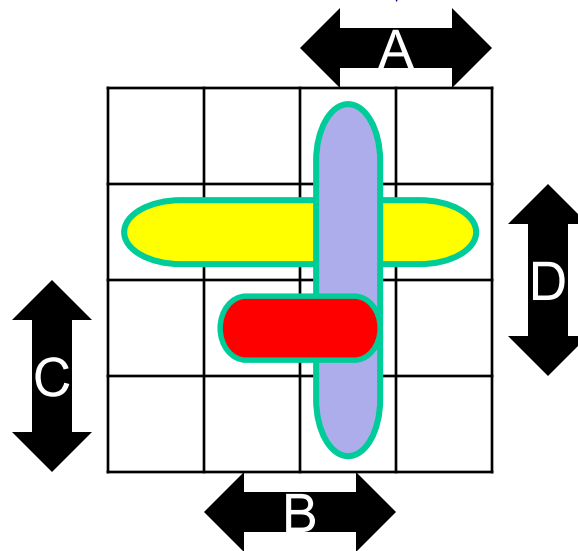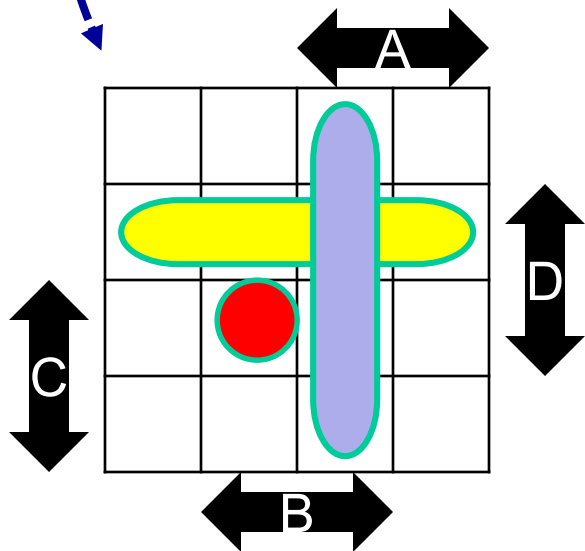


Minterms Covered by a Product

- A product from which k variables have been eliminated, covers 2^k minterms.
- Example: For four variables, A, B, C, D

Product AC covers $2^2 = 4$ minterms:

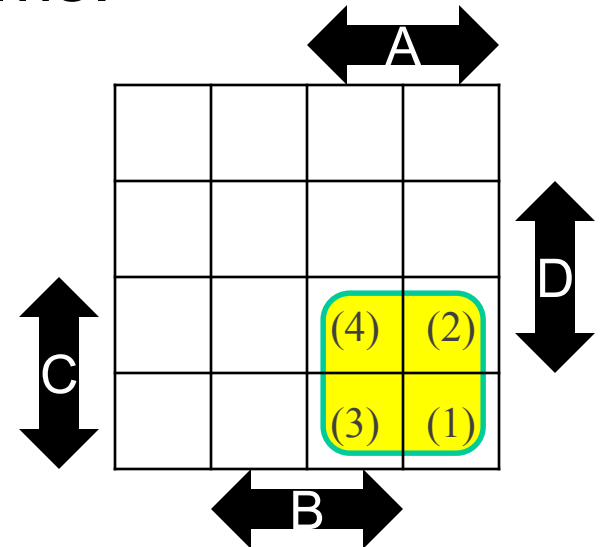- 1) $A \bar{B} C \bar{D}$
- 2) $A \bar{B} C D$
- 3) $A B C \bar{D}$
- 4) $A B C D$

Obtained by inserting the eliminated variables in all possible ways.




Truth Table with Don't Cares

- ❑ Don't cares entries represent combinations that are impossible to happen
- ❑ Example: $X=1$ indicates an elevator at top, and $Y=1$ indicates elevator at ground \rightarrow X and Y can never be one at the same time
- ❑ Don't care entries can be assumed any value and can thus leverage the simplification process
- ❑ There can be more than one minimal grouping, as a result of don't cares

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>F</i>
0	0	0	0	<i>d</i>
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	<i>d</i>
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	<i>d</i>

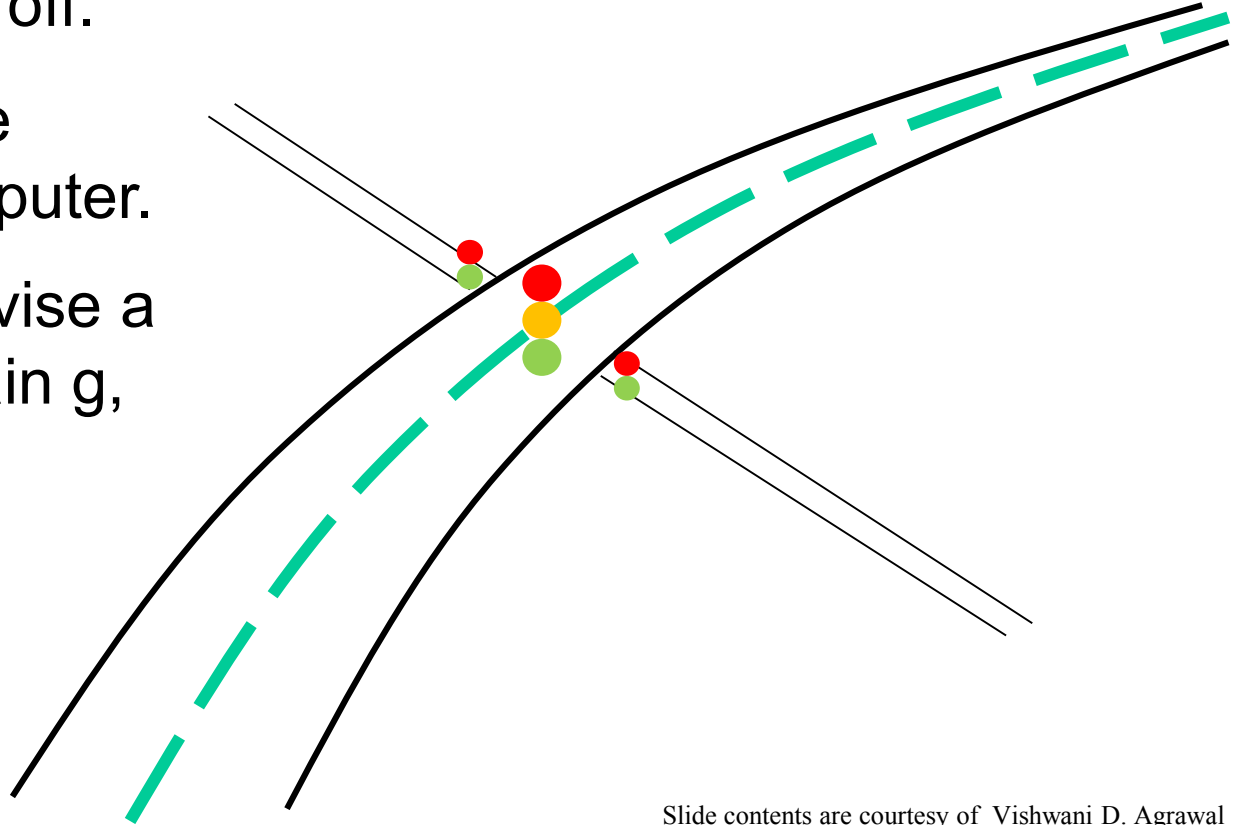
Example: Traffic Signals

- Consider two roads crossing:
 - Highway with traffic signal, red (R), yellow (Y) or green (G).
 - Rural road with red (r) or green (g) signal.
- Here R, Y, G, r and g are Boolean variables; 1 implies light is on, 0 means light is off.
- Highway signals are controlled by a computer.
- We only need to devise a digital circuit to obtain g, because $r = \bar{g}$.




Completely Specified Function

Truth Table				
0	0	0	0	0
2	0	1	0	0
4	1	0	0	1
6	1	1	0	0

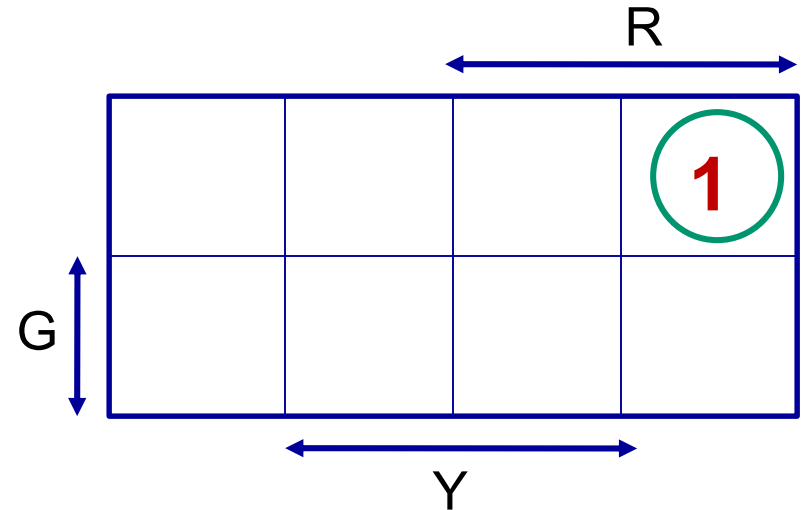


$$g = R \bar{Y} \bar{G}$$

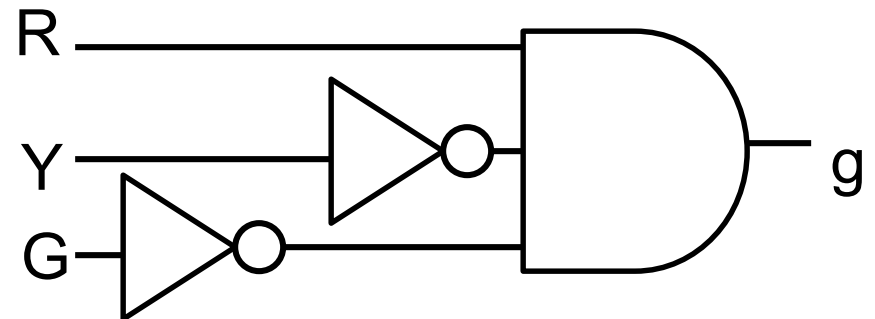

Incompletely Specified Function

Truth Table				
0	0	0	0	0
2	0	1	0	0
4	1	0	0	1
6	1	1	0	Φ

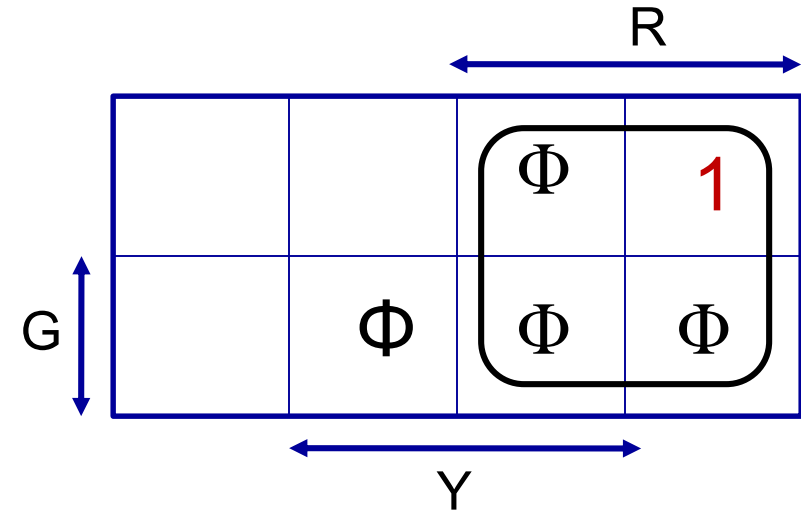


$$g = R$$


$$R \text{ ————— } g$$

Functions with Don't Care Minterms

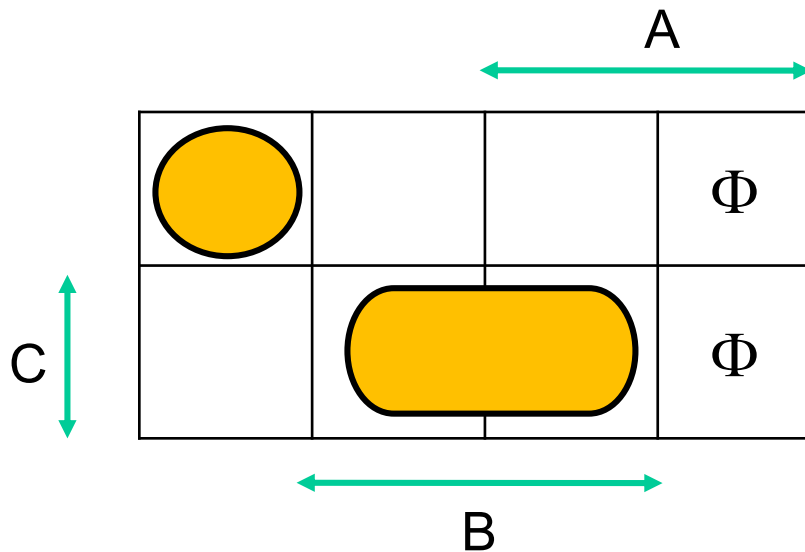- $F(A,B,C) = \sum m(0,3,7) + d(4,5)$
- Include don't care minterms when beneficial



$$F = B C + \bar{A} \bar{B} \bar{C}$$

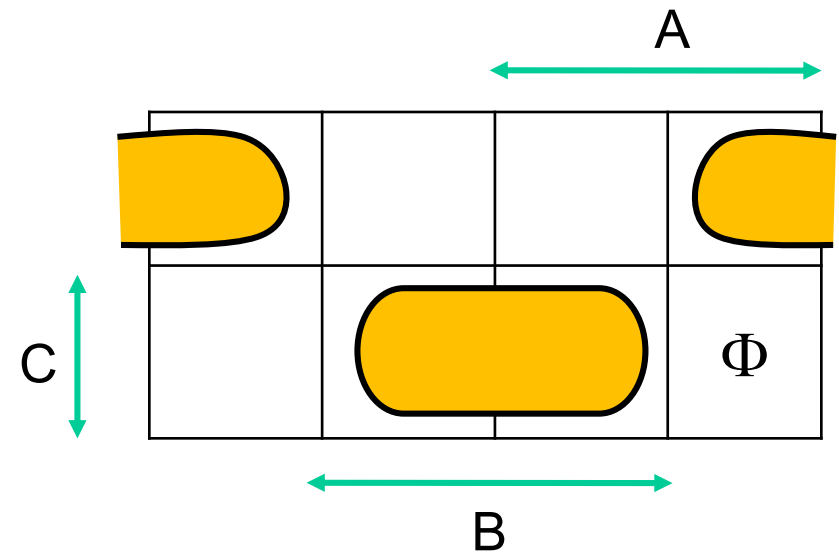

$$F = B C + \bar{B} \bar{C}$$

K-Maps and Don't Cares

- ❑ Don't care entries can be assumed any value and can thus leverage the simplification process
- ❑ There can be more than one minimal grouping, as a result of don't cares

$AB \backslash CD$	00	01	11	10
00	1			d
01		1	1	
11		1	1	
10	d			


$$F = \overline{B} \overline{C} \overline{D} + B D$$

$AB \backslash CD$	00	01	11	10
00	1			d
01		1	1	
11		1	1	
10	d			


$$F = \overline{A} \overline{B} \overline{D} + B D$$

Five-Variable K-Map

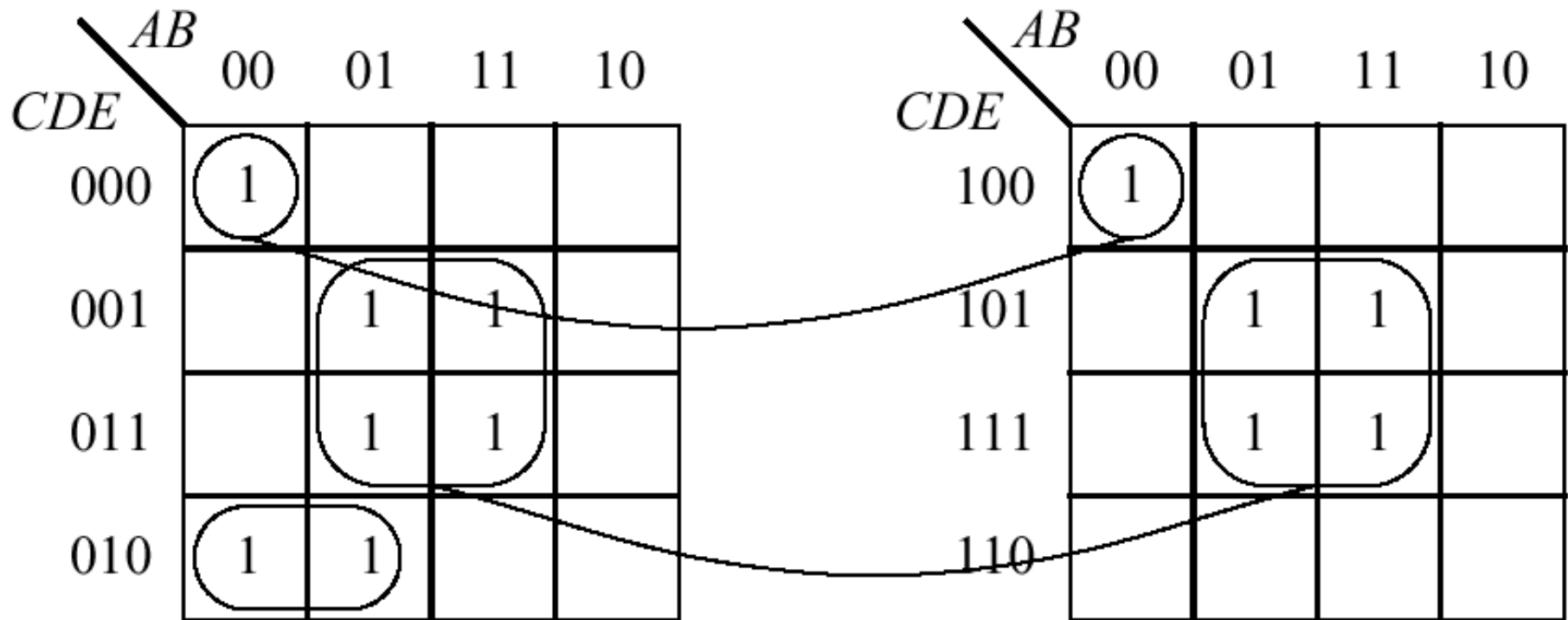- Visualize two 4-variable K-maps stacked one on top of the other; groupings are made in three dimensional cubes.



$$F = \overline{A}\overline{C}D\overline{E} + \overline{A}\overline{B}\overline{D}\overline{E} + BE$$

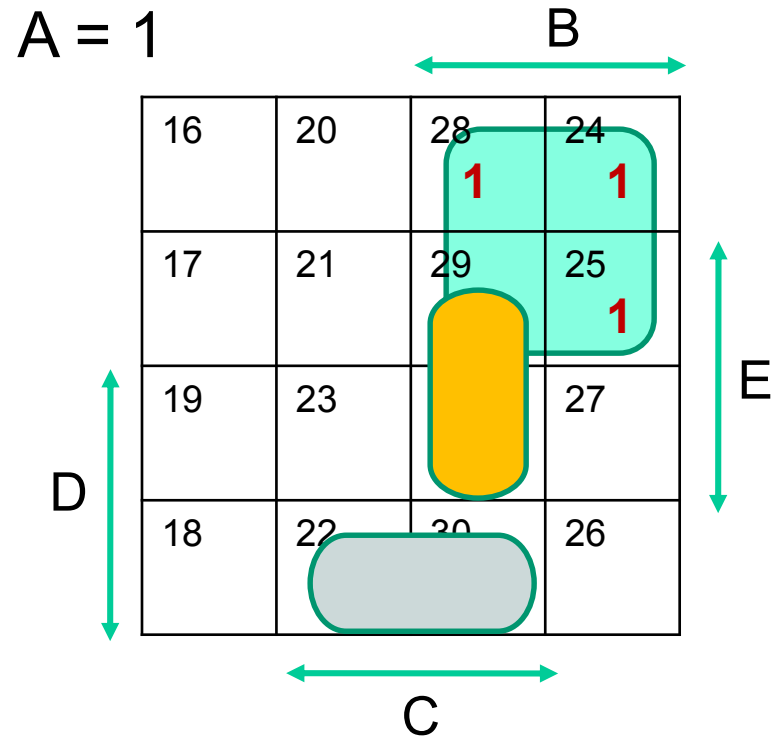
$$F(A,B,C,D,E) = \sum m(0,1,4,5,6,13,14,15,22,24,25,28,29,30,31)$$




The logo for the University of Maryland, Baltimore (UMBC) Center for Systems Engineering and Engineering (CSEE). It is a blue diamond shape with a white border. Inside the diamond, the text "CSEE" is at the top, "Computer Science / Electrical Engineering" is in the middle, and "UMBC" is at the bottom.

Six-Variable K-Map

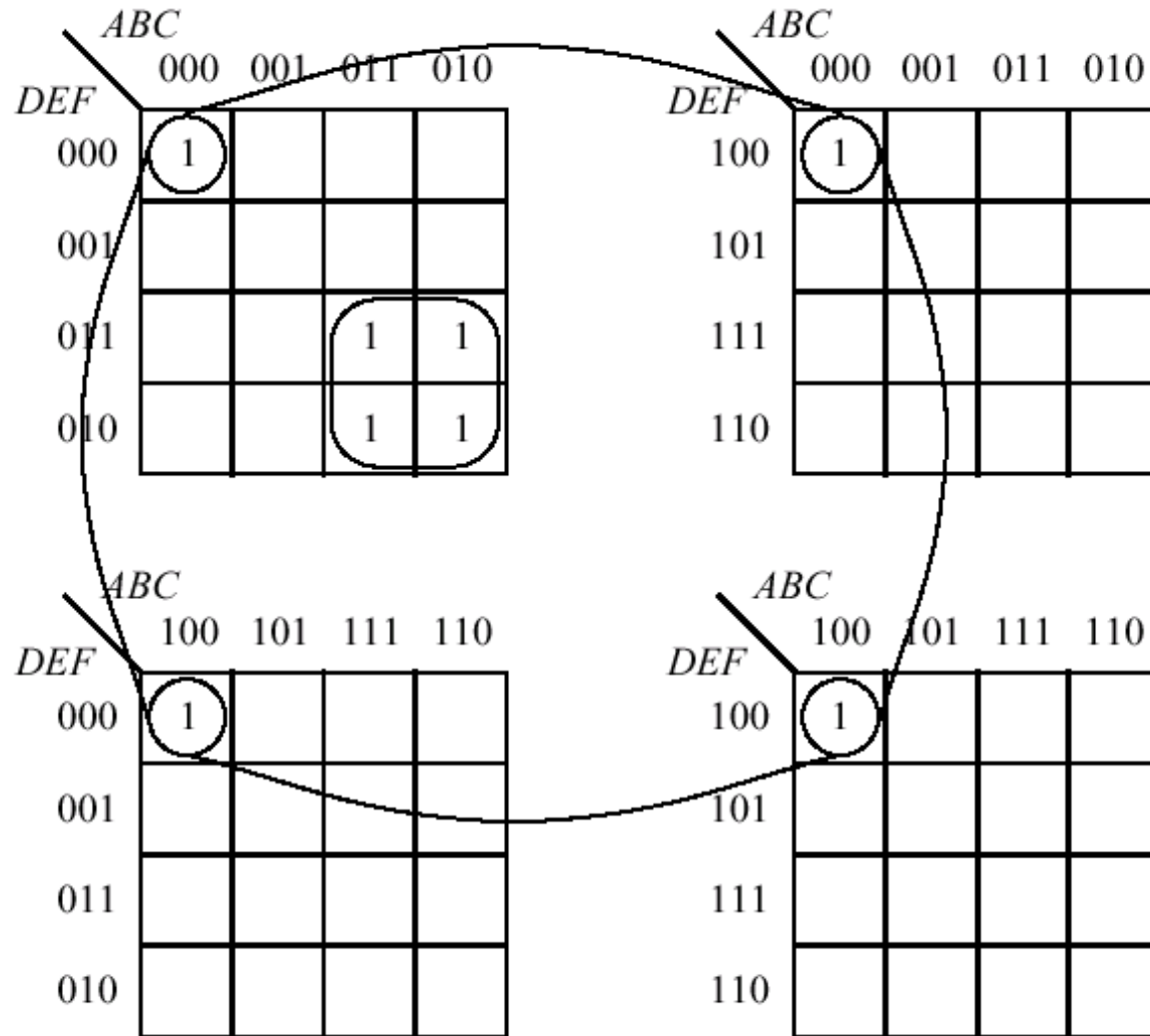
- Visualize four 4-variable K-maps stacked one on top of the other; groupings are made in three dimensional cubes.



$$G = \overline{B} \overline{C} \overline{E} \overline{F} + \overline{A} B \overline{D} E$$

Map-Entered Variables

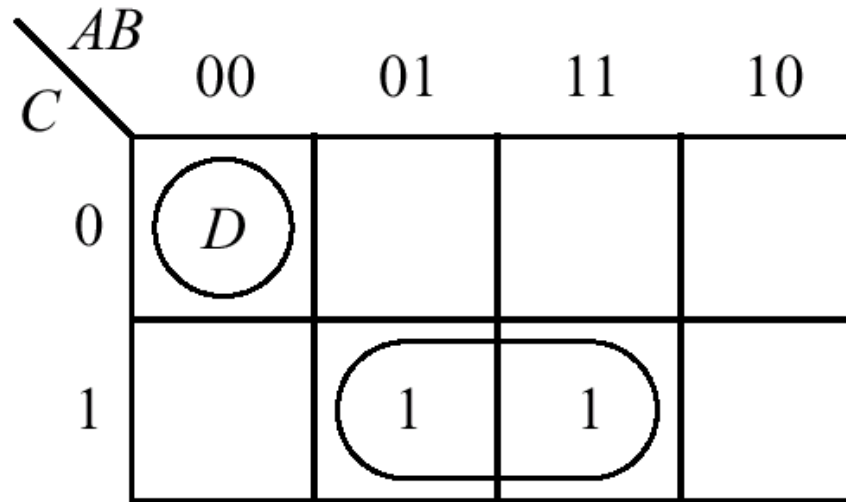- Allowing variables to be entered in the K-map simplifies the representation of some functions (less map size)




$$F = B C + \overline{A} \overline{B} \overline{C} D$$

- The map-entered variable D is treated as a 1 for the purpose of grouping, which in this case results in a 1-group since there are no adjacent 1's to the D cell
- Notice that the variable D appears in the final expression

Multiple-Output Function

Need five products


Inputs				Outputs	
A	B	C	D	F1	F2
0	0	0	0	0	0
0	0	0	1	1	0
0	0	1	0	0	0
0	0	1	1	0	0
0	1	0	0	0	0
0	1	0	1	1	0
0	1	1	0	0	0
0	1	1	1	1	1
1	0	0	0	0	1
1	0	0	1	1	1
1	0	1	0	0	1
1	0	1	1	0	1
1	1	0	0	0	0
1	1	0	1	1	1
1	1	1	0	0	0
1	1	1	1	1	1

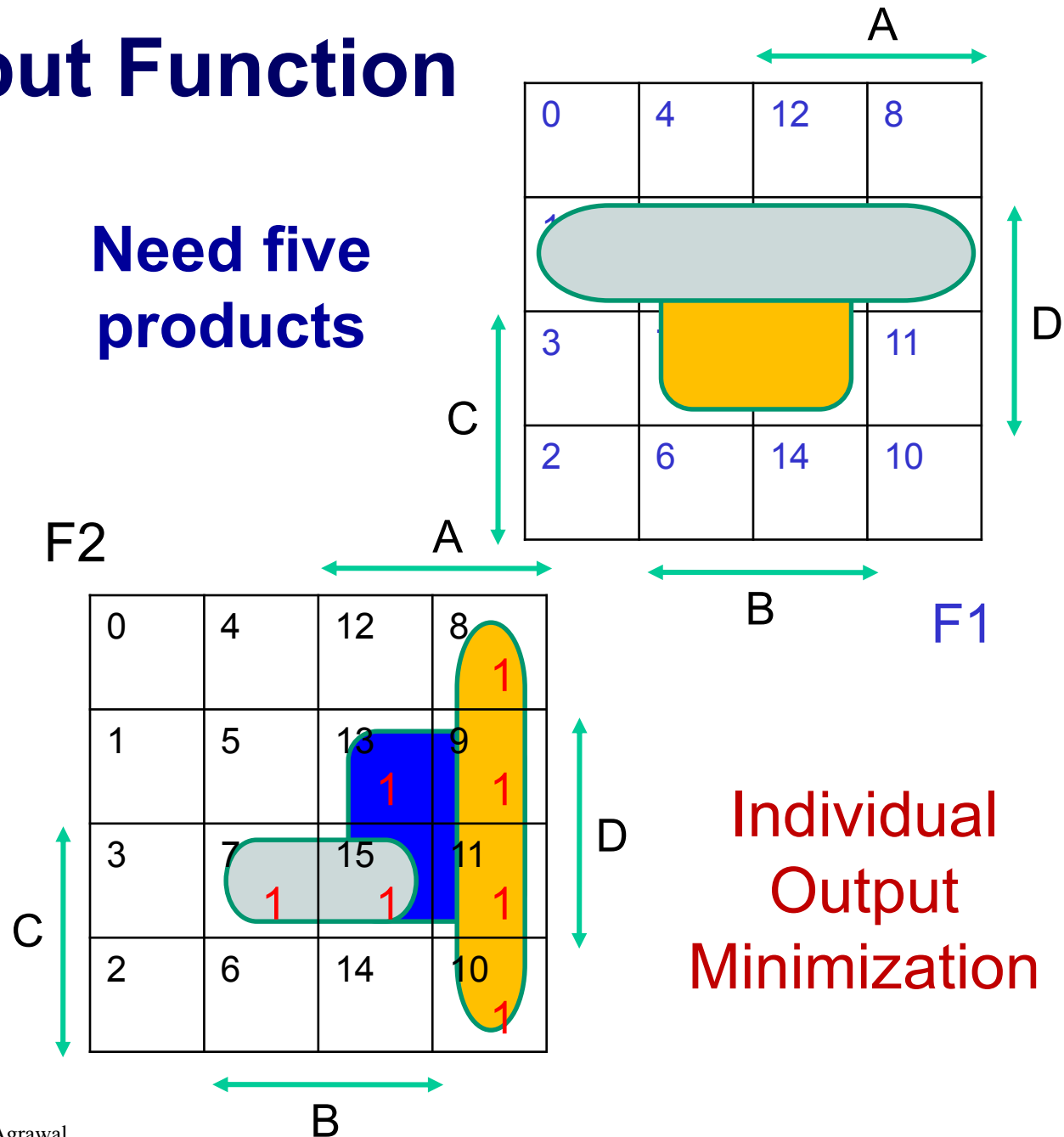

Multiple-Output Function

Inputs				Outputs	
A	B	C	D	F1	F2
0	0	0	0	0	0
0	0	0	1	1	0
0	0	1	0	0	0
0	0	1	1	0	0
0	1	0	0	0	0
0	1	0	1	1	0
0	1	1	0	0	0
0	1	1	1	1	1
1	0	0	0	0	1
1	0	0	1	1	1
1	0	1	0	0	1
1	0	1	1	0	1
1	1	0	0	0	0
1	1	0	1	1	1
1	1	1	0	0	0
1	1	1	1	1	1


Need **Four** products

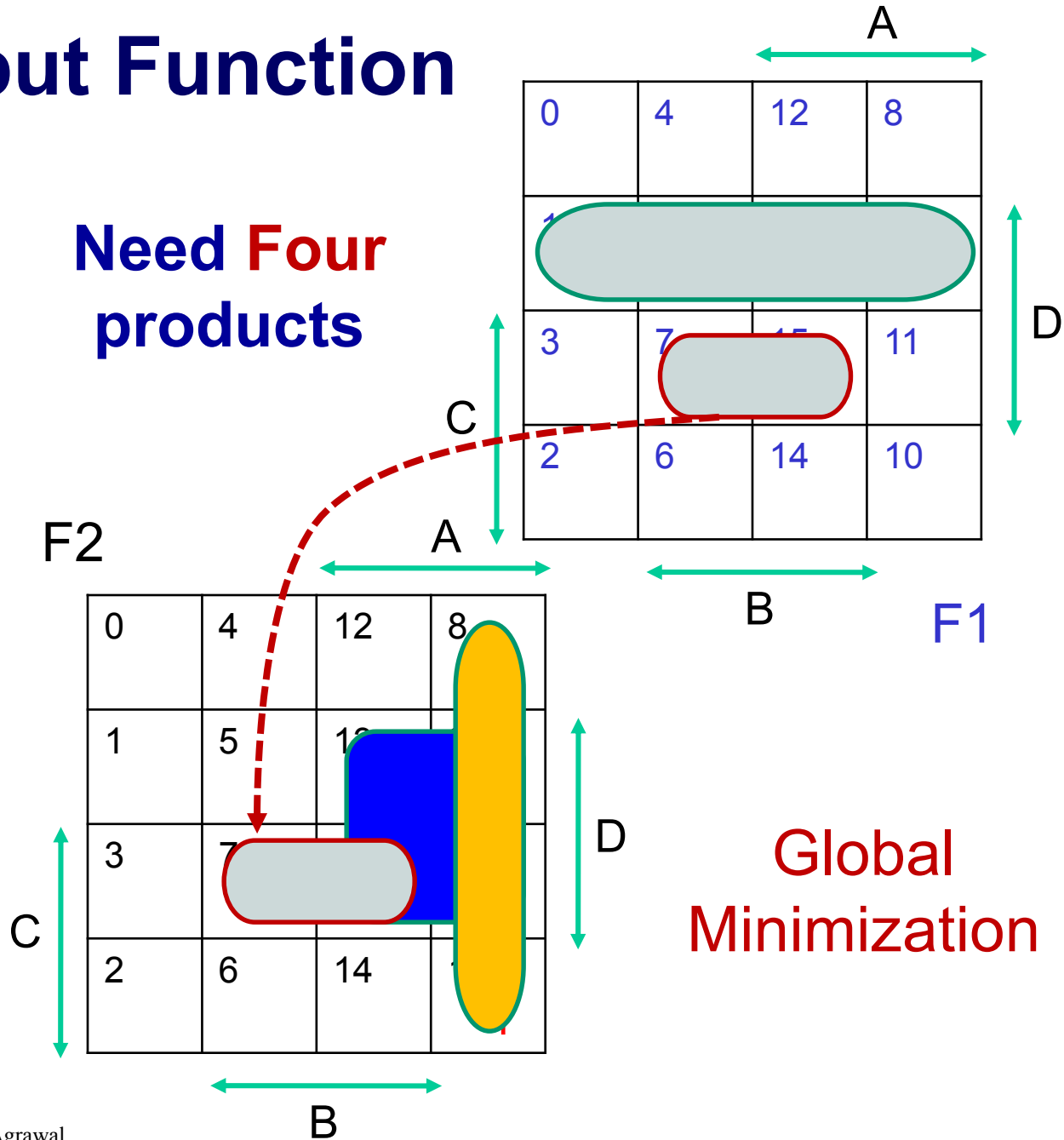


Minimized SOP and POS

- $$F(A,B,C,D) = \sum m(1,3,4,7,11) + d(5,12,13,14,15)$$
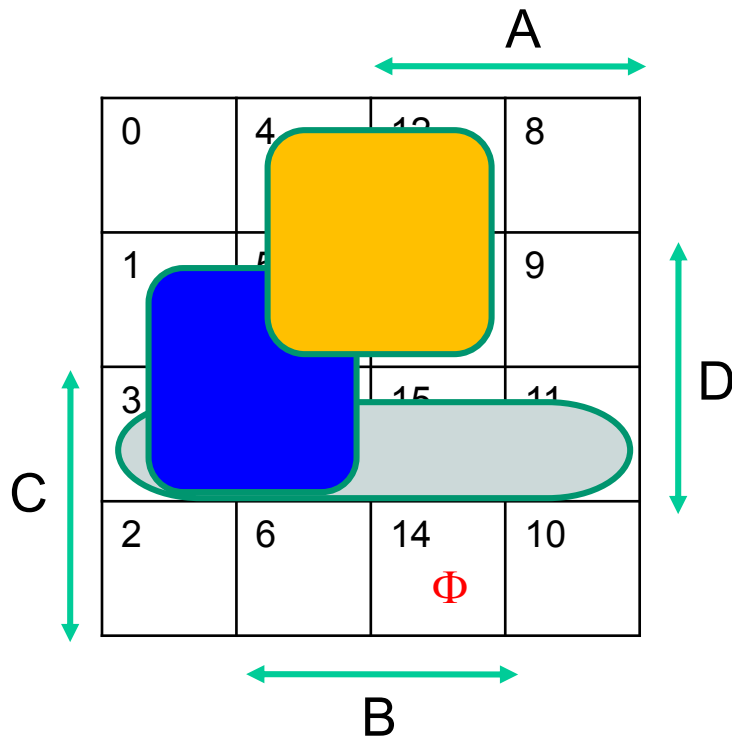
$$= \prod M(0,2,6,8,9,10) D(5,12,13,14,15)$$



$$F = B \bar{C} + \bar{A}D + CD$$

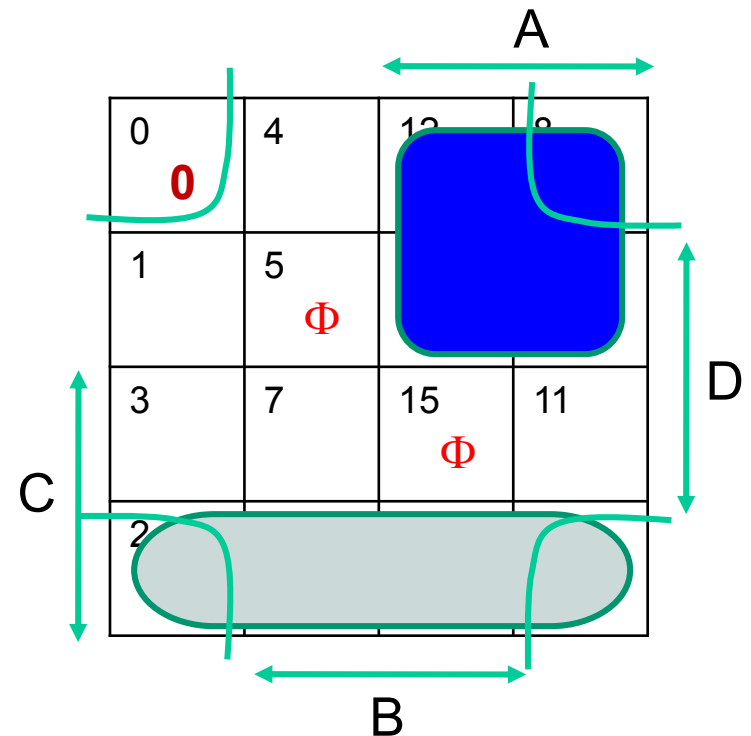


$$\bar{F} = \bar{B} \bar{D} + C \bar{D} + A \bar{C}$$

$$F = (B + D)(\bar{C} + D)(\bar{A} + C)$$


SOP and POS Circuits

- $F(A,B,C,D) = \sum m(1,3,4,7,11) + d(5,12,13,14,15)$
 $= \prod M(0,2,6,8,9,10) D(5,12,13,14,15)$

$$F = B \bar{C} + \bar{A}D + CD$$

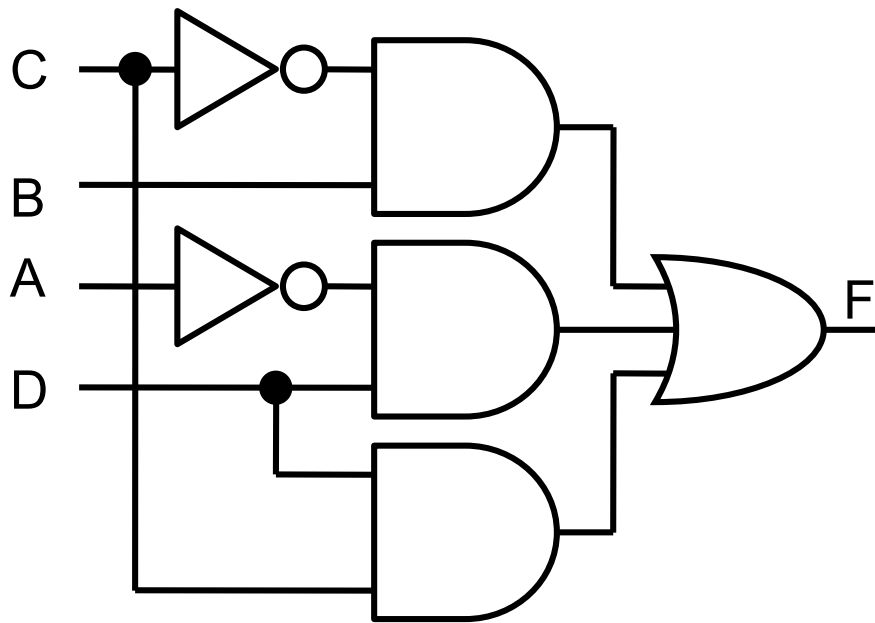
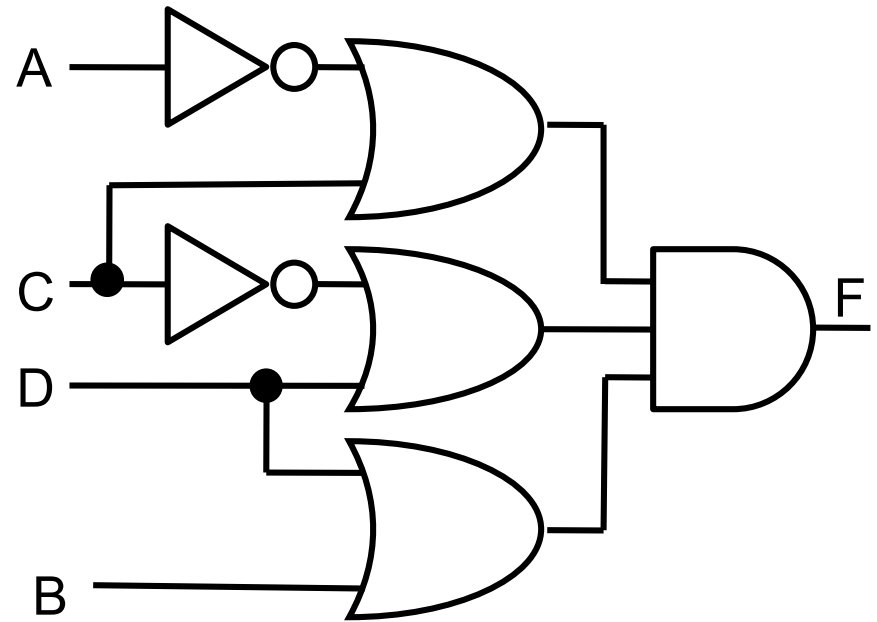
$$F = (B + D)(\bar{C} + D)(\bar{A} + C)$$



Are two circuits functionally Identical?

Conclusion

□ Summary

- ➔ Reduction of combinational logic
(Types, Goals, Methodology, Fundamental Concept)
- ➔ The Karnaugh map method
(Basic concept, Implicants, prime implicants)
- ➔ Extended K-map procedure
(Minterm covering, Multi-output optimization, map-entered variable)
- ➔ Optimization of incompletely specified functions
- ➔ Scalability limitation of the K-map method

□ Next Lecture

- ➔ The Quine-McCluskey algorithm
- ➔ Other circuit performance considerations

Reading assignment: Sections 3.1-3.7 in the textbook