

CMPE 411

Computer Architecture

Lecture 7

Multiplier's Design

September 21, 2017

[www.csee.umbc.edu/~younis/CMPE411/
CMPE411.htm](http://www.csee.umbc.edu/~younis/CMPE411/CMPE411.htm)



Lecture's Overview

□ Previous Lecture

- Constructing an Arithmetic Logic Unit
(Different blocks and gluing them together)
- Scaling bit operations to word sizes
(Ripple carry adder, MIPS ALU)
- Optimization for carry handling
(Measuring performance, Carry lookahead)

□ This Lecture

- Algorithms for multiplying unsigned numbers
- Booth's algorithm for signed number multiplication
- Multiple hardware design for integer multiplier


Multiply Unsigned

- Paper and pencil example (unsigned):

$$\begin{array}{r} \text{Multiplicand} \quad 1000 \\ \text{Multiplier} \quad \times 1001 \\ \hline 1000 \\ 0000 \\ 0000 \\ 1000 \\ \hline \text{Product} \quad 01001000 \end{array}$$

- m bits \times n bits = $m+n$ bit product (Overflow ?)
- Binary makes it easy:
 - 0 \Rightarrow place 0 (0 \times multiplicand)
 - 1 \Rightarrow place a copy (1 \times multiplicand)
- 4 versions of multiply hardware & algorithm:
 - successive refinement


Unsigned Combinational Multiplier

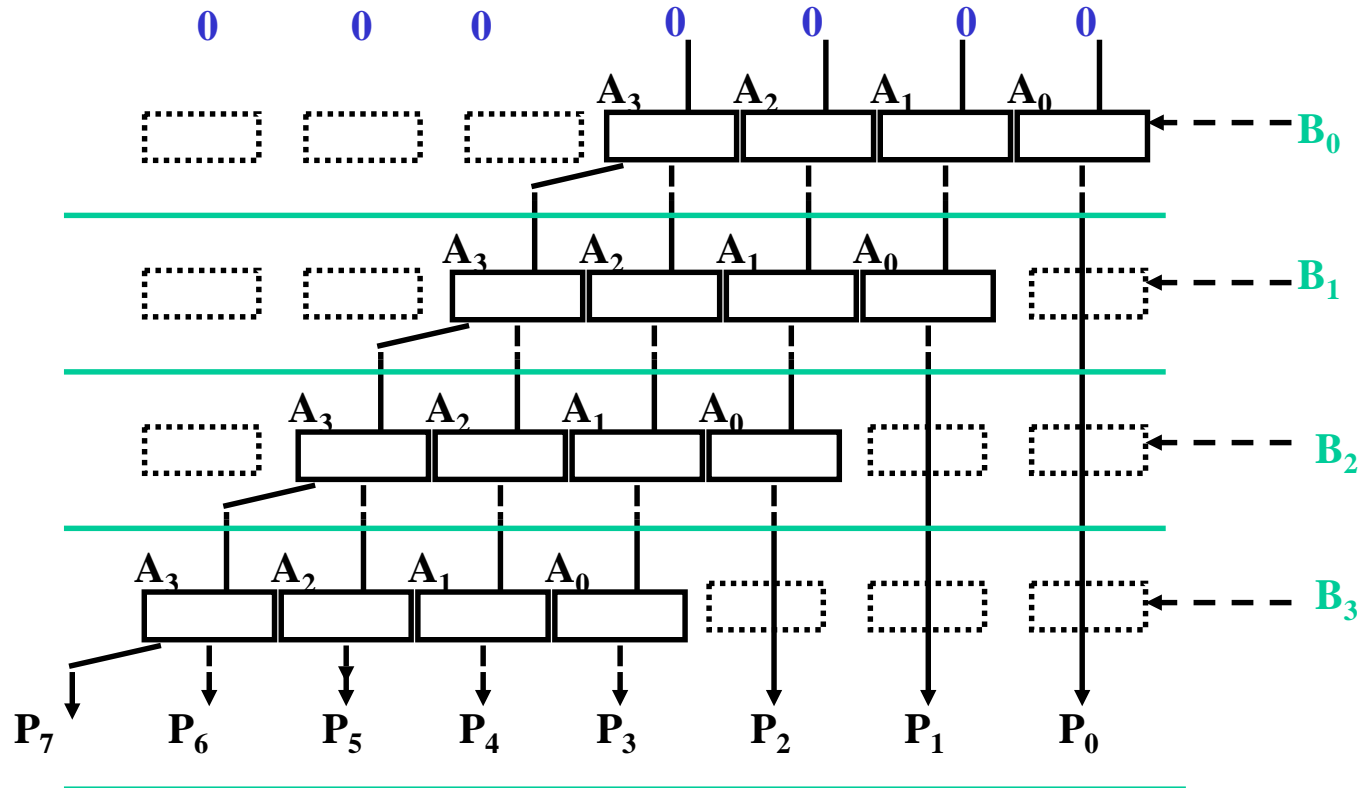

- ❑ Stage i accumulates $A * 2^i$ if $B_i == 1$
- ❑ At each stage shift A left ($\times 2$)
- ❑ Use next bit of B to determine whether to add in shifted multiplicand
- ❑ Accumulate $2n$ bit partial product at each stage

Unsigned shift-add multiplier (version 1)

- ❑ 64-bit Multiplicand register, 64-bit ALU, 64-bit Product register, and 32-bit Multiplier register
- ❑ The 32-bit value of the Multiplicand starts in the right half of the 64-bit register
- ❑ The Multiplier is shifted in the opposite direction of the Multiplicand shift
- ❑ The product register starts with an initial value of zero
- ❑ Control decides when to shift the Multiplicand and the Multiplier registers and when to write new value into the product register

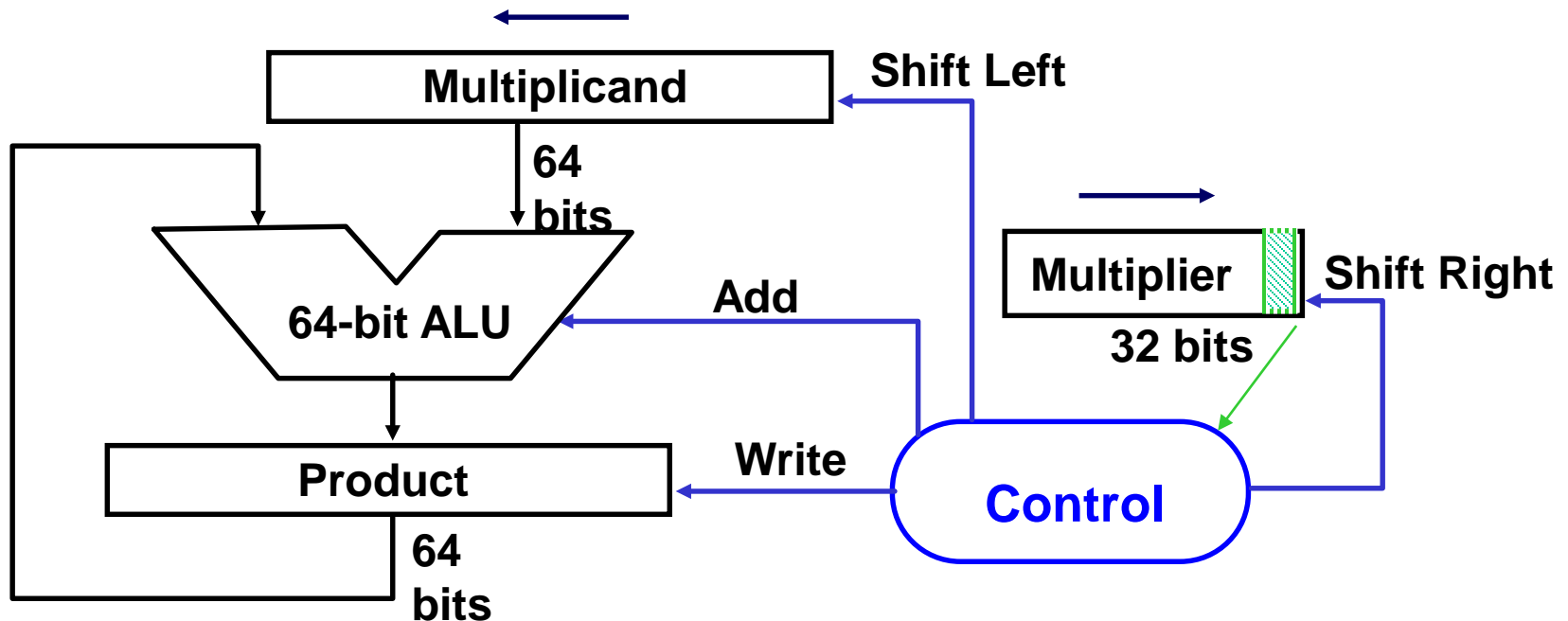


Multiplier = datapath + control

Multiply Algorithm Version 1

Multiplying two n -bit numbers needs a maximum of $2n^2$ addition operations mostly for adding zeros

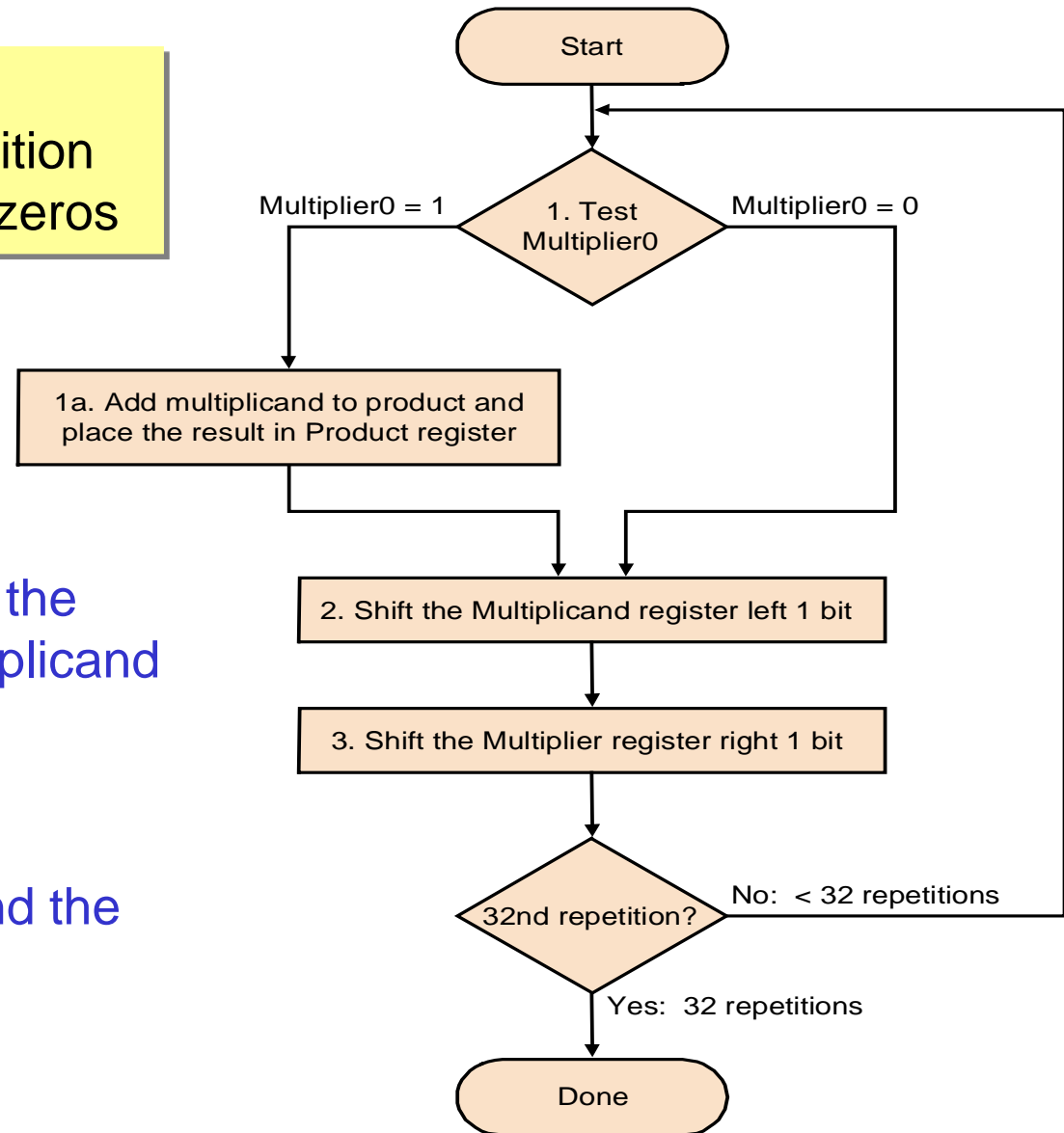- ➔ If the least significant bit of the multiplier is 1, add the multiplicand to the product
- ➔ If not, go to the next bit
- ➔ shift the multiplicand left and the multiplier right
- ➔ Repeat for 32 times




An Example

Follow the multiplication algorithm (version 1) to get the product of 2×3 using only 4-bit binary representation


Iteration	Step	Multiplier	Multiplicand	Product
0	Initial value	0011	0000 0010	0000 0000
1	1a: $1 \Rightarrow \text{Prod} = \text{Prod} + \text{Mcand}$	0011	0000 0010	0000 0010
	2: Shift left Multiplicand	0011	0000 0100	0000 0010
	3: Shift right Multiplier	0001	0000 0100	0000 0010
2	1a: $1 \Rightarrow \text{Prod} = \text{Prod} + \text{Mcand}$	0001	0000 0100	0000 0110
	2: Shift left Multiplicand	0001	0000 1000	0000 0110
	3: Shift right Multiplier	0000	0000 1000	0000 0110
3	1a: $0 \Rightarrow$ no operation	0000	0000 1000	0000 0110
	2: Shift left Multiplicand	0000	0001 0000	0000 0110
	3: Shift right Multiplier	0000	0001 0000	0000 0110
4	1a: $0 \Rightarrow$ no operation	0000	0001 0000	0000 0110
	2: Shift left Multiplicand	0000	0010 0000	0000 0110
	3: Shift right Multiplier	0000	0010 0000	0000 0110

Multiply Hardware Version 2


- ❑ Since half of the 64-bit Multiplicand are zeros, a 64-bit ALU looks wasteful in the first version of multiplier
- ❑ Uses only 32-bit Multiplicand register, 32-bit ALU, 64-bit Product register, and 32-bit Multiplier register
- ❑ Since the least significant bits of the product would not change, the product could be shifted to the right instead of shifting the multiplicand
- ❑ The most significant 32-bits would be used by the ALU as a result register

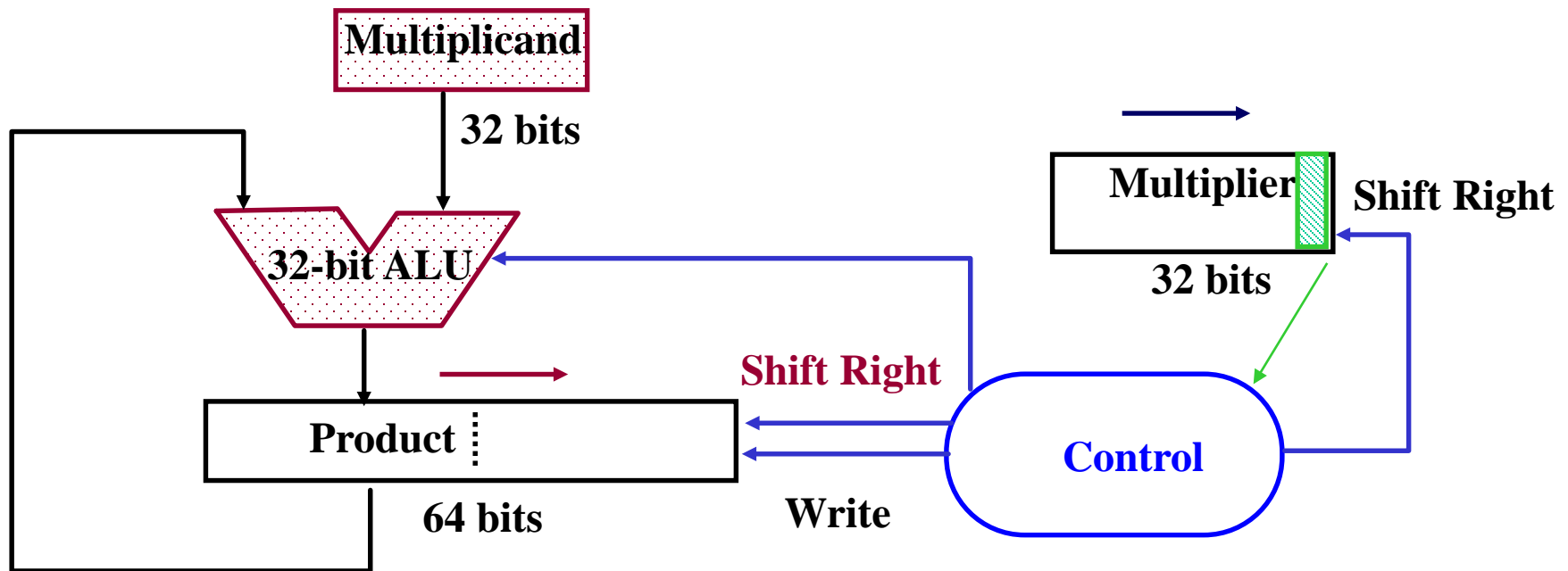

Multiply Algorithm Version 2

 

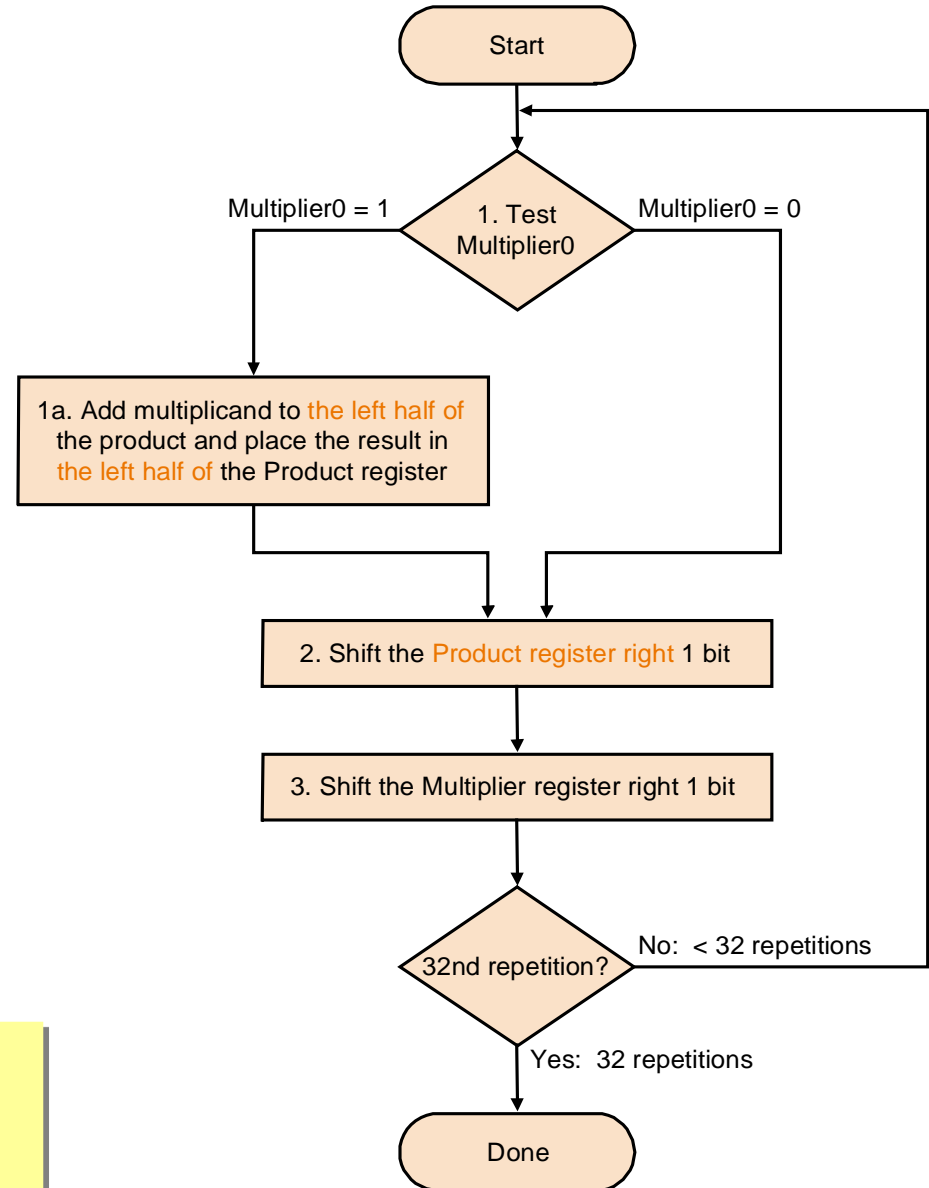Multiplicand stays still and product moves right



* Figure is courtesy of Dave Patterson


An Example

Follow the multiplication algorithm (version 2) to get the product of 2×3 using only 4-bit binary representation

Iteration	Step	Multiplier	Multiplicand	Product
0	Initial value	0011	0010	0000 0000
1	1a: $1 \Rightarrow \text{Prod} = \text{Prod} + \text{Mcand}$	0011	0010	0010 0000
	2: Shift right Product	0011	0010	0001 0000
	3: Shift right Multiplier	0001	0010	0001 0000
2	1a: $1 \Rightarrow \text{Prod} = \text{Prod} + \text{Mcand}$	0001	0010	0011 0000
	2: Shift right Product	0001	0010	0001 1000
	3: Shift right Multiplier	0000	0010	0001 1000
3	1a: $0 \Rightarrow$ no operation	0000	0010	0001 1000
	2: Shift right Product	0000	0010	0000 1100
	3: Shift right Multiplier	0000	0010	0000 1100
4	1a: $0 \Rightarrow$ no operation	0000	0010	0000 1100
	2: Shift right Product	0000	0010	0000 0110
	3: Shift right Multiplier	0000	0010	0000 0110


Multiply Hardware Version 3

- ❑ Product register wastes space that exactly matches size of multiplier
⇒ combine Multiplier register and Product register
- ❑ Uses only 32-bit Multiplicand register, 32-bit ALU, 64-bit Product register, and 0-bit Multiplier register
- ❑ Shifting the product register would remove the least significant bit which is already used in the multiplication
- ❑ The most significant 32-bits are still being used by ALU as a result register

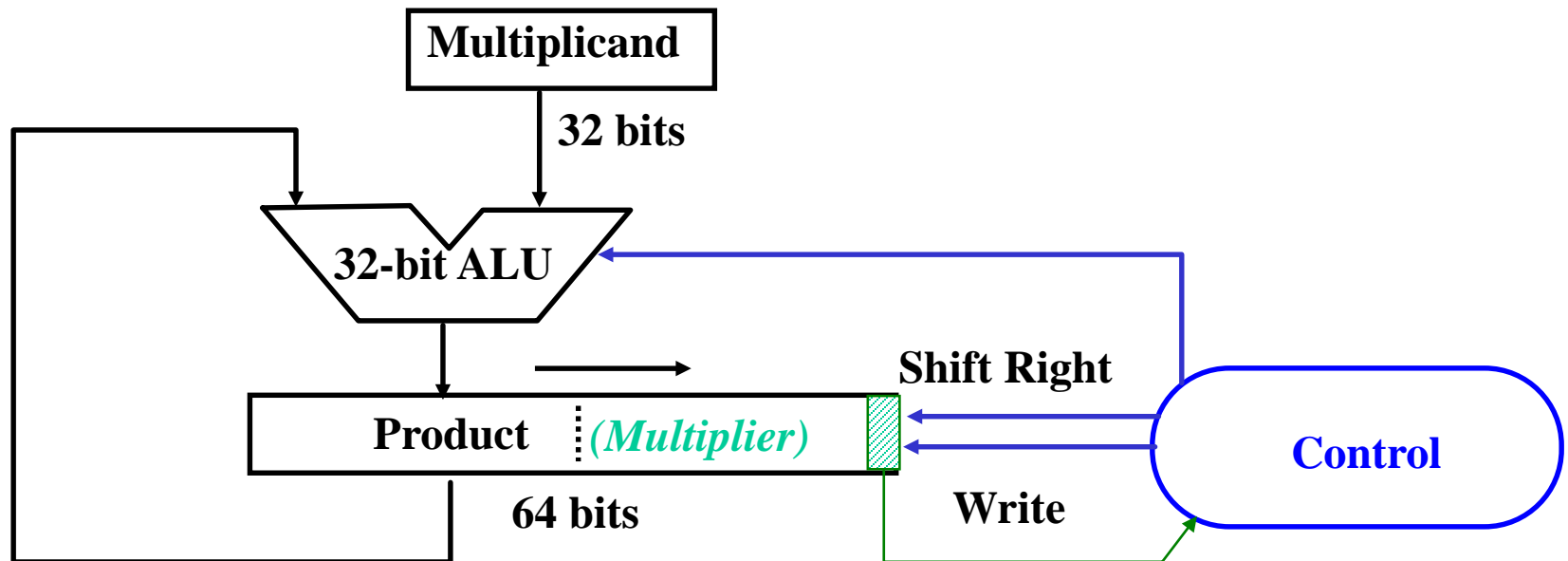

Multiply Algorithm Version 3

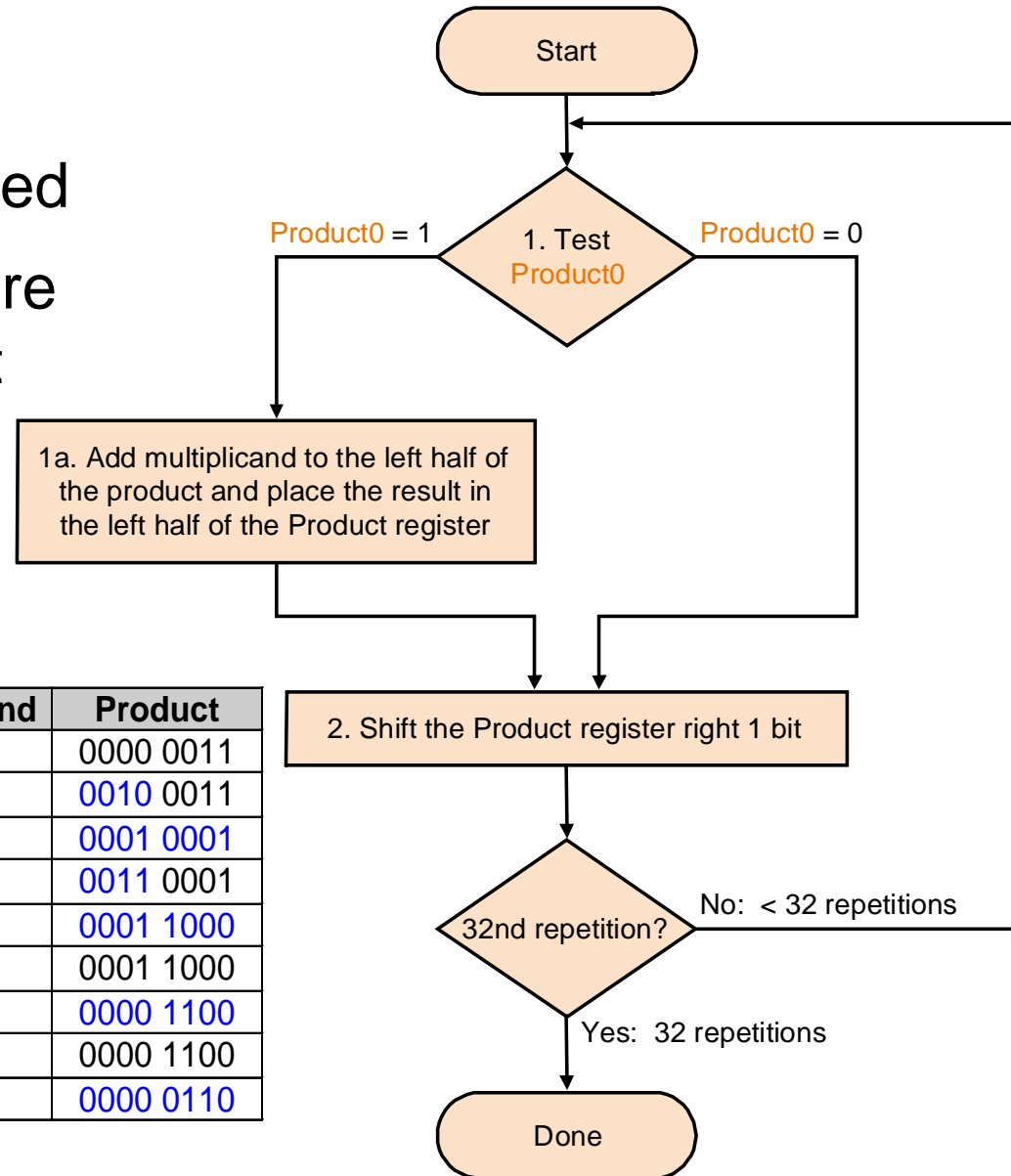- 2 steps per bit because Multiplier & Product combined
- MIPS registers Hi and Lo are left and right half of Product



Iteration	Step	Multiplicand	Product
0	Initial value	0010	0000 0011
1	1a: 1 \Rightarrow Prod = Prod + Mcand	0010	0010 0011
	2: Shift right Product	0010	0001 0001
2	1a: 1 \Rightarrow Prod = Prod + Mcand	0010	0011 0001
	2: Shift right Product	0010	0001 1000
3	1a: 0 \Rightarrow no operation	0010	0001 1000
	2: Shift right Product	0010	0000 1100
4	1a: 0 \Rightarrow no operation	0010	0000 1100
	2: Shift right Product	0010	0000 0110

The product of 2×3

Multiplying Signed Number

- ① Easiest solution is to make both positive & remember whether to complement product when done (leave out the sign bit, run for 31 steps)
- ② Apply definition of 2's complement \Rightarrow need to sign-extend partial products

Example: multiply 1001 (-7) by 0010 (+2)

Iteration	Step	Multiplicand	Product
0	Initial value	1001	0000 0010
1	1a: 0 \Rightarrow no operation	1001	0000 0010
	2: Shift right Product	1001	0000 0001
2	1a: 1 \Rightarrow Prod = Prod + Mcand	1001	1001 0001
	2: Shift right Product	1001	1100 1000
3	1a: 0 \Rightarrow no operation	1001	1100 1000
	2: Shift right Product	1001	1110 0100
4	1a: 0 \Rightarrow no operation	1001	1110 0100
	2: Shift right Product	1001	1111 0010

Does it work for all cases?

Multiply 0111 (+7) by 1110 (-2)

Iteration	Step	Multiplicand	Product
0	Initial value	0111	0000 1110
1	1a: 0 \Rightarrow no operation	0111	0000 1110
	2: Shift right Product	0111	0000 0111
2	1a: 1 \Rightarrow Prod = Prod + Mcand	0111	0111 0111
	2: Shift right Product	0111	0011 1011
3	1a: 0 \Rightarrow Prod = Prod + Mcand	0111	1010 1011
	2: Shift right Product	0111	1101 0101
4	1a: 0 \Rightarrow Prod = Prod + Mcand	0111	0100 0101
	2: Shift right Product	0111	0010 0010



Iteration	Step	Multiplicand	Product
0	Initial value	0111	1111 1110
1	1a: 0 \Rightarrow no operation	0111	1111 1110
	2: Shift right Product	0111	1111 0111
2	1a: 1 \Rightarrow Prod = Prod + Mcand	0111	0110 0111
	2: Shift right Product	0111	0011 0011
3	1a: 0 \Rightarrow Prod = Prod + Mcand	0111	1010 0011
	2: Shift right Product	0111	1101 0001
4	1a: 0 \Rightarrow Prod = Prod + Mcand	0111	0110 0001
	2: Shift right Product	0111	0011 0000



Multiply 1111 (-7) by 1110 (-2)

Iteration	Step	Multiplicand	Product
0	Initial value	1001	0000 1110
1	1a: 0 \Rightarrow no operation	1001	0000 1110
	2: Shift right Product	1001	0000 0111
2	1a: 1 \Rightarrow Prod = Prod + Mcand	1001	1001 0111
	2: Shift right Product	1001	1100 1011
3	1a: 0 \Rightarrow Prod = Prod + Mcand	1001	0101 0011
	2: Shift right Product	1001	0010 1001
4	1a: 0 \Rightarrow Prod = Prod + Mcand	1001	1011 0100
	2: Shift right Product	1001	1101 0010



Iteration	Step	Multiplicand	Product
0	Initial value	1001	1111 1110
1	1a: 0 \Rightarrow no operation	1001	1111 1110
	2: Shift right Product	1001	1111 0111
2	1a: 1 \Rightarrow Prod = Prod + Mcand	1001	1000 0111
	2: Shift right Product	1001	1100 0011
3	1a: 0 \Rightarrow Prod = Prod + Mcand	1001	0101 0011
	2: Shift right Product	1001	0010 1001
4	1a: 0 \Rightarrow Prod = Prod + Mcand	1001	1011 0100
	2: Shift right Product	1001	1101 0010



Multiplying Signed Number

- ① Easiest solution is to make both positive & remember whether to complement product when done (leave out the sign bit, run for 31 steps)
- ② Apply definition of 2's complement \Rightarrow need to sign-extend partial products

Example: multiply 1001 (-7) by 0010 (+2)

Iteration	Step	Multiplicand	Product
0	Initial value	1001	0000 0010
1	1a: 0 \Rightarrow no operation	1001	0000 0010
	2: Shift right Product	1001	0000 0001
<div>Does NOT it work for all cases?</div>			
3	1a: 0 \Rightarrow no operation	1001	1100 1000
	2: Shift right Product	1001	1110 0100
4	1a: 0 \Rightarrow no operation	1001	1110 0100
	2: Shift right Product	1001	1111 0010

- ③ Booth's Algorithm is elegant way to multiply signed numbers using same hardware as before and save cycles



Motivation for Booth's Algorithm

- Example $2 \times 6 = 0010 \times 0110$:

	0010	
x	0110	
+	0000	shift (0 in multiplier)
+	0010	add (1 in multiplier)
+	0010	add (1 in multiplier)
+	0000	shift (0 in multiplier)
	<u>00001100</u>	

- ALU with add or subtract gets same result in more than one way:

$$6 = -2 + 8$$

$$0110 = -00010 + 01000 = 11110 + 01000$$

- Booth observed that there are multiple ways to compute a product with the ability to add and subtract

	0010	
x	0110	
+	0000	shift (0 in multiplier)
-	0010	sub (first 1 in multiplication)
+	0000	shift (mid string of 1s)
+	0010	add (prior step had last 1)
	<u>00001100</u>	



* Slide is courtesy of Dave Patterson

Intuition behind Booth's Algorithm

- ❑ Which of the following decimal multiplications is easier?

$$789634 \times 10001 \quad \text{and} \quad 789634 \times 9999$$

- ❑ How about doing the second multiplication as follows:

$$789634 \times 9999 = 789634 \times (10000 - 1)$$

- ❑ Let's consider binary, which is of the following involves fewer additions

→ $1101 \times 0100 \Rightarrow$ needs 1 8-bit numbers addition = 8 1-bit addition

→ $1101 \times 0111 \Rightarrow$ needs 3 8-bit numbers addition = 24 1-bit addition

→ $1101 \times 0111 = 1101 \times (1000 - 0001)$

\Rightarrow needs 1 8-bit addition and 1 8-bit subtraction

- ❑ Booth's observed and proved that this can be partially applied to multiplication of long binary numbers

- ❑ **Advantage:**

→ Fast multiplication (for consecutive 0's or 1's in the multiplier).

→ Handling of signed multiplication as well


- ❑ For more about the theoretical basis of Booth Algorithm, you may check:
http://fourier.eng.hmc.edu/e85_old/lectures/arithmetic_html/node10.html



Booth's Algorithm

Current bit	Bit to the right	Explanation	Example
1	0	Beginning of a run of 1s	0000111 1 000
1	1	Middle of a run of 1s	00001 11 1000
0	1	End of a run of 1s	0000 1 111000
0	0	Middle of a run of 0s	000 01111000

 End of run Middle of run Beginning of run



- Depending on the current and previous bits, do one of the following
 - 00: Middle of a string of 0s \Rightarrow no arithmetic operation
 - 01: End of a string of 1s \Rightarrow add the multiplicand to the left half of the product
 - 10: Beginning of a string of 1s \Rightarrow subtract multiplicand from left half of the product
 - 11: Middle of a string of 1s \Rightarrow no arithmetic operation
- Shift the Product register to the right for 1 bit

Booth's algorithm works for both signed and unsigned numbers

Example (unsigned numbers)

Compare the multiplication algorithm (version 3) and Booth's algorithm applied to getting the product of 2×6 using only 4-bit binary representation

Multiplicand	Original Algorithm		Booth's Algorithm	
	Step	Product	Step	Product
0010	Initial value	0000 0110	Initial value	0000 0110 0
0010	1a: 0 \Rightarrow no operation	0000 0110	1a: 00 \Rightarrow no operation	0000 0110 0
0010	2: Shift right Product	0000 0011	2: Shift right Product	0000 0011 0
0010	1a: 1 \Rightarrow Prod = Prod + Mcand	0010 0011	1a: 10 \Rightarrow Prod = Prod - Mcand	1110 0011 0
0010	2: Shift right Product	0001 0001	2: Shift right Product	1111 0001 1
0010	1a: 1 \Rightarrow Prod = Prod + Mcand	0011 0001	1a: 11 \Rightarrow no operation	1111 0001 1
0010	2: Shift right Product	0001 1000	2: Shift right Product	1111 1000 1
0010	1a: 0 \Rightarrow no operation	0001 1000	1a: 01 \Rightarrow Prod = Prod + Mcand	0001 1000 1
0010	2: Shift right Product	0000 1100	2: Shift right Product	0000 1100 0

- ☐ Booth's algorithm uses both the current bit and the previous bit to determine its course of action
- ☐ Extend the sign when shifting to preserve the sign (*arithmetic right shift*)

Example (signed numbers)

Follow Booth's algorithm to get the product of 2×-3 using only 4-bit binary representation


Iteration	Step	Multiplicand	Product
0	Initial value	0010	0000 1101 0
1	1a: 10 \Rightarrow Prod = Prod - Mcand	0010	1110 1101 0
	2: Shift right Product	0010	1111 0110 1
2	1a: 01 \Rightarrow Prod = Prod + Mcand	0010	0001 0110 1
	2: Shift right Product	0010	0000 1011 0
3	1a: 10 \Rightarrow Prod = Prod - Mcand	0010	1110 1011 0
	2: Shift right Product	0010	1111 0101 1
4	1a: 11 \Rightarrow no operation	0010	1111 0101 1
	2: Shift right Product	0010	1111 1010 1

Fast Multiplication

- ❑ Whether to add the multiplicand or not is known by looking at the individual multiplier's bits
- ❑ To multiply fast, one can provide a 32-bit adder for every bit in the multiplier
- ❑ The multiplier bit is ANDed with the multiplicand (each of its bits)

Why is this faster?

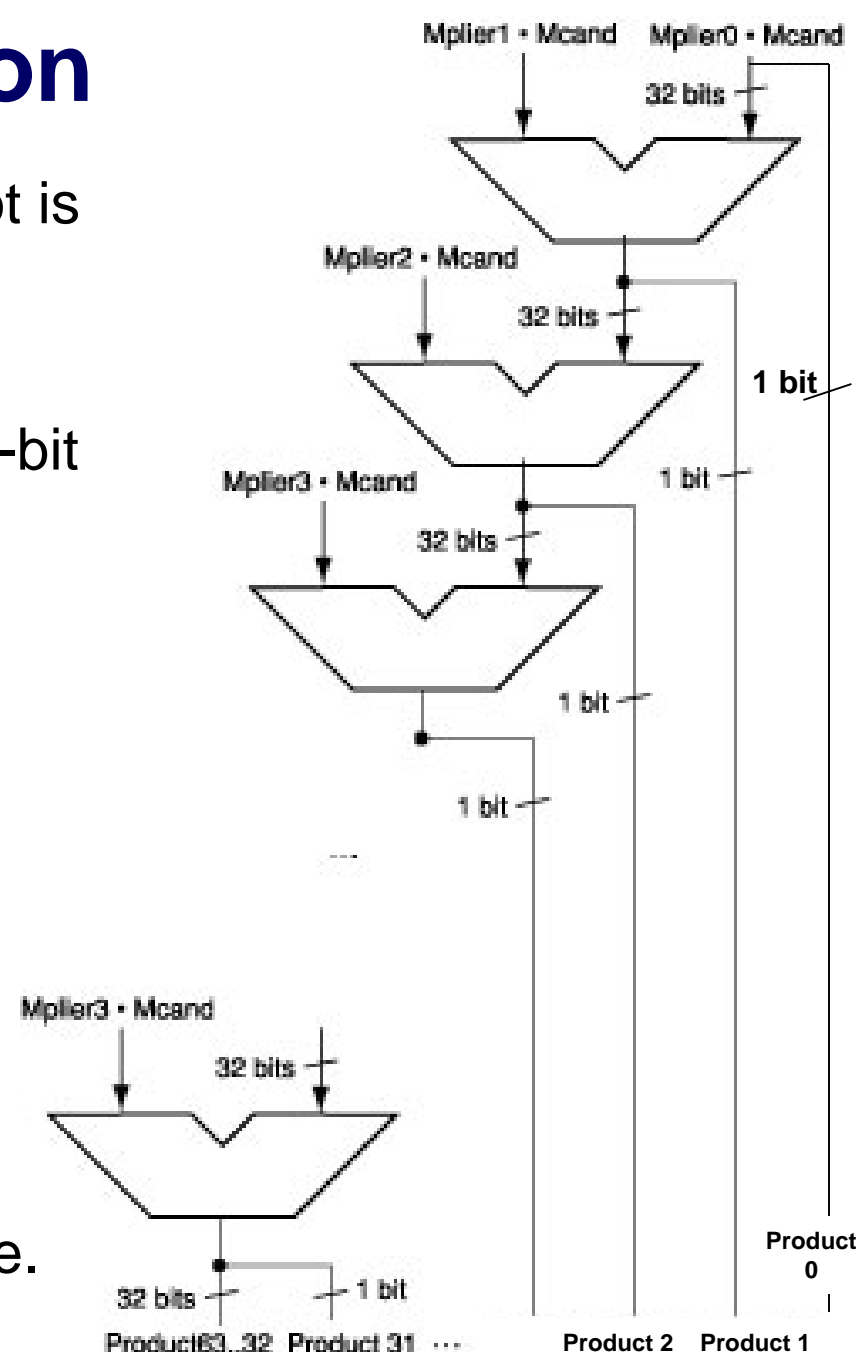- No data storage required (no need for clock)
- Clock based operation slows down the multiplication since we are effectively adding once per clock cycle.



Conclusion

□ Summary

- ➔ Algorithms for multiplying unsigned numbers
(Evolution of optimization, complexity)
- ➔ Booth's algorithm for signed number multiplication
(Different approach to multiplying, 2-bit based operation selection)
- ➔ Multiple hardware design for integer multiplier
(Hardware cost-driven optimization, fast multiplication)

□ Next Lecture

- ➔ Algorithms for dividing unsigned numbers
- ➔ Handling of sign while performing a division
- ➔ Hardware design for integer division

Read section 3.3 in 5th Ed., or section 3.3 in 4th Ed. of the textbook