

CMPE 212

Principles of Digital Design

Lecture 17

Programmable Logic Devices

March 28, 2016

www.csee.umbc.edu/~younis/CMPE212/CMPE212.htm



Lecture's Overview

□ Previous Lecture:

- ➔ Modular Combinational Logic
- ➔ Examples of medium scale integration components
(Multiplexers, Decoders, Encoders, etc.)
- ➔ Designing with digital components
(Tree-type arrangements, implementing switching functions)
- ➔ Binary ripple-carry adders

□ This Lecture

- ➔ Programmable logic devices
- ➔ Logic using Diode Biasing
- ➔ Programmable devices and how to configure them
- ➔ PLA, PAL, ROM and FPGA devices



Design Options

- Custom Integrated Circuits: Design and realize using a library modules on a single integrated circuit
 - Complete control over all circuit parameters (increases speed, reduces size and power consumption)
 - Most expensive and slowest to design and manufacture
- Semi-custom ICs: Use some pre-designed components, e.g.,
 - *Standard Cell libraries*
 - Use pre-designed units, just place and interconnect
 - All processing steps need to be done (same as fully costumed design)
 - *Generic gate arrays*
 - Integrated circuits with many unconnected gates
 - Flexible interconnections to enable implementation
 - Large volume enables commodity pricing and off-the-shelf availability
 - Examples are programmable logic arrays (PLA), programmable logic devices (PLD), and field programmable gate arrays (FPGAs)

Programmable Logic Array


- ❑ A PLA is a customizable AND matrix followed by a customizable OR matrix.
- ❑ Every intersection has a switch that controls the connection

Black box view of PLA

  

Implementation of Majority Function Using PLA

 
Dots reflects that the vertical line is an input to the AND gate or the horizontal line is an input to the OR gate



PLA Realization of Full Adder


$$CarryOut = (b.CarryIn) + (a.CarryIn) + (a.b)$$
 
$$Sum = (a.\bar{b}.\overline{CarryIn}) + (\bar{a}.b.\overline{CarryIn}) + (\bar{a}.\bar{b}.CarryIn) + (a.b.CarryIn)$$









Programmable Logic Devices (PLD)





- ❑ PLD are built to enable different functional configurations using conductor diodes, transistor switches or similar elements
- ❑ Diodes can be used for implementing gates:
 - When voltage source is connected to the anode of a diode, it becomes forward-biased and acts as a short circuits
 - When the cathode is attached to the voltage source the diode becomes a large resistive element (reverse-biased) and acts as an open circuit 0
- ❑ When the PLD are programmed in the field, rather than at manufacturing facilities, they called field programmable
- ❑ Fuses are used to enable the programmability in the field (to connect internal blocks)
- ❑ Focus on AND-OR devices (NAND-NOR devices are popular)

 

Logic using Diode Biasing

      




AND using Diodes

    


OR using Diodes

Key point:

   
Biasing and arranging the diodes enable implementation of gates, interconnecting them and connecting them to inputs lines



Diode-based Logic Circuit

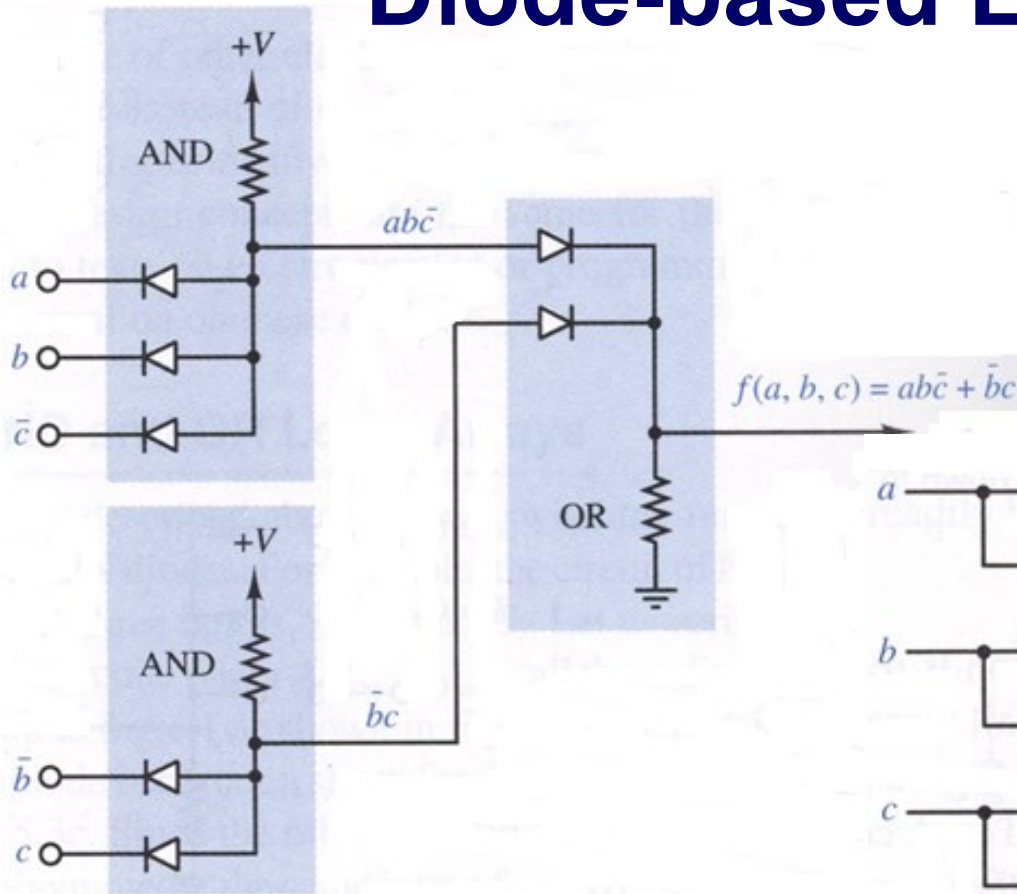

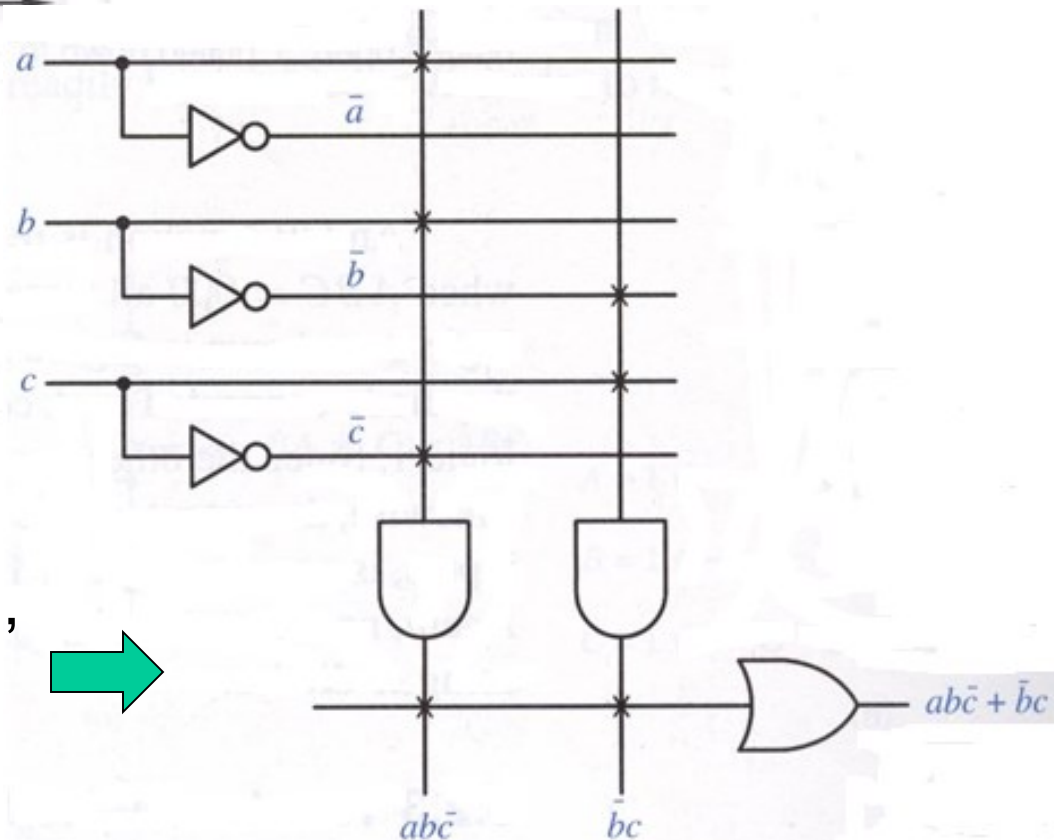
Sum of product implementation realized with AND-OR arrays



Compact form representation, where the mark X indicates presence of a diode

Field Programmable Logic Circuit

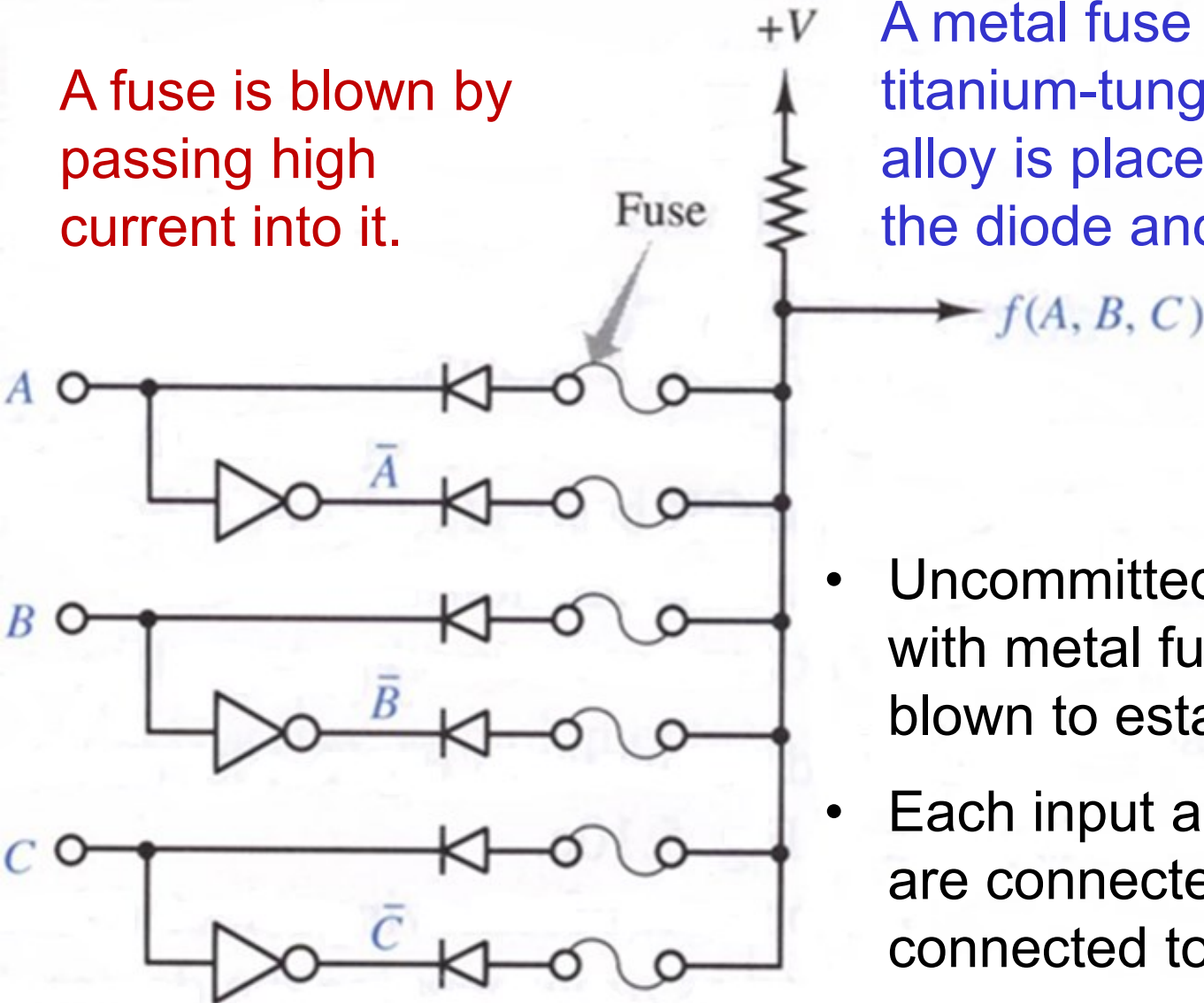
A fuse is blown by passing high current into it.




A metal fuse (nickel-chromium, titanium-tungsten, or similar alloy) is placed in series between the diode and the output line

- Uncommitted AND/OR arrays with metal fuses that can be blown to establish connectivity
- Each input and its complement are connected and fuses are connected to the output


Example: Field Programmable Circuit

 



Input-Output Port Options

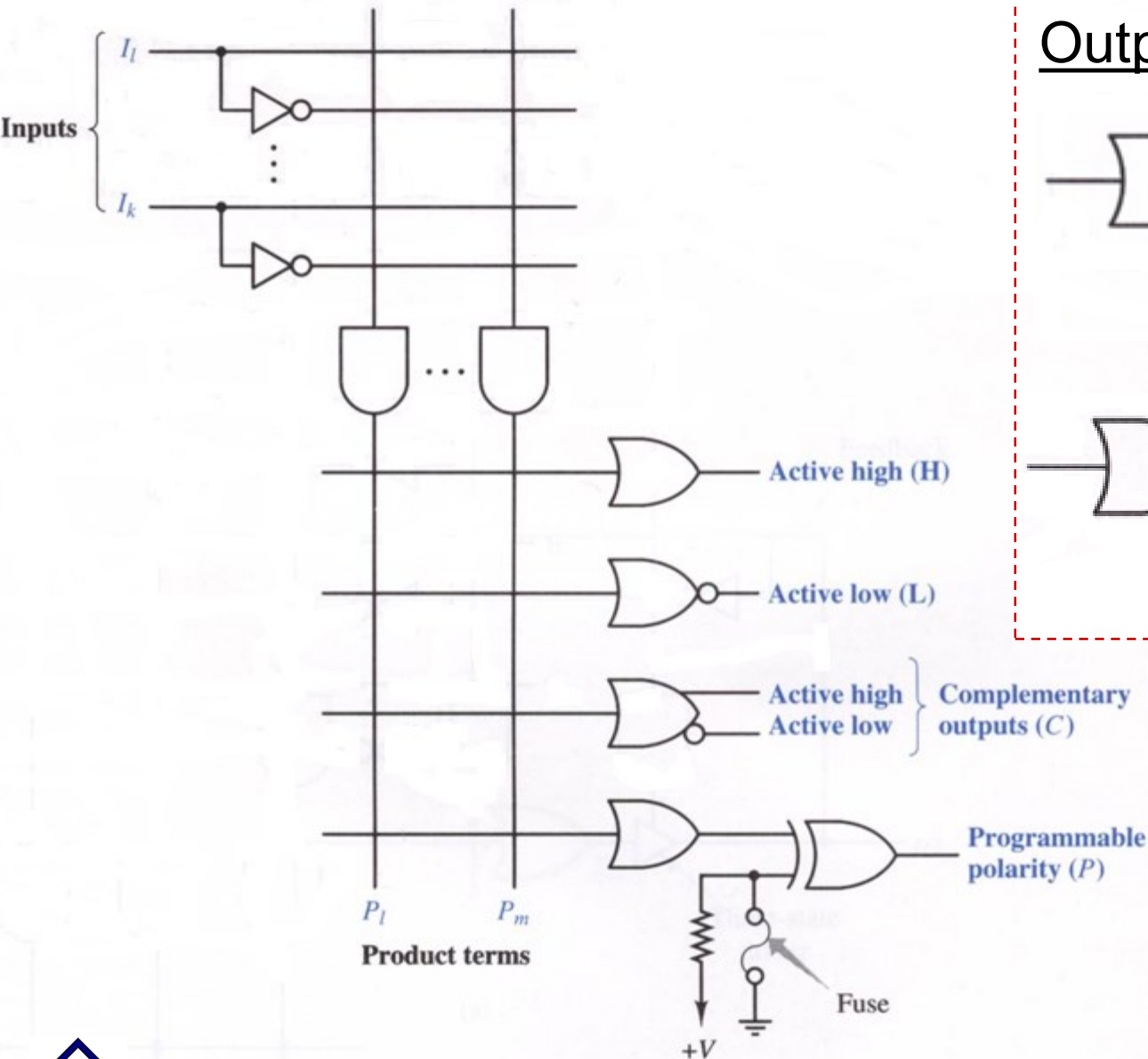


Output polarity

 

Bidirectional Port Option

 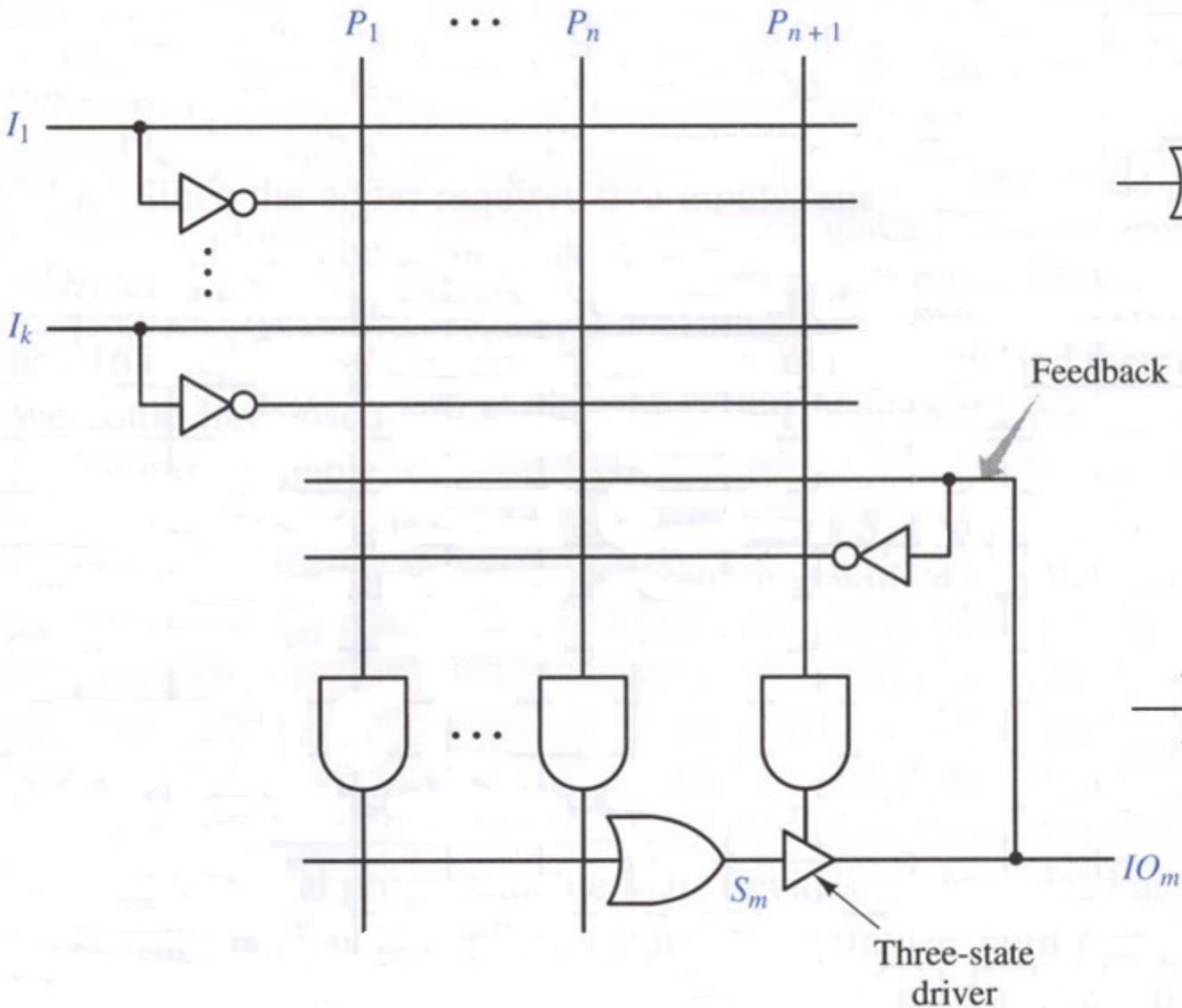

Tristate driver
disabled ($P_{n+1} = 0$)

 


Tristate driver
enabled ($P_{n+1} = 1$)


Bidirectional Pins

Tristate driver configuration:

 - Tristate driver enabled: S_m is available as output and is also fed back to be used as an intermediate input to the gate array
- Tristate driver disabled: IO_m becomes an external input port to the array




Tristate driver disabled

 


Tristate driver enabled

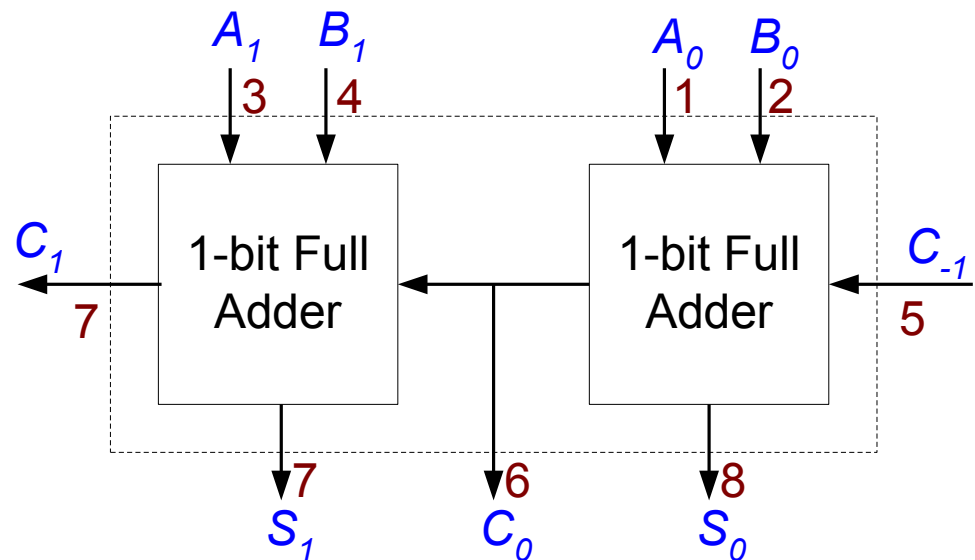Example: Implementing of a 2-bit ripple-carry adder using PLA

- C_{-1} is considered an external input to the array (control line for subtract/add)
- C_1 is the carry-out of the ripple adder, i.e., an output from the array.
- C_0 is an intermediate carry (to be fed back to array)




Example: Two-bit ripple carry adder

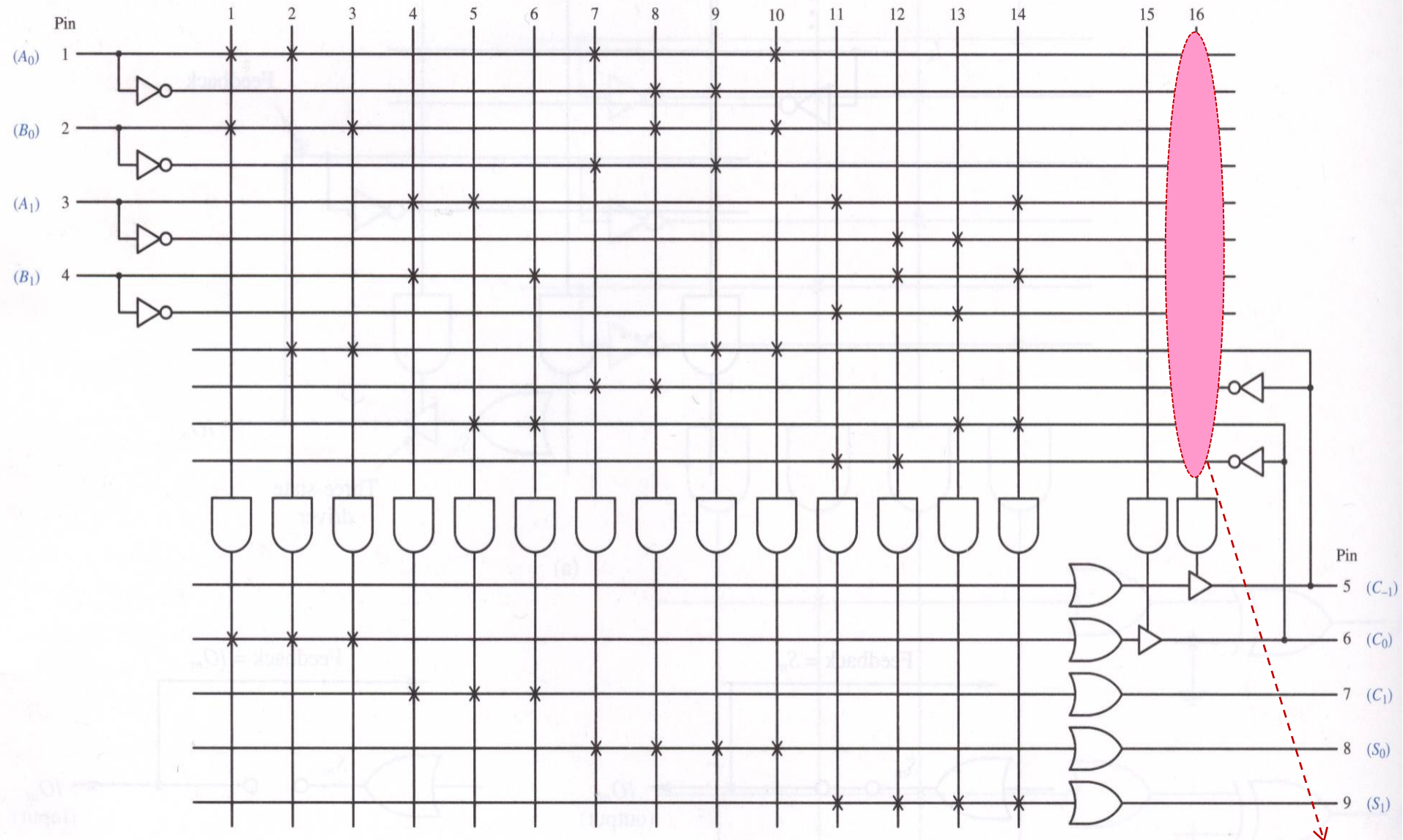


Pin₁₆ connected to inputs & their complements to prevent feeding back C_{-1}


Classifying Three Basic PLDs

 

(Programmable) Read-Only Memory (ROM)

 

Programmable Logic Array (PLA)

 



Programmable Array Logic (PAL) Devices

Example Commercial PLDs

Device	Description	Inputs	Product Terms	Outputs	Output Polarity
PLS100	PLA	16	48	8	Programmable
PLS153	PLA	16	42	10	Programmable
82S123	PROM	5	32	8	Active high
82S129	PROM	8	256	4	Active high
82S131	PROM	9	512	4	Active high
82S135	PROM	8	256	8	Active high
82S137	PROM	10	1024	4	Active high
82S147	PROM	9	512	8	Active high
82S181	PROM	10	1024	8	Active high
82S185	PROM	11	2048	4	Active high
82S191	PROM	11	2048	8	Active high
82S321	PROM	12	4096	8	Active high
PAL16L8	PAL	16	8	8	Active low
PAL14H4	PAL	14	4	4	Active high
PAL16C1	PAL	16	16	1	Complementary
PAL18P8	PAL	18	8	8	Programmable

Read Only Memory (ROM)

  - Configure for “Permanent” storage of binary information
- Non-volatile: Power off does not erase stored information




Fuse can be implemented as a diode or a transistor

Example: Programming 32x8 ROM



A4	A3	A2	A1	A0	D7	D6	D5	D4	D3	D2	D1	D0
0	0	0	0	0	1	1	0	0	0	1	0	1
0	0	0	0	1	1	0	0	0	1	0	1	1
0	0	0	1	0	1	0	1	1	0	0	0	0
...
1	1	1	0	1	0	0	0	1	0	0	0	0
1	1	1	1	0	0	1	0	1	0	1	1	0
1	1	1	1	1	1	1	1	0	0	0	0	0

Start with truth table →

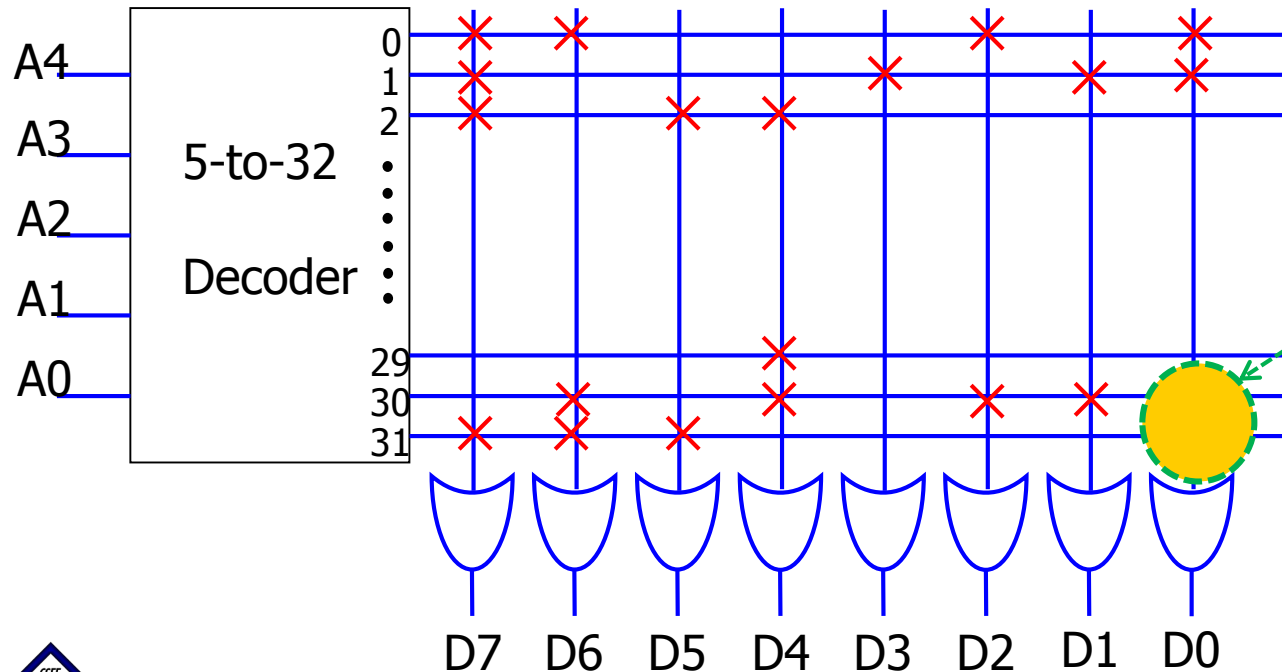


For every minterm make a connection for all corresponding output OR gates


Example: Lookup Table using ROM

- A square lookup table for $F(X) = X^2$ using ROM

X	$F(X)=X^2$
0	0
1	1
2	4
3	9
4	16
5	25
6	36
7	49

 


X	$F(X)=X^2$
000	000000
001	000001
010	000100
011	001001
100	010000
101	011001
110	100100
111	110001

 


Example: Lookup Table using ROM

- A square lookup table for $F(X) = X^2$ using ROM


X	$F(X)=X^2$
0	0
1	1
2	4
3	9
4	16
5	25
6	36
7	49

 


X	$F(X)=X^2$
000	000000
001	000001
010	000100
011	001001
100	010000
101	011001
110	100100
111	110001

 


Programmable Logic Array (PLA)

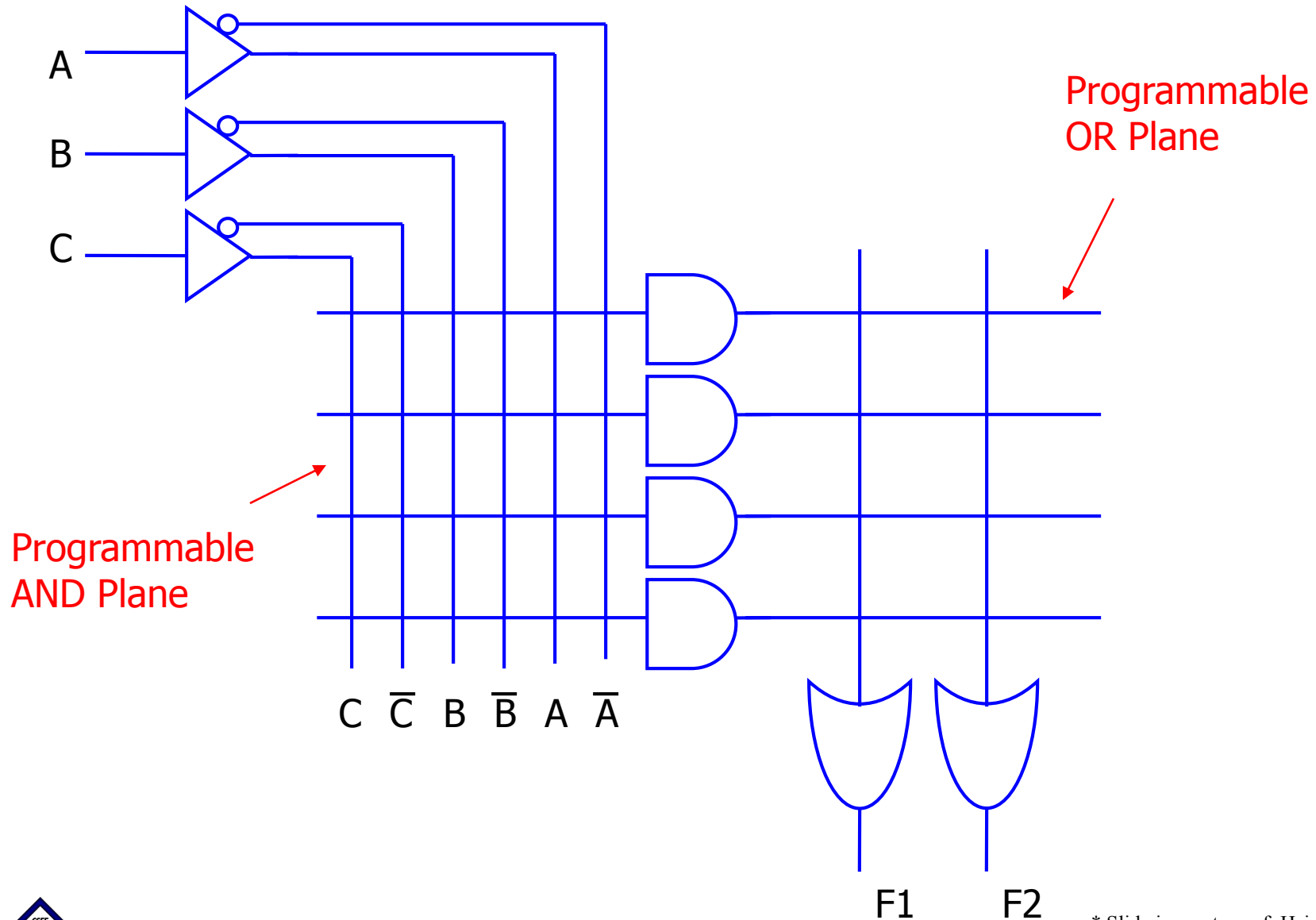


Example of Using PLA

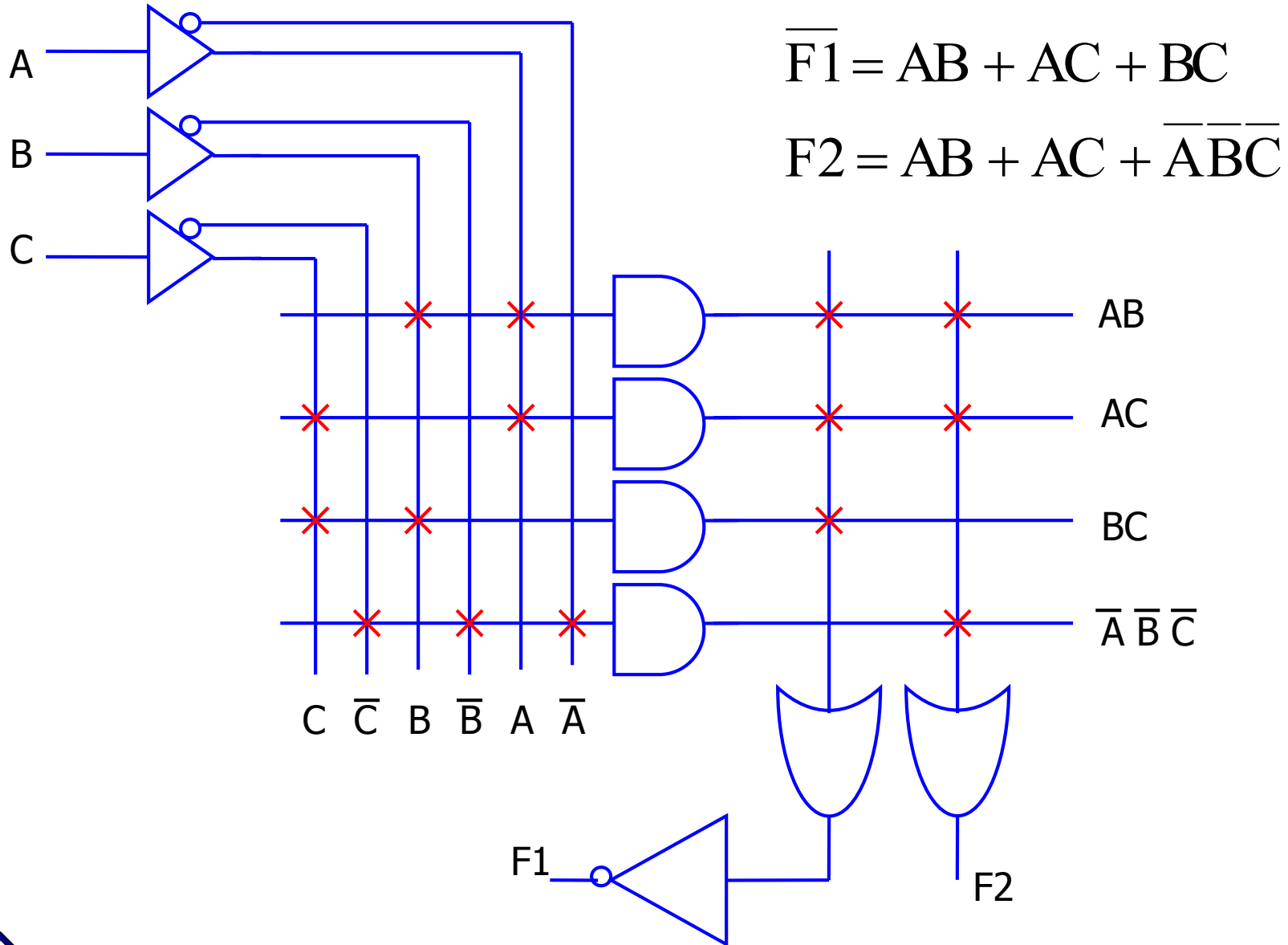

PAL Devices

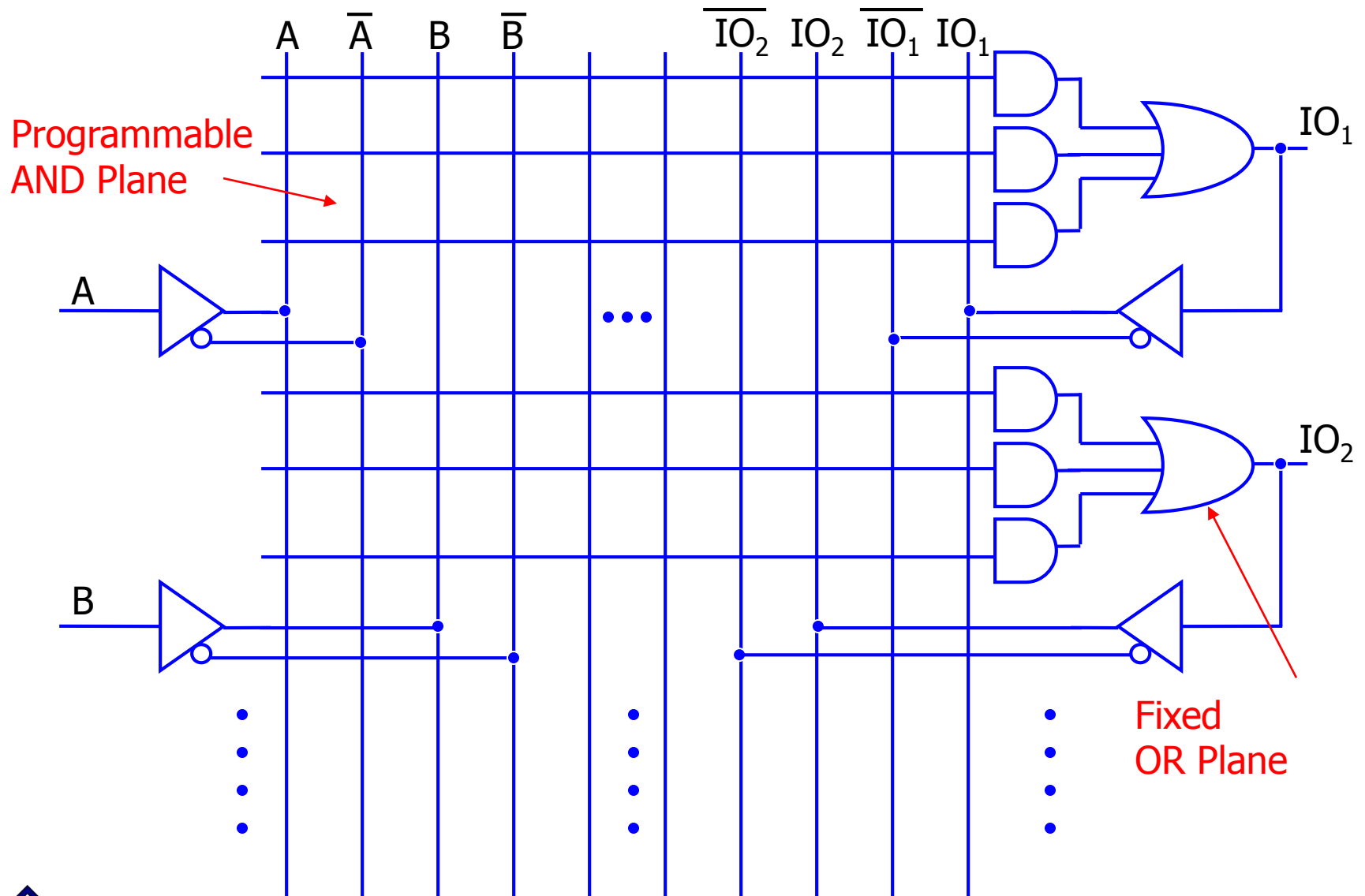


Example: PAL Device Design

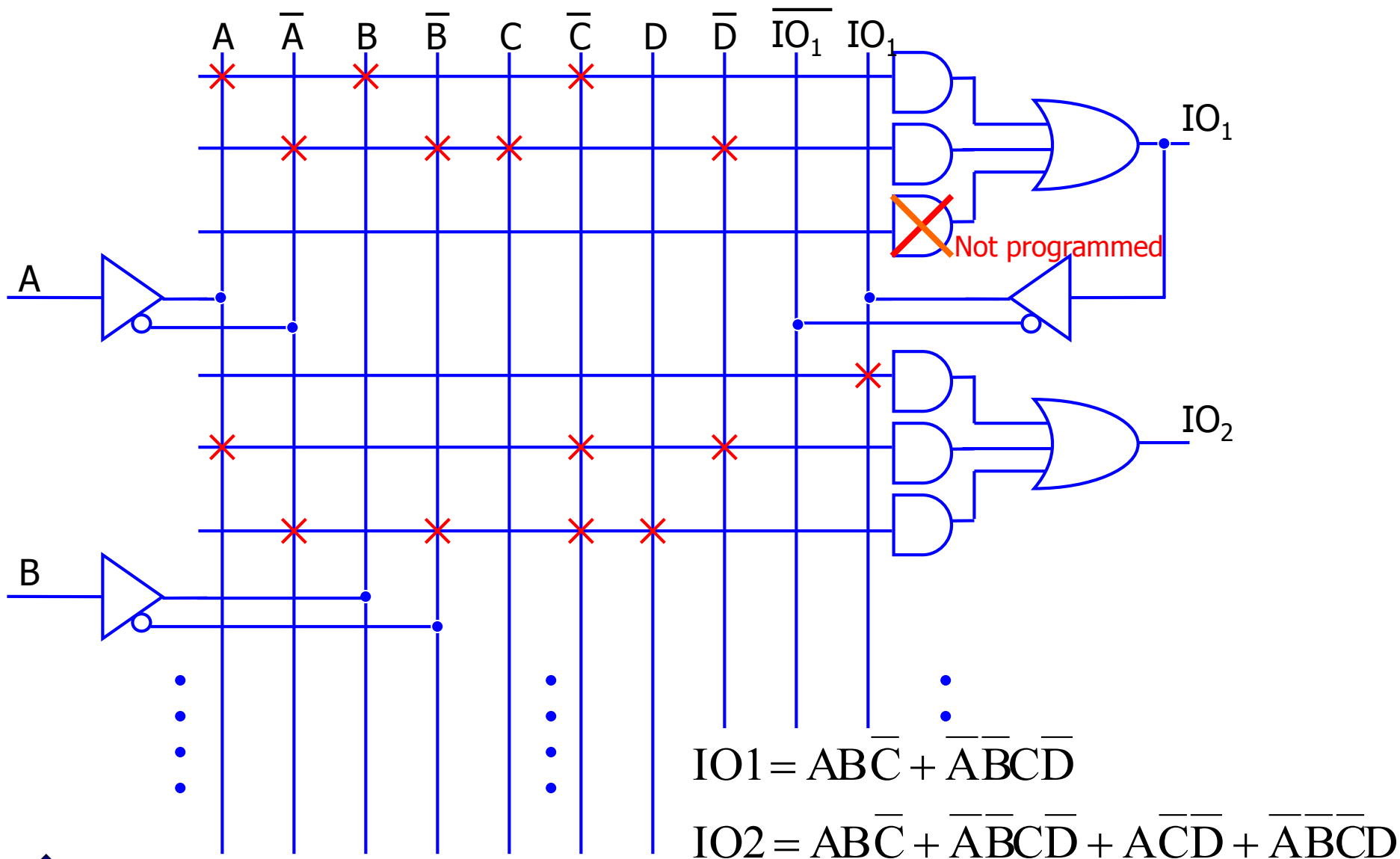


* Slide is courtesy of Hsien-Hsin Sean Lee

Complex Programmable Logic Devices

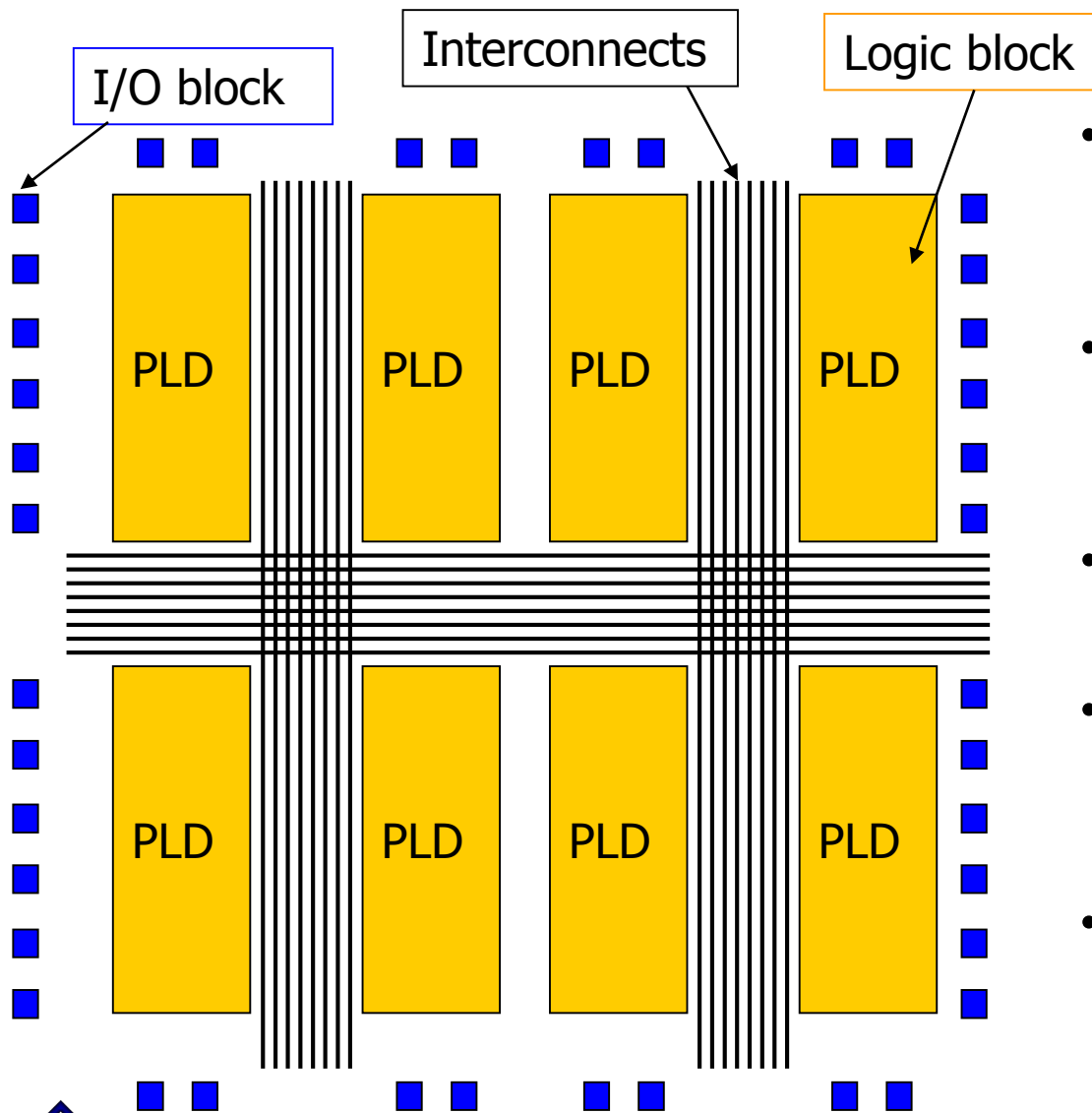

- Multiple PLDs (e.g. PALs, PLAs) with programmable interconnection structure
- Complex Programmable Logic Devices (CPLD) are very popular nowadays
- Pioneered by Altera (a major player in the market)
- Consists of logic, IO, and interconnects blocks (all programmable)
- CPLD offers logic resources with a wide number of inputs (AND planes)

Field-Programmable Gate Array (FPGA)

 

- High logic capacity with large distributed interconnection structure
- Logic capacity \approx number of 2-input NAND gates
- Offers more narrow logic resources
- Offer a higher ratio of Flip-flops to logic resources than CPLD
- SRAM-controlled switches (e.g., Pass transistors)
- HCPLD (High Capacity PLD) is often used to refer to both CPLD and FPGA

Conclusion

□ Summary

- ➔ Programmable logic devices
(Concept of logic matrix, example applications)
- ➔ Logic using Diode Biasing
(AND-OR circuits using diodes settings)
- ➔ Programmable devices and how to configure them
(fuse management, port configurations and applications)
- ➔ PLA, PAL, ROM and FPGA devices
(architectures, key features, examples)

□ Next Lecture

- ➔ Introduction to sequential circuits
- ➔ Memory devices

Reading assignment: Sections 5.1 – 5.5 in the textbook