

CMPE 314: Principles of Electronic Circuits

Dr. Yan

Lab 04 Report

Transistor Characteristics

Sabbir Ahmed

Yu Fu

1. Objective

Construct a transistor circuit and measure basic transistor characteristics.

2. Equipment

- Resistors; $1 \times 2.2 \text{ k}\Omega$, $1 \times 220 \text{ k}\Omega$
- Transistor; $1 \times 2\text{N}3904$ NPN
- DC power supply, digital multi-meter(s), breadboard

3. Background

A bipolar junction transistor (BJT) is a three-terminal electronic device constructed of doped semiconductor material and may be used in amplifying or switching applications. The BJT consists of two very closely spaced PN-junctions (diodes) - the base-emitter junction and the base-collector junction. Under typical operating conditions (forward active mode), the base-emitter junction is forward biased while the base-collector junction is reverse biased. A BJT in the forward active mode can be thought of as a current controlled current source.

4. Procedures

4.1 Part A. Forward Active Mode I-V Characteristics

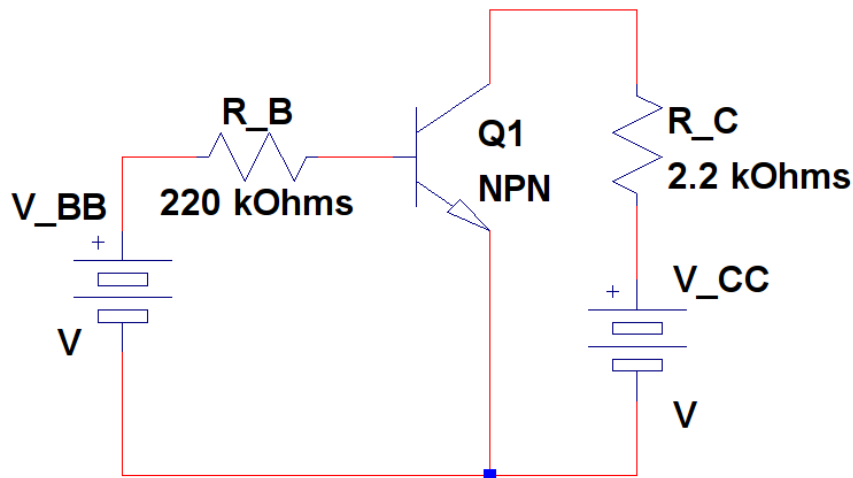


Figure 1: Common Emitter Circuit with an NPN Transistor

- Use the NPN transistor to construct the circuit from Figure 1.
- Increase the DC voltage V_{BB} from 0 V to 3 V with step of 0.5 V. For each V_{BB} step, increase V_{CC} from 0 V to 10 V with step of 0.25 V for $V_{CC} \leq 2 \text{ V}$ and with step of 1 V for $V_{BB} > 2 \text{ V}$. Record the corresponding voltage V_{CE} and V_{BE} for each VCC input. Calculate corresponding I_B and I_C .
- Plot all the I_C vs V_{CE} curves for a given I_B on the same plot, which is called collector characteristic curves. Find the DC forward current gain β_F .

4.2 Part B. DC Analysis

- Set $V_{CC} = 10\text{ V}$, and vary V_{BB} from 1 V to 4 V, with step of 0.5 V. Measure I_C and V_{CE} .
- Plot the I_C vs V_{CE} loadline on the same plot with the I-V characteristics curves got in Part (A). Plot the theoretical I_C vs V_{CE} loadline on the same plot. Identify the cutoff, saturation, and forward active regions on the plots.

4.3 Part C. PSPICE Simulation

- Use PSPICE to simulate Part (A) and Part (B).

5. Results

The circuit from Figure 1 was constructed and the outputs V_{BB} and V_{CC} were recorded. I_C was computed with the relationship $I_C = \frac{V_{CC} - V_{CE}}{R_C}$ and I_B through $I_B = \frac{V_{BB}}{R_B}$. The DC current gain β_F was computed by taking the ratio of the average of I_C to the average of I_B , $\beta_F = \frac{I_C}{I_B}$, which yielded $\beta_F = \frac{8.37 \times 10^{-3}}{6.82 \times 10^{-6}} = 122.70$ as the gain.

The V_{CE} was plotted against I_C , along with the cutoff, saturation and forward active regions indicated as shown below:

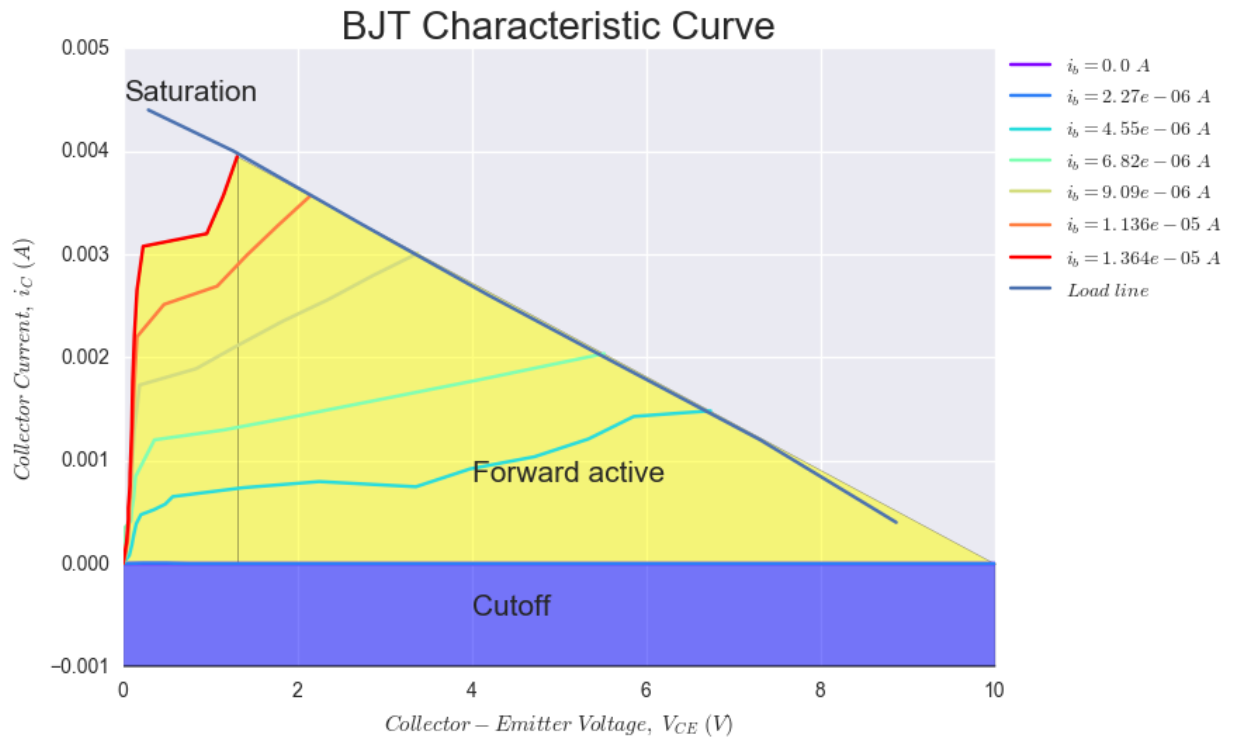


Figure 2: I-V Characteristic Curves of the Transistor Used in the Circuit Constructed from Figure 1

The transistor circuit was constructed on PSPICE, and the outputs V_{CE} and I_C were dumped and plotted to create the following transistor characteristics curve plot.

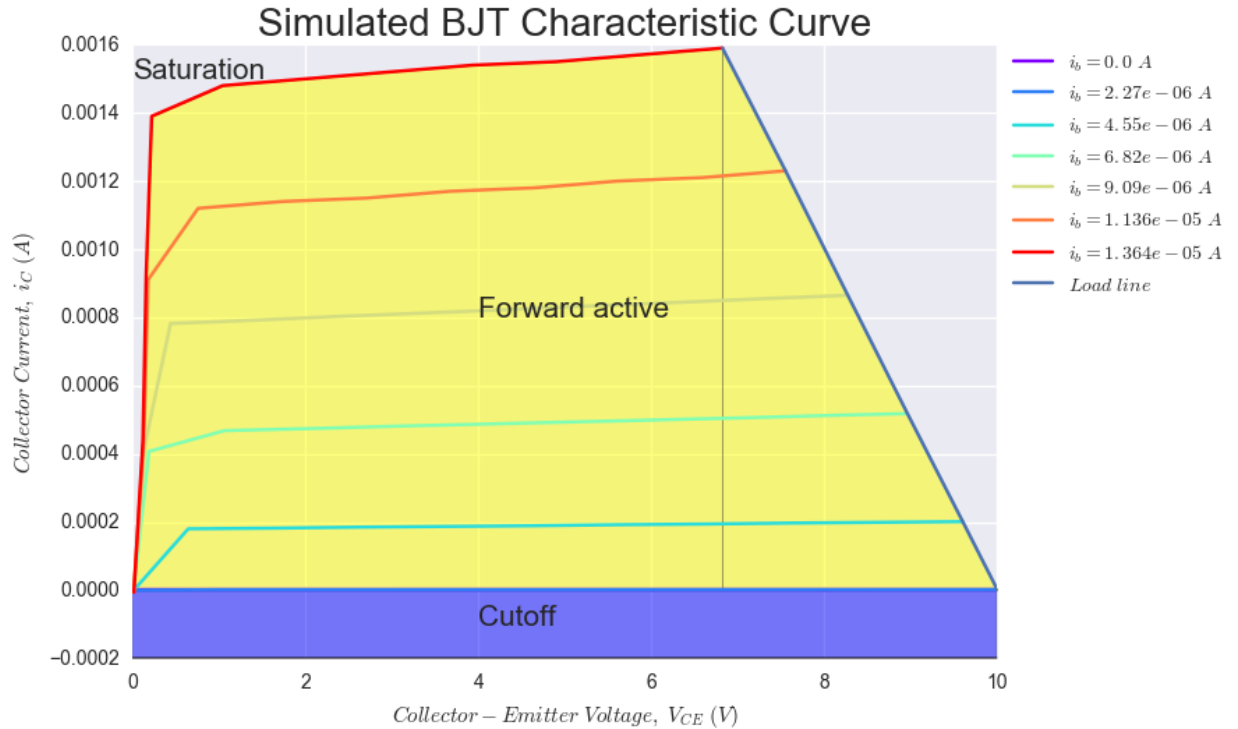


Figure 3: I-V Characteristic Curves of the Transistor Simulated on PSPICE

6. Conclusion

The I-V characteristics curves plotted from the experiment have a large error from the one plotted from the simulated circuit on PSPICE. The I_C of the curves from the measured data appear to be significantly larger than the simulated plot, and the V_{CE} seem to starting losing its data points after V_{CC} exceeds a certain threshold. The discrepancy of the plots might have been caused from inaccurate measurements of the very sensitive components used in the construction of the circuit.