



## CMPE 212L, Principles of Digital Design Laboratory

### Experiment #5

Friday 2/26/2016

### Objective

The main objective in this lab is to practice the implementation of a switching function and compare the complexity and timing to an optimized version.

### Required Equipment

- 7400: includes four 2-input NAND gates.
- 7403: includes four 2-input NAND gates.
- 7402: includes four 2-input NOR gates.
- 7408: includes four 2-input AND gates.
- 7404: Hex inverter gates.
- 7486: Quad 2- input exclusive OR.
- 74136: Quad 2- input exclusive OR.
- (10K ohms, 330 ohms) resistors, breadboard, power supply, multi-meter, LED.

### Experiments:

1. Implement the function  $\bar{f}(a,b,c) = (b \oplus \bar{c}) + \overline{ab\bar{a} + c}$ .
2. Draw the function's truth table and test your implementation's functionality.
3. Simplify the function and implement the simplified version as well.
4. Measure and compare input-output delay time in both implementations.
5. Bonus: compare the power consumption and number of transistors needed for both implementation.

Figure 2 - 7486

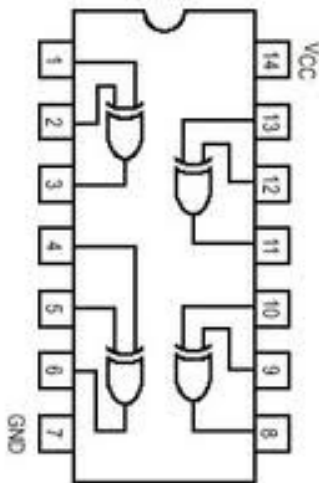


Figure 1 - 7408

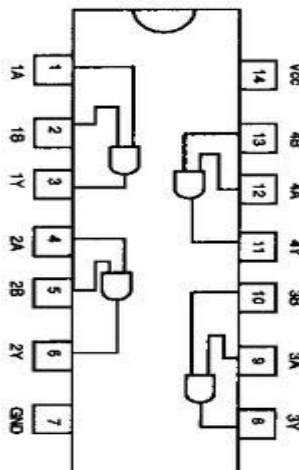


Figure 3 - 7404

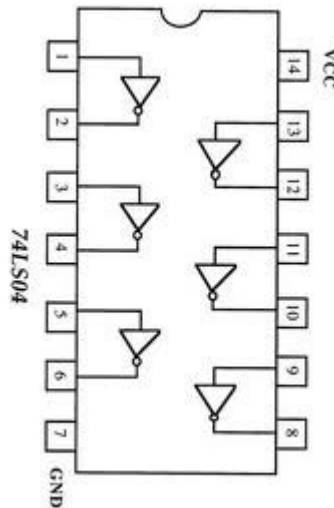


Figure 4 - 7402

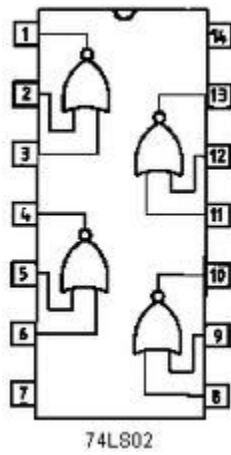


Figure 6 - 7403

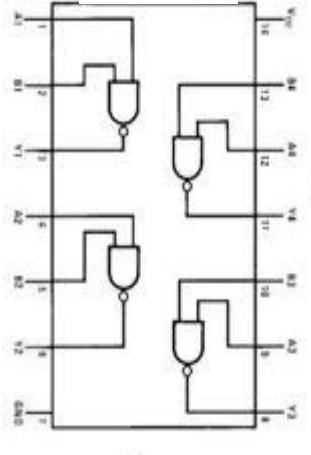


Figure 5 - 7400

