

# CMPE 212

## Principles of Digital Design

### Lecture 24

## Analysis of Sequential Circuits

April 20, 2016

[www.csee.umbc.edu/~younis/CMPE212/CMPE212.htm](http://www.csee.umbc.edu/~younis/CMPE212/CMPE212.htm)



# Lecture's Overview


## □ Previous Lecture

- ➔ Modulo-N Counters
- ➔ Synchronous and asynchronous BCD counters
- ➔ Counter resetting
- ➔ Shift register as a counter
- ➔ Multiple sequence counters
- ➔ Fractional rate multipliers

## □ This Lecture

- ➔ Synchronous sequential circuits models
- ➔ Describing the behavior of sequential circuits
- ➔ Sequential circuits analysis

# Sequential Circuit Model

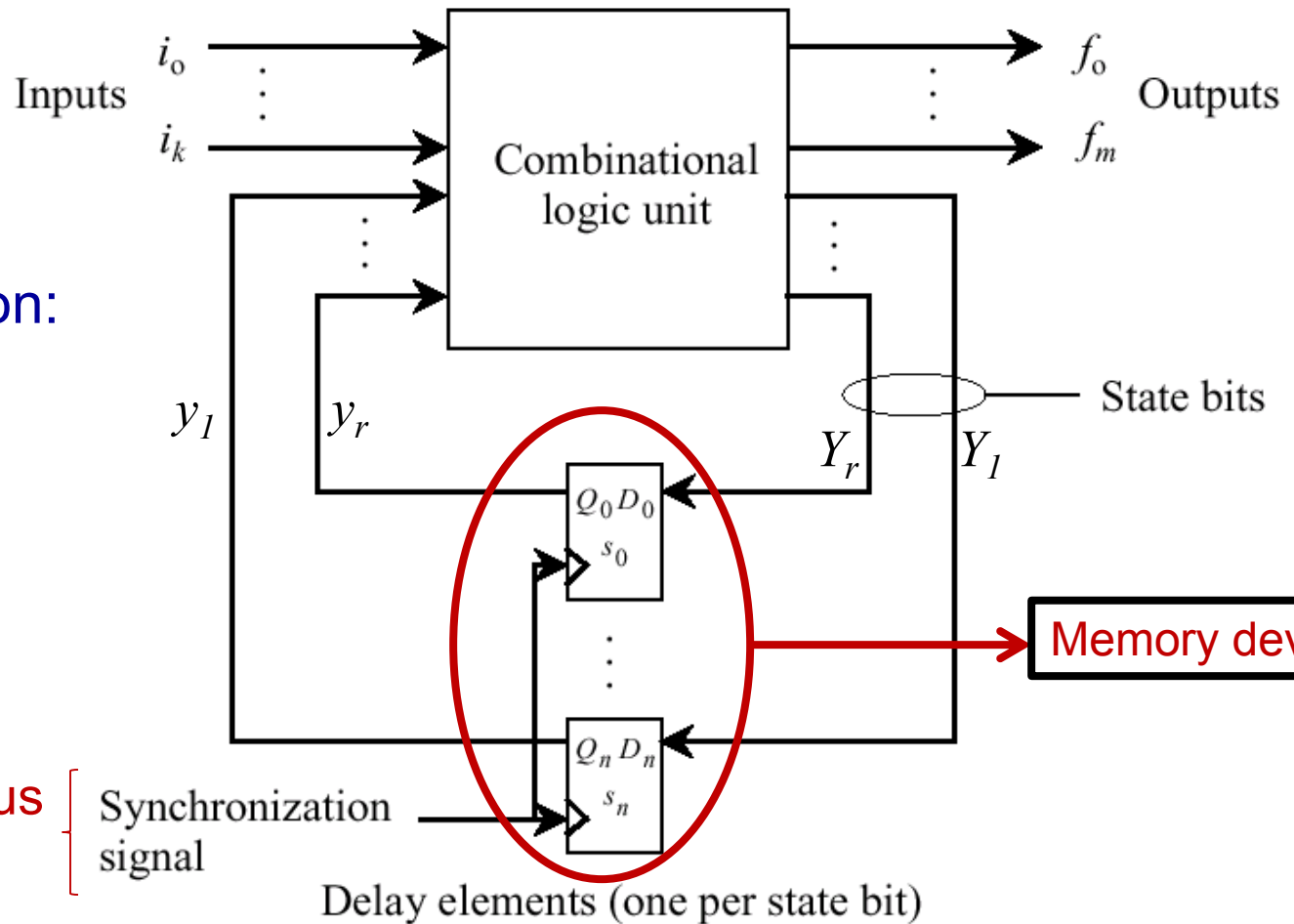

Possible realization:

1. Mealy model
2. Moore model

Can be synchronous  
or asynchronous


Synchronization  
signal

- ❑ Composed of a combinational logic unit and delay elements in a feedback path, which maintains state information
- ❑ Defined by output relation to input and circuit state (values in flip-flops)



 
# Example: FSM for Modulo-4 Counter

- ❑ Finite state machines use flip flops and combinational logic to implement the desired function
- ❑ A counter is a sequential circuit that tracks the number of ones or zeros in an input or the number of clock cycles
- ❑ A modulo-4 counter has two output lines, which take on values of 00, 01, 10, and 11 on subsequent clock cycles



# Mealy Model

 


- ❑ Categorized by having the outputs to be a function of state bits and inputs

Present state	Input x	
	0	1
A	B/1	C/0
B	B/0	A/1
C	A/0	C/0


Next state/output

Time:	0	1	2	3	4	5
Present state:	A	B	A	C	A	C
Input:	0	1	1	0	1	0
Output:	1	1	0	0	0	0
Next state:	B	A	C	A	C	A

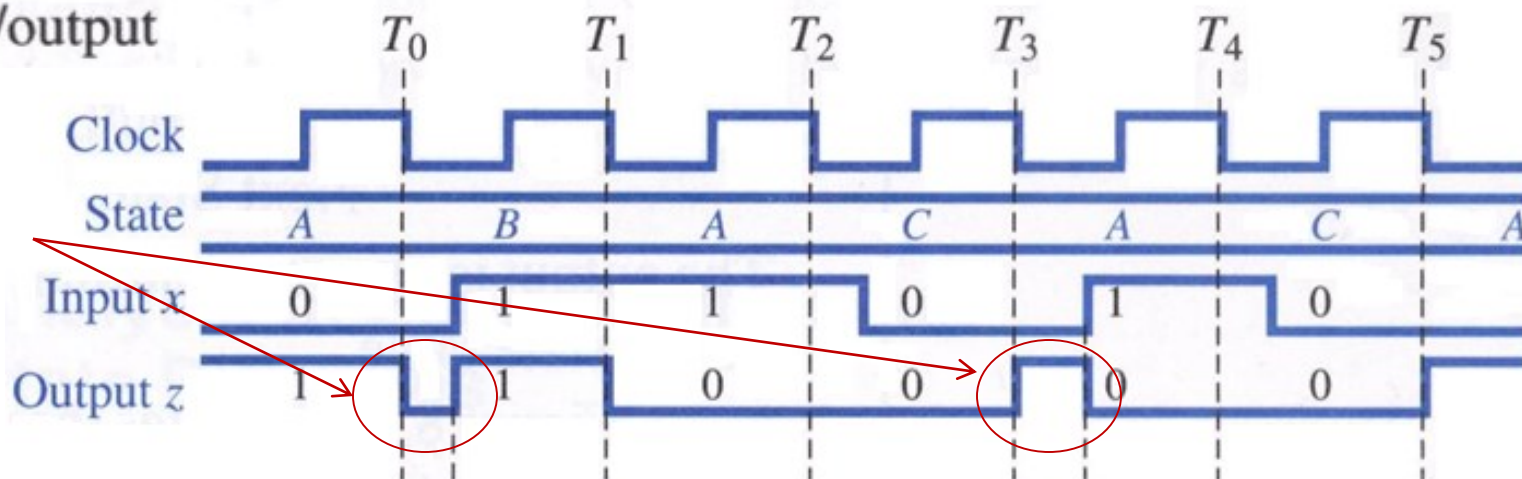o/p depends on i/p and thus should be checked at the right time




# Moore Model

 

- ❑ Outputs is a function of ONLY the state bits
- ❑ Less design flexibility and more states (flip-flops), yet more stable output than Mealy model)


Present state	Input x		Outputs
	0	1	
W	Y	X	0
X	X	Y	1
Y	X	W	0

Time:	0	1	2	3	4	5
Present state:	W	Y	W	X	X	Y
Input:	0	1	1	0	1	0
Output:	0	0	0	1	1	0
Next State:	Y	W	X	X	Y	X

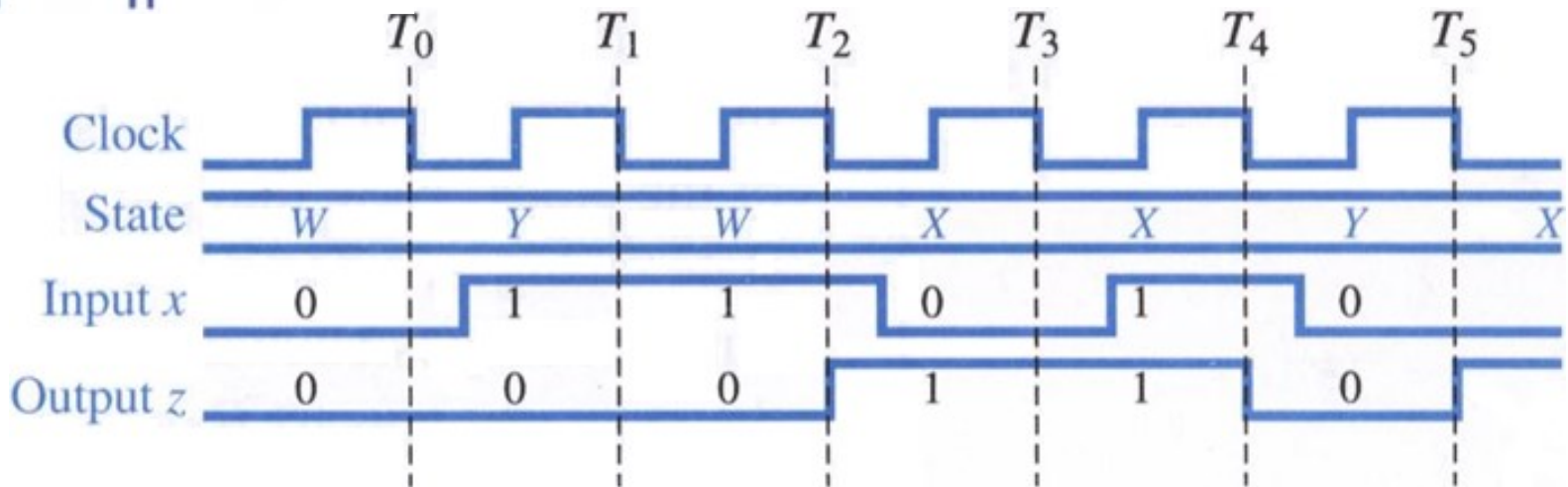


Output is synchronized with the state transition

# Analyzing Sequential Circuits

 

 
- Available: sequential circuit schematic
- Determine the circuit response to an input sequence (using relation between inputs, state variables, and outputs)
- Type: Mealy or Moore sequential circuit?



**Problem:** Given a circuit determine the state diagram





# Timing Behavior Analysis

 

$$z = xy$$

$$Y = x\bar{y} + \bar{x}y = x \oplus y$$

$x=01101000$

  

Transient change in the output (byproduct of Mealy design)



# Deriving State Diagram

- There is only 1 flip-flop  $\rightarrow$  there is only 2 states ( $0 \equiv A$ ;  $1 \equiv B$ )
- Notation:  $y^k$  represents  $y(k \Delta t)$ ,  $k = \text{integer}$ ;  $\Delta t = \text{clock period}$

		Input $x^k$	
		0	1
Present state $y^k$	0		
	1		

		Input $x^k$	
		0	1
Present state $y^k$	0	0/0	1/0
	1	1/0	0/1

Next state/output

		Input $x^k$	
		0	1
Present state	A	A/0	B/0
	B	B/0	A/1


Next state/output

Reflects  $Y^k = y^{k+1}$   
and  $z^k$

$$z^k = x^k y^k$$

Populated using


$$Y^k = x^k \oplus y^k = y^{k+1}$$

 

# Analysis Procedure

- 1) If a state table or diagram is given, proceed to steps 6 and 7, otherwise use combinational logic analysis to derive the flip-flop input and circuit output equations
- 2) Construct the k-maps for all logic equations from step 1
- 3) Combine the k-maps for all flip-flops inputs into a single map
- 4) Using the characteristic equations of the flip-flops, construct a next-state map
- 5) Combine the next-state and output maps into a single map to construct a binary state table
- 6) Form a binary state diagram from the binary state table, if desired.
- 7) Draw a timing diagram showing the clock, the given input sequence and the starting state
- 8) On the timing diagram, derive the waveforms for the flip-flop input(s) and state(s) for all remaining circuit input values
- 9) On the timing diagram derive the waveforms of the circuit output(s)

# Example

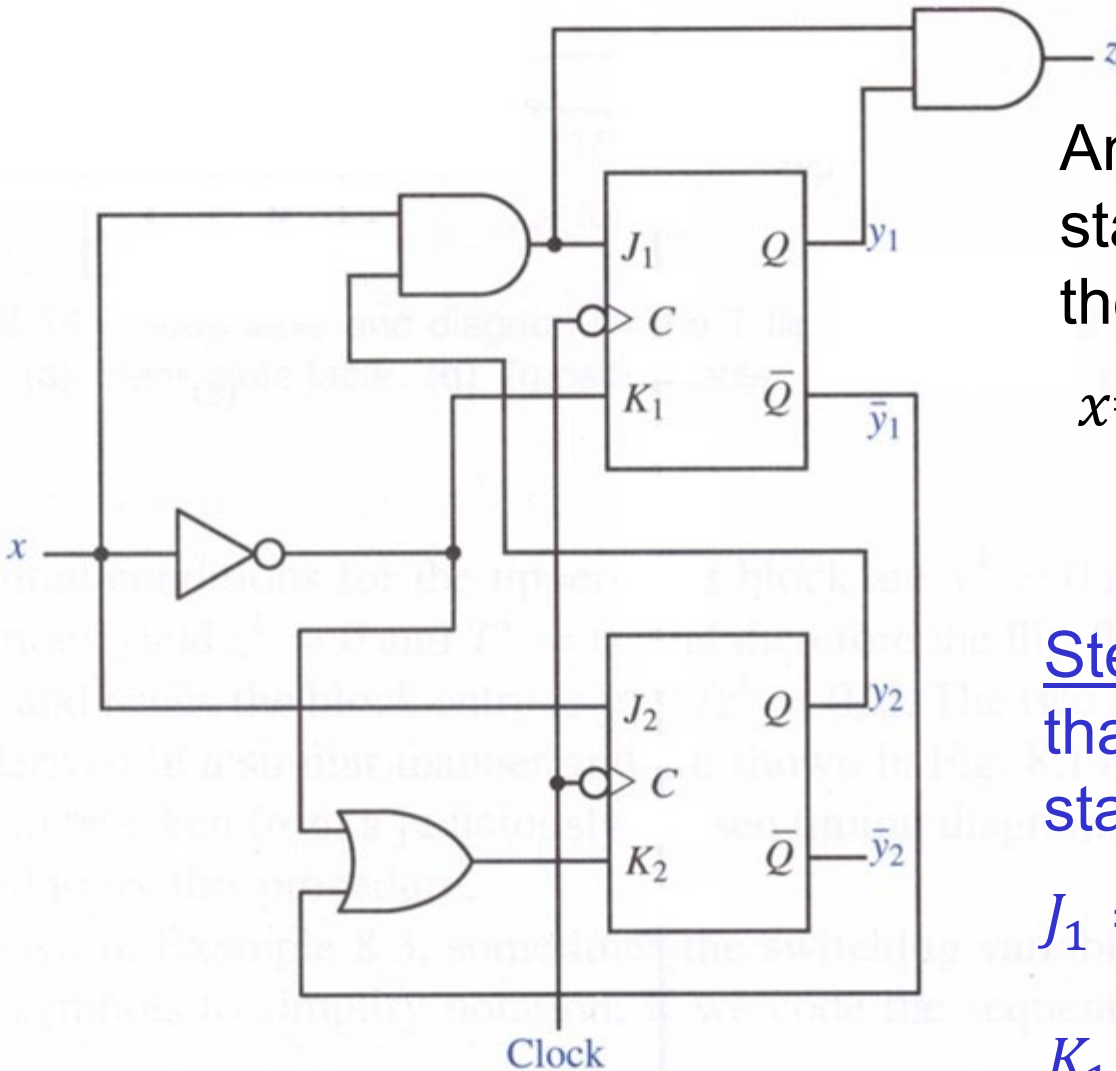

Analyze the circuit (show the state and timing diagram) for the input sequence:

$$x=0011110, \text{ and } y_1^0 y_2^0=10$$

Step 1: The logic equations that describe the input and state variables are:

$$J_1 = xy_2, \quad J_2 = x, \quad z = xy_1y_2,$$

$$K_1 = \bar{x}, \quad K_2 = \bar{x} + \overline{y_1}$$

Two flip-flops  $\rightarrow$  4 states  
sequential circuit

# Step 2: k-maps for i/p & state variables

$y_1 y_2$		$x$	
		0	1
00		0	0
01		0	1
11		0	1
10		0	0

$J_1$

$y_1 y_2$		$x$	
		0	1
00		1	0
01		1	0
11		1	0
10		1	0

$K_1$

$y_1 y_2$		$x$	
		0	1
00		0	1
01		0	1
11		0	1
10		0	1

$J_2$

$y_1 y_2$		$x$	
		0	1
00		1	1
01		1	1
11		1	0
10		1	0

$K_2$

$$J_1 = xy_2, \quad J_2 = x$$


$$K_1 = \bar{x}, \quad K_2 = \bar{x} + \bar{y}_1$$

$$z = xy_1y_2,$$


$y_1 y_2$		$x$	
		0	1
00		0	0
01		0	0
11		0	1
10		0	0

$z$

# Steps 3-5: Form Binary State Table

 

# Steps 7-9

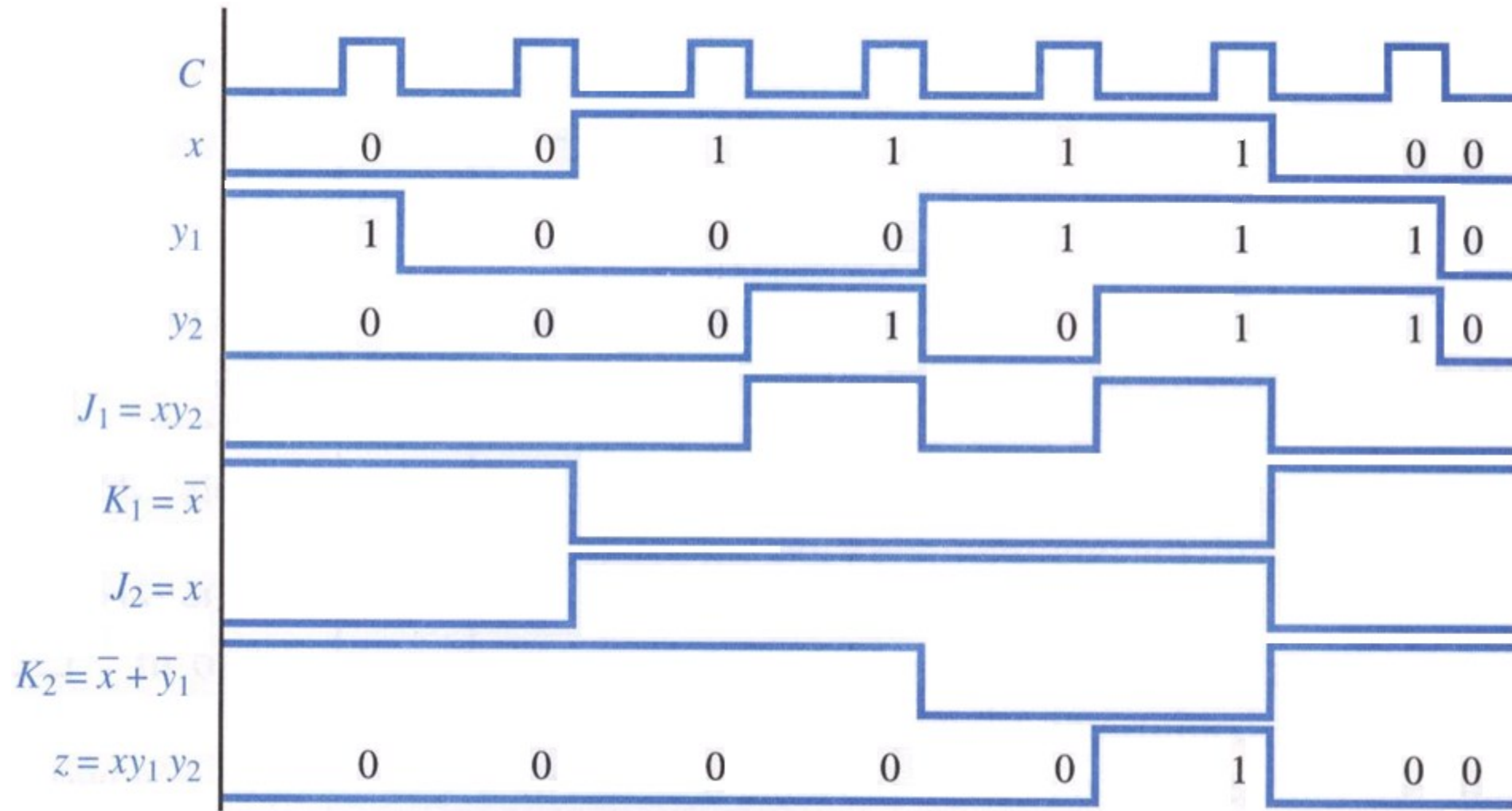



# Conclusion

## □ Summary

- ➔ What does analyzing sequential circuit mean?
- ➔ Mealy and Moore models
- ➔ Procedure for analyzing a sequential circuit
  1. Define relation between input and state variables and output
  2. Combine the logic equations (and k-map) to define state table
  3. Draw state diagram from state table
  4. Draw timing diagram to capture behavior

## □ Next Lecture

- ➔ Synthesis of synchronous sequential circuits

Reading assignment: Sections 8.1 – 8.2 in the textbook