



## CMPE 212, Digital Systems Design


### Assignment #4

Due: Mon 4/11/16 in the class
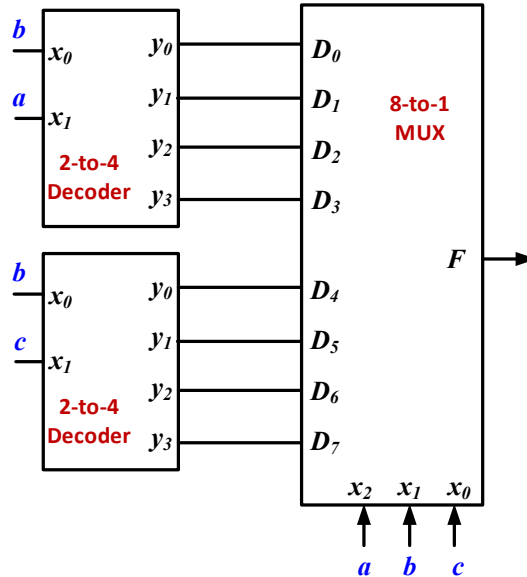
#### Question 1:

(15 Points)

Find the canonical SOP expression for the function  $F$  realized by the following circuit:



#### Question 2:

(15 Points)

Realize the following set of functions using only a single 74154 decoder module and logic gates:

$$f_1(A, B, C, D) = \sum m(2, 4, 10, 11, 12, 13)$$

$$f_2(A, B, C, D) = C(\bar{B} + A) + \bar{A}\bar{C}D$$

$$f_3(A, B, C, D) = \prod M(0, 1, 2, 3, 6, 7, 8, 9, 12, 14, 15)$$

#### Question 3:

(20 Points)

Design a 32-to-1 multiplexer using:

- Two 74150 modules, one inverter, and one NAND gate.
- Only 74151A modules. (Do not use any additional gates.)

#### Question 4:

(20 Points)

Design a subtraction module with 1-bit data  $A$  and  $B$ , and carry-in  $C_{in}$ . The module outputs the result  $S$ , and carry-out  $C_{out}$ .

- Use a 3-to-8 decoder and 2-input OR gates.
- Use two 4-1 multiplexer and one inverter.

#### Question 5:

(30 Points)

Design a BCD to excess-3 code converter using:

- PLA (Like Figure 5.7 in the textbook)
- ROM (Like Figure 5.25 in the textbook)