

CMPE 310 Systems Design and Programming

L6: Chapter 10 – Memory Interface

UMBC

AN HONORS UNIVERSITY IN MARYLAND

L6 Objectives

- * Explore Semiconductor memories
- * Three main characteristics of memory devices
- * Memory address decoding

Semiconductor memories

- * Almost all systems contain two basic types:

- * **ROM: Read-only memory**
- * **RAM: Read-Write memory**

- * Three Memory Characteristics:


- * **IC Memory/ Chip Capacity**
 - * No. of bits that a chip can store

- * **Memory Organization**

- * 2^x locations, x = no. of address pins
- * Each location contains y bits; y = no. of data pins
- * Chip contain $2^x \times y$ bits

- * **Speed**

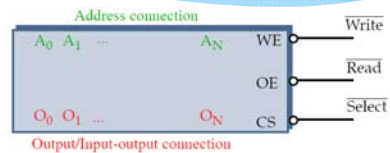- * Access time varies \rightarrow IC technology used



Example

- * If you have a memory chip with 12 address pins and 8 data pins:
 - * Memory organization
 - * Chip capacity
- * If you have a 512K chip with 8 data pins:
 - * Memory organization
 - * Number of address pins

Memory Interface

Memory Chips

- * The number of address pins is related to the number of **memory locations**.
 - * Common sizes today are **1K to 1G locations**.
 - * Therefore, between 10 and 30 address pins are present.
- * The data pins are typically **bi-directional in read-write memories**.
 - * The number of data pins is related to the **size of the memory location**.
 - * For example, an 8-bit wide (byte-wide) memory device has **8 data pins**.
 - * Catalog listing of **1K X 8** indicate a **byte addressable 8K bit memory with 10 address pins**.

Memory chips

Memory Chips


- * Each memory device has at least one **chip select (\overline{CS}) or chip enable (\overline{CE}) or select (\overline{S}) pin** that enables or select the memory device.
 - * This enables read and/or write operations.
 - * If more than one are present, then all must be 0 in order to perform a read or write.
- * Each memory device has at least one control pin.
 - * ROMs: an **output enable (\overline{OE}) or gate (\overline{G}) connection is present**.
 - * The OE pin enables and disables a set of tristate buffers located in the device and must be active to read data.
 - * RAMs: a **read-write (R/\overline{W}) or write enable (\overline{WE}) and read enable (\overline{OE}) are present**.
 - * For dual control pin devices, it must be hold true that both are not 0 at the same time to read or write data.

Memory Interface

Memory Chips

- * **ROM:**
 - * Non-volatile memory: Maintains its state when powered down.
 - * There are several forms:
 - * ROM: Factory programmed, cannot be changed. Older style.
 - * PROM: Programmable Read-Only Memory.
 - * Field programmable but only once. Older style.
 - * EPROM: Erasable Programmable Read-Only Memory.
 - * Reprogramming requires up to 20 minutes of high-intensity UV light exposure.
- * **Flash (EEPROM): Electrically Erasable Programmable ROM.**
 - * Also called **EAROM (Electrically Alterable ROM)** and **NOVRAM (Non-Volatile RAM)**.
 - * Writing is much slower than a normal RAM.
 - * Used to store setup information, e.g. video card on computer systems.
 - * Can be used to replace EPROM for BIOS ROM memory.


Intel 2716 EPROM

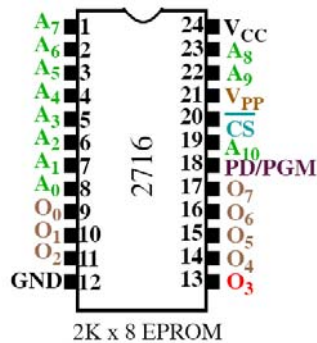

V_{pp} is used to program the device by applying 25V and pulsing PGM while holding CS high

Pin(s)	Function
A_0-A_{10}	Address
PD/PGM	Power down/Program
CS	Chip Select
O_0-O_7	Outputs

2716 Timing diagram

 


Sample of the data sheet for the 2716 A.C. Characteristics.

Symbol	Parameter	Limits			Unit	Test Condition
		Min	Typ.	Max		
t_{ACC1}	Addr. to Output Delay		250	450	ns	PD/PGM = $\overline{CS} = V_{IL}$
t_{OH}	Addr. to Output Hold	0			ns	PD/PGM = $\overline{CS} = V_{IL}$
t_{DF}	Chip Deselect to Output Float	0		100	ns	PD/PGM = V_{IL}
...

Memory Interface

SRAMs

 - * Data is available as long as power supplied
- * Volatile Memory: as data is lost at power down
- * **TI TMS 4016 SRAM (2K X 8):**



Pin(s)	Function
A_0 - A_{10}	Address
DQ_0 - DQ_7	Data In/Data Out
S (CS)	Chip Select
G (OE)	Read Enable
W (WE)	Write Enable


- * Virtually identical to the EPROM with respect to the pinout.
- * However, access time is faster (250ns).
- * See the timing diagrams and data sheets in text.
- * Modern SRAMs used for caches have access times as low as 10ns.

Memory Interface

SRAMs

* 62256 (32K X 8) RAM

- * Access Time: 120-150 ns

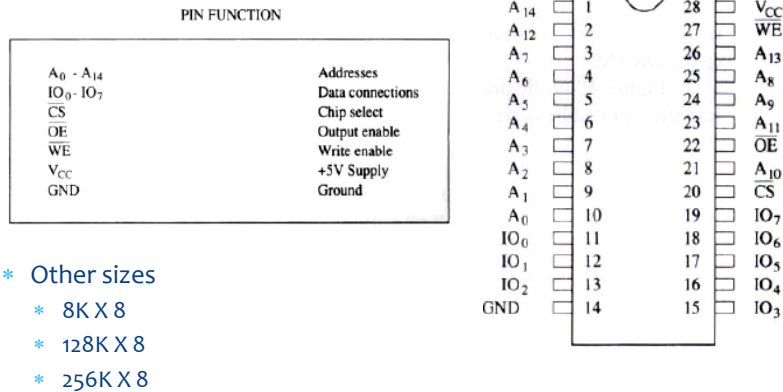


* Other sizes

- * 8K X 8
- * 128K X 8
- * 256K X 8

DRAM

- * SRAMs are limited in size (up to 1M X 8).
- * DRAMs are available in much larger sizes (up to 4G; 256 x 8, 4G x 1).
- * Requires as little as 70 ns to access data
 - * DRAMs MUST be refreshed (rewritten) every 2 to 4 ms
- * This refresh is performed by a special circuit in the DRAM which refreshes the entire memory.
 - * Refresh also occurs on a normal read or write.
- * The large storage capacity of DRAMs make it impractical to add the required number of address pins.
 - * Instead, the address pins are multiplexed.

TI TMS4464 DRAM

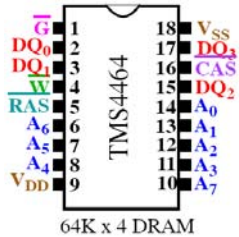


Pin(s)	Function
A ₀ -A ₇	Address
DQ ₀ -DQ ₃	Data In/Data Out
RAS	Row Address Strobe
CAS	Column Address Strobe
G	Output Enable
W	Write Enable

CS

- * Total chip capacity → **256K bits** of data.
- * It has **64K** addressable locations which means it needs 16 address inputs, but **it has only 8**.
 - * 16 address bits can be forced into eight address pins in two 8-bit increments
 - * The **row address** (A₀ - A₇) are placed on the address pins and strobed into a set of internal latches by **RAS**
 - * The **column address** (A₈ - A₁₅) is then strobed in using **CAS**

TI TMS4464 DRAM timing diagram

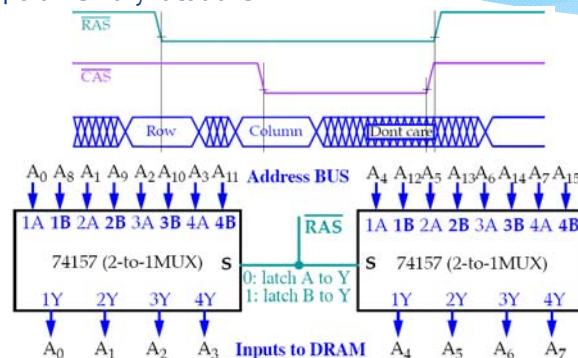- * 16-bit address in the internal latches, which addresses the contents of one of the 4-bit memory locations.




- * Multiplexers used to strobe col and row addresses into the 8 address pins
- * **RAS** signal strobes the row address into the DRAM and selects which part of the address is applied to the address inputs.

Memory address decoding

- * The processor can usually address a memory space that is *much larger than the memory space covered by an individual memory chip.*
- * In order to splice a memory device into the address space of the processor, decoding is necessary.
- * For example, the 8088 issues **20-bit addresses for a total of 1MB of memory address space.**
- * However, the BIOS on a 2716 EPROM has only 2KB of memory and 11 address pins.
- * A decoder can be used to decode the additional 9 address pins and allow the EPROM to be placed in any 2KB section of the 1MB address space.


NAND gate decoder

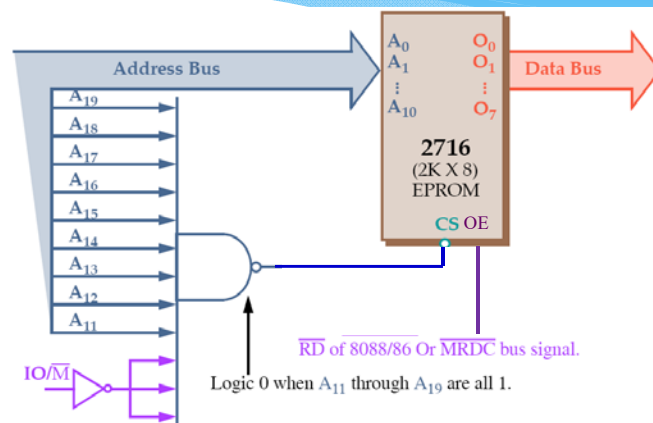

OE connection for RD (PD/PGM pin on chip)


20-bit address decoding

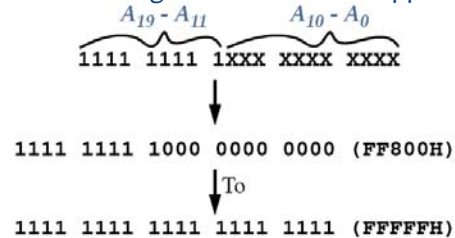- * To determine the address range that a device is mapped into:




- * This 2KB memory segment maps into the **reset location** of the 8086/8088 (FFFF0H).
- * NAND gate decoders are not often used
 - * Large fan-in NAND gates are not efficient
 - * Multiple NAND gate IC's might be required to perform such decoding
 - * Rather the 3-to-8 Line Decoder (74LS138) is more common.

3-to-8 line decoder (74LS138)

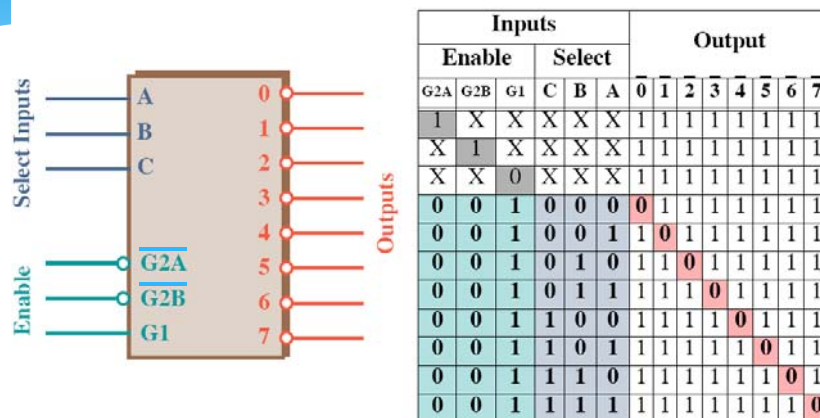

- * Note that all three Enables ($\overline{G2A}$, $\overline{G2B}$, and $G1$) must be active, e.g. low, low and high, respectively.
- * Each output of the decoder can be attached to an 2764 EPROM (8K X 8).


Memory address decoding

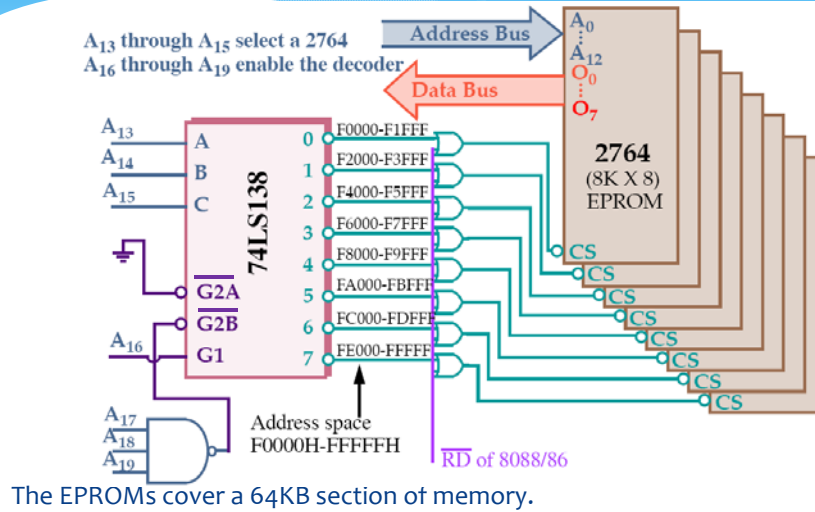

Memory address decoding

* AMD 16L8 PAL decoder

- * Commonly used to decode the memory address, particularly for 32-bit addresses generated by the 80386DX and above.
- * It has 10 fixed inputs (Pins 1-9, 11), two fixed outputs (Pins 12 and 19) and 6 pins that can be **either** (Pins 13-18).
- * AND/NOR device with logic expressions (outputs) with up to 16 ANDed inputs and 7 ORed product terms.
- * **Programmed to decode address lines A_{19} - A_{13} onto 8 outputs.**

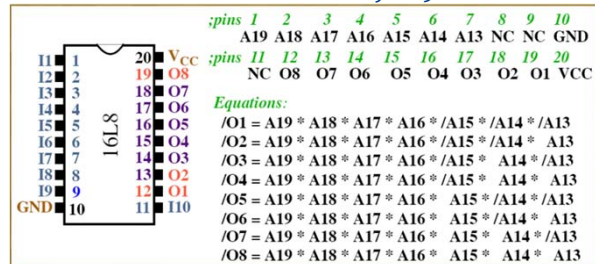

Next Time

- * Memory Interfacing
 - * 8-bit memory interface

