

CMPE 212

Spring, 2016

Project 2 Report

Sabbir Ahmed  
Teaching assistant:  
Ahmed Shahin


## 1. Project description:

The goal of this project is to design and implement a finite state machine through combinational and sequential circuits. With one 1-bit input corresponding to 25 ¢ or 10 ¢, the machine is to behave similarly to a vending machine dispensing an output after an amount of 70 ¢ or higher has been accumulated, except when the excess is either 5 ¢ or 15 ¢, in which case a change of 5 ¢ will also be outputted leaving the remaining as credit for the next simulation.

## 2. Process:
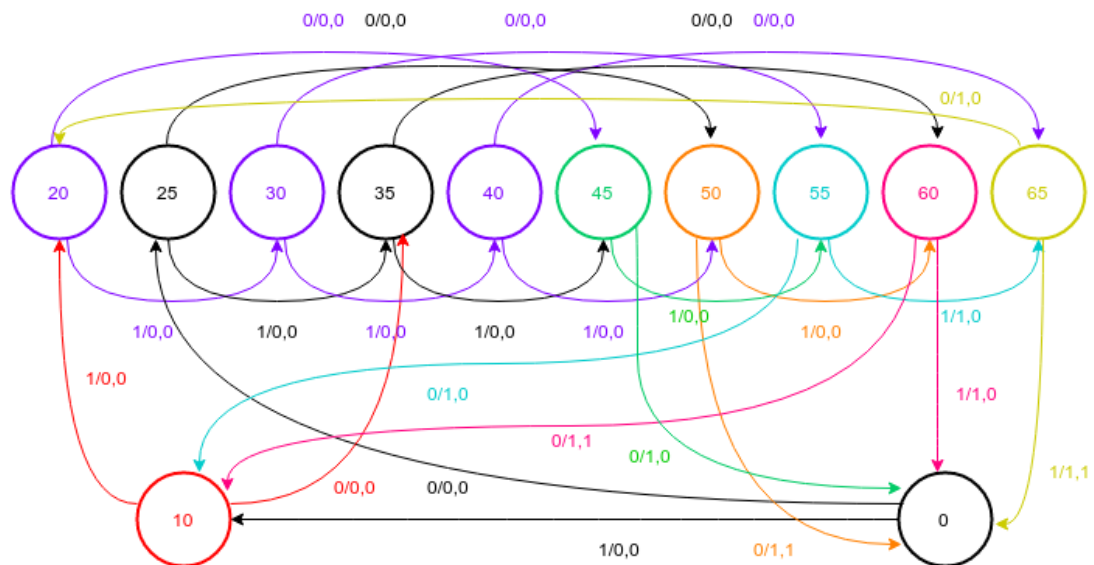
### a. State diagram:

The following state diagram was derived from the description:



State diagram for a vending machine finite state machine with outputs y0, y1

The states were verified by an executable Python script, `vending_machine_fsm.py` attached to the report in the `src` directory. The script is written in Python 2.7 syntax.

### Usage:

Systems with a python2 compiler as default:

```
python vending_machine_fsm.py
```

Systems with a newer Python compiler:

```
python2.x vending_machine_fsm.py
```

The script generates the following outputs:

```
Switch = 0
A 0000 -> D 0010 (0, 0)
C 0011 -> H 0110 (0, 0)
B 0001 -> F 0101 (0, 0)
E 0100 -> J 1101 (0, 0)
D 0010 -> I 1100 (0, 0)
G 0111 -> L 1110 (0, 0)
F 0101 -> K 1111 (0, 0)
I 1100 -> A 0000 (1, 1)
H 0110 -> A 0000 (1, 0)
K 1111 -> B 0001 (1, 1)
J 1101 -> B 0001 (1, 0)
L 1110 -> C 0011 (1, 0)
```

```
Switch = 1
A 0000 -> B 0001 (0, 0)
C 0011 -> E 0100 (0, 0)
B 0001 -> C 0011 (0, 0)
E 0100 -> G 0111 (0, 0)
D 0010 -> F 0101 (0, 0)
G 0111 -> I 1100 (0, 0)
F 0101 -> H 0110 (0, 0)
I 1100 -> K 1111 (0, 0)
H 0110 -> J 1101 (0, 0)
K 1111 -> A 0000 (1, 0)
J 1101 -> L 1110 (0, 0)
L 1110 -> A 0000 (1, 1)
```

12 states with their corresponding code assignments

## b. Functions:

The script was also used to determine the minterms for each of the Boolean functions for the 4 flip flops and 2 outputs:

```
Default don't cares: [8, 9, 11, 10, 24, 25, 27, 26]
J0 [2, 4, 5, 7, 22, 23]
J0_D [12, 13, 14, 15, 28, 29, 30, 31]
J1 [1, 2, 3, 18, 19]
J1_D [4, 5, 6, 7, 12, 13, 14, 15, 20, 21, 22, 23, 28, 29, 30, 31]
J2 [0, 5, 17, 20, 21, 28, 29]
J2_D [2, 3, 6, 7, 14, 15, 18, 19, 22, 23, 30, 31]
J3 [4, 14, 16, 18, 20, 22, 28]
J3_D [1, 3, 5, 7, 13, 15, 17, 19, 21, 23, 29, 31]
K0 [12, 13, 14, 15, 30, 31]
K0_D [0, 1, 2, 3, 4, 5, 6, 7, 16, 17, 18, 19, 20, 21, 22, 23]
K1 [6, 12, 13, 14, 15, 30, 31]
K1_D [0, 1, 2, 3, 16, 17, 18, 19]
K2 [2, 6, 15, 18, 19, 22, 23, 30, 31]
K2_D [0, 1, 4, 5, 12, 13, 16, 17, 20, 21, 28, 29]
K3 [3, 7, 19, 21, 23, 29, 31]
K3_D [0, 2, 4, 6, 12, 14, 16, 18, 20, 22, 28, 30]
z0 [6, 12, 13, 14, 15, 30, 31]
z1 [12, 15, 30]
```

Minterms for all the functions generated by simulating the state machine  
(variables with '\_D' represent don't cares)

The minterms were then used to reduce functions through use of Karnaugh maps:

	$\bar{D}\bar{E}$	$\bar{D}E$	$DE$	$D\bar{E}$
$\bar{A}\bar{B}\bar{C}$	0	0	0	1
$\bar{A}\bar{B}C$	1	1	1	0
$\bar{A}B\bar{C}$	x	x	x	x
$\bar{A}BC$	x	x	x	x
$A\bar{B}\bar{C}$	0	0	0	0
$A\bar{B}C$	0	0	1	1
$AB\bar{C}$	x	x	x	x
$ABC$	x	x	x	x

$$j0 = \bar{A}\bar{C}\bar{D} + \bar{A}CE + ACD + \bar{A}CDE$$

	$\bar{D}\bar{E}$	$\bar{D}E$	$DE$	$D\bar{E}$
$\bar{A}\bar{B}\bar{C}$	x	x	x	x
$\bar{A}\bar{B}C$	x	x	x	x
$\bar{A}B\bar{C}$	1	1	1	1
$\bar{A}BC$	x	x	x	x
$A\bar{B}\bar{C}$	x	x	x	x
$A\bar{B}C$	x	x	x	x
$AB\bar{C}$	0	0	1	1
$ABC$	x	x	x	x

$$k0 = \bar{A} + D$$

	$\bar{D}\bar{E}$	$\bar{D}E$	$D\bar{E}$	$DE$
$\bar{A}\bar{B}\bar{C}$	0	1	1	1
$\bar{A}\bar{B}C$	x	x	x	x
$\bar{A}B\bar{C}$	x	x	x	x
$\bar{A}BC$	x	x	x	x
$A\bar{B}\bar{C}$	0	0	1	1
$A\bar{B}C$	x	x	x	x
$AB\bar{C}$	x	x	x	x
$ABC$	x	x	x	x

$$j1 = \bar{A}E + D$$

	$\bar{D}\bar{E}$	$\bar{D}E$	$D\bar{E}$	$DE$
$\bar{A}\bar{B}\bar{C}$	x	x	x	x
$\bar{A}\bar{B}C$	0	0	0	1
$\bar{A}B\bar{C}$	1	1	1	1
$\bar{A}BC$	x	x	x	x
$A\bar{B}\bar{C}$	x	x	x	x
$A\bar{B}C$	0	0	0	0
$AB\bar{C}$	0	0	1	1
$ABC$	x	x	x	x

$$k1 = \bar{A}B + BD + \bar{A}D\bar{E}$$

	$\bar{D}\bar{E}$	$\bar{D}E$	$D\bar{E}$	$DE$
$\bar{A}\bar{B}\bar{C}$	1	0	x	x
$\bar{A}\bar{B}C$	0	1	x	x
$\bar{A}B\bar{C}$	0	0	x	x
$\bar{A}BC$	x	x	x	x
$A\bar{B}\bar{C}$	0	1	x	x
$A\bar{B}C$	1	0	x	x
$AB\bar{C}$	1	1	x	x
$ABC$	x	x	x	x

$$j2 = AE + AC + \bar{A}\bar{C}\bar{E} + \bar{B}CE$$

	$\bar{D}\bar{E}$	$\bar{D}E$	$D\bar{E}$	$DE$
$\bar{A}\bar{B}\bar{C}$	x	x	0	1
$\bar{A}\bar{B}C$	x	x	0	1
$\bar{A}B\bar{C}$	x	x	1	0
$\bar{A}BC$	x	x	x	x
$A\bar{B}\bar{C}$	x	x	1	1
$A\bar{B}C$	x	x	1	1
$AB\bar{C}$	x	x	1	1
$ABC$	x	x	x	x

$$k2 = A + \bar{B}\bar{E} + BE$$

	$\bar{D}\bar{E}$	$\bar{D}E$	$D\bar{E}$	$DE$
$\bar{A}\bar{B}\bar{C}$	0	x	x	0
$\bar{A}\bar{B}C$	1	x	x	0
$\bar{A}B\bar{C}$	0	x	x	1
$\bar{A}BC$	x	x	x	x
$A\bar{B}\bar{C}$	1	x	x	1
$A\bar{B}C$	1	x	x	1
$AB\bar{C}$	1	x	x	0
$ABC$	x	x	x	x

$$j3 = A\bar{B} + A\bar{D} + \bar{B}C\bar{D} + \bar{A}BD$$

	$\bar{D}\bar{E}$	$\bar{D}E$	$D\bar{E}$	$DE$
$\bar{A}\bar{B}\bar{C}$	x	0	1	x
$\bar{A}\bar{B}C$	x	0	1	x
$\bar{A}B\bar{C}$	x	0	0	x
$\bar{A}BC$	x	x	x	x
$A\bar{B}\bar{C}$	x	0	1	x
$A\bar{B}C$	x	1	1	x
$AB\bar{C}$	x	1	1	x
$ABC$	x	x	x	x

$$k3 = \bar{B}D + AC$$

	$\overline{D.E}$	$\overline{D.E}$	$D.E$	$D.E$
$\overline{A.B.C}$	0	0	0	0
$\overline{A.B.C}$	0	0	0	1
$\overline{A.B.C}$	1	1	1	1
$\overline{A.B.C}$	x	x	x	x
$A.B.C$	0	0	0	0
$A.B.C$	0	0	0	0
$A.B.C$	0	0	1	1
$A.B.C$	x	x	x	x


$$y_0 = \overline{A}B + BD + \overline{A}\overline{C}D\overline{E}$$

	$\overline{D.E}$	$\overline{D.E}$	$D.E$	$D.E$
$\overline{A.B.C}$	0	0	0	0
$\overline{A.B.C}$	0	0	0	0
$\overline{A.B.C}$	1	0	1	0
$\overline{A.B.C}$	x	x	x	x
$A.B.C$	0	0	0	0
$A.B.C$	0	0	0	0
$A.B.C$	0	0	0	1
$A.B.C$	x	x	x	x

$$y_1 = \overline{A}B\overline{D}\overline{E} + \overline{A}BDE + \overline{A}BD\overline{E}$$

 **c. Design:**

After several Boolean function manipulation, a design for the circuit was realized. Since the number of flip flops can be found by computing  $\lceil \log_2(states) \rceil$ , 4 JK flip flops were used. A decoder was used as well to generate 4 3-bit minterms that were used multiple times. The following schematic was designed and used as the working blueprint during the implementation:



**Circuit design of the vending machine finite state machine**

#### d. Verification and simulation:

The logic of the entire circuit was verified using Verilog. Several testbenches have been included along with a makefile for convenience. The scripts were compiled using Icarus Verilog (iverilog) successfully, and ncvrilog on GL, where it showed occasional runtime errors.

##### Usage:

Compile testbench for JK flip flop module:

```
make jk
```

Compile testbench for the machine:

```
make compile
```


Run executable:

```
make run
```

Simulate the testbench (after running script):

```
make simulate
```

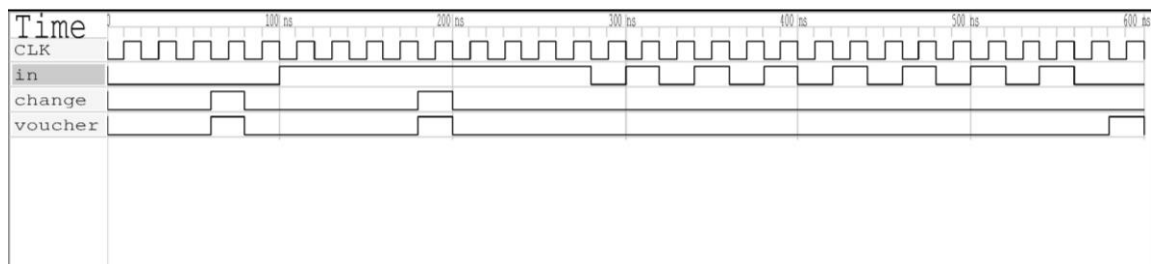The following was simulated using the main testbench:



Timing diagram simulated on GTKWave on a Debian Linux system

### 3. Conclusion:

After the designing processes were completed, the circuit was constructed on a breadboard, and the logic above was verified again. Due to possible pin mapping errors and/or flawed logic, the state machine was not able to be implemented correctly and debugging the entire machine was not possible.