

1 Background

Create a synthesizable sequential module that accepts two 4-bit inputs *x* and *y* and generates a 4-bit output *q* based on *x* and a function selector *s*. The selector should select the bit-wise operator to be applied to *x* and *y* in order to produce *q*. The output *q* should be a registered output, and so the module should accept *clk* signal *clk*. There should be no unnecessary cycle delays from input to the output.

- 0: and
- 1: or
- 2: xor
- 3: nand
- 4: nor

2 Implementation

The output '*q*' was generated in a case block with bitwise operators applied to the inputs '*x*' and '*y*'.

The module implementation along with its testbench can be found in the 'scripts' directory. A sample of the waveform generated is provided:

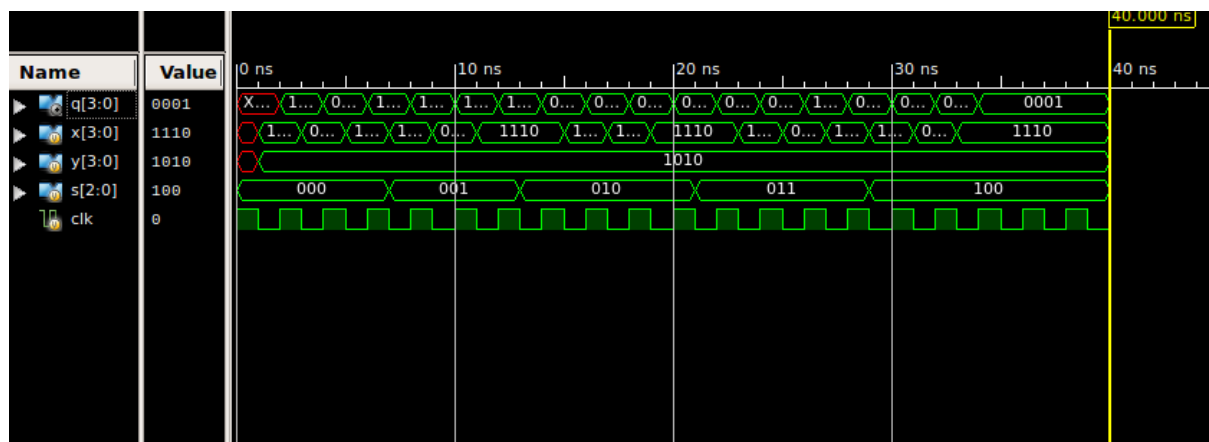


Figure 1: Waveform Generated from Part 4 Test Bench

A table of the inputs and outputs generated in the test bench is also generated:

Table 1: Inputs and Outputs of The Part 4 Test Bench

x	op	y	q	s
1001	&	1010	1000	0
0000	&	1010	0000	0
1110	&	1010	1010	0
1001		1010	1011	1
0101		1010	1111	1
1110		1010	1110	1
1001	^	1010	0011	2
1111	^	1010	0101	2
1110	^	1010	0100	2
1001	~&	1010	0111	3
0000	~&	1010	1111	3
1110	~&	1010	0101	3
1001	~	1010	0100	4
0101	~	1010	0000	4
1110	~	1010	0001	4