

1 Background

Create a synthesizable combinational module that accepts a 4-bit input x and generates a single-bit output y based on x and function select signal s . The selector should select which reduction operator to be applied to x in order to produce y according to the following:

- 0: and
- 1: or
- 2: xor
- 3: nand
- 4: nor

2 Implementation

The output 'y' was generated in a case block with reduction operators applied to the input 'x'.

The module implementation along with its testbench can be found in the 'scripts' directory. A sample of the waveform generated is provided:

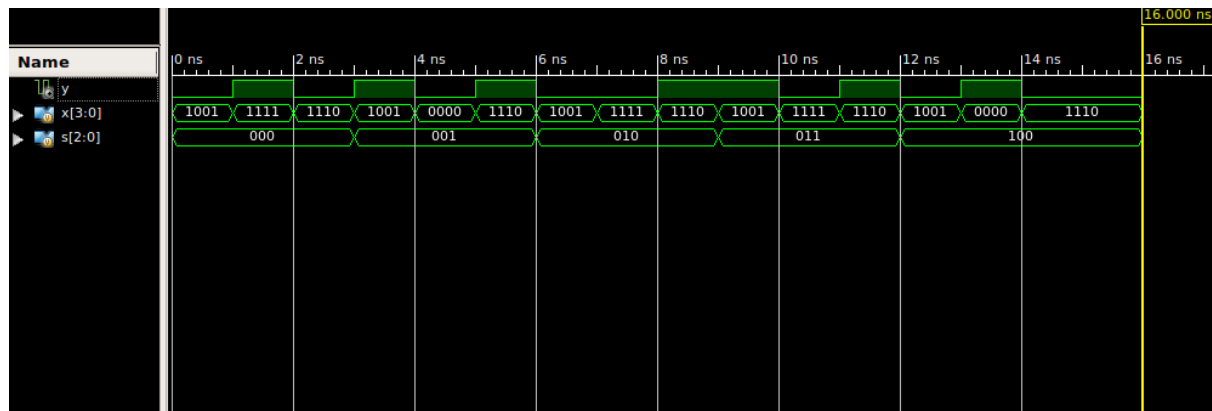


Figure 1: Waveform Generated from Part 3 Test Bench

A table of the inputs and outputs generated in the test bench is also generated:

Table 1: Inputs and Outputs of The Part 3 Test Bench

| op | x | y |
|-----------|----------|----------|
| & | 1001 | 0 |
| & | 1111 | 1 |
| & | 1110 | 0 |
| | 1001 | 1 |
| | 0000 | 0 |
| | 1110 | 1 |
| ^ | 1001 | 0 |
| ^ | 1111 | 0 |
| ^ | 1110 | 1 |
| ~& | 1001 | 1 |
| ~& | 1111 | 0 |
| ~& | 1110 | 1 |
| ~ | 1001 | 0 |
| ~ | 0000 | 1 |
| ~ | 1110 | 0 |