

CMPE 310 Systems Design and Programming

L8: Chapter 10 – Memory Interface

UMBC

AN HONORS UNIVERSITY IN MARYLAND


L8 Objectives

- * To interface memory components to x86 – Pentium
- * Diagram how EPROM and SRAM modules are connected to x86 – Pentium

8086 - 80386SX (16-bit) memory interface

These machines differ from the 8088/80188 in several ways:

- * The data bus is 16-bits wide.
- * The $\overline{IO/\overline{M}}$ pin is replaced with $\overline{M/\overline{IO}}$ (8086/80186) and \overline{MRDC} and \overline{MWTC} for 80286 and 80386SX.
- * \overline{BHE} , **Bus High Enable**, control signal is added.
- * Address pin A_0 (or \overline{BLE} , **Bus Low Enable**) is used differently.
- * The 16-bit data bus presents a new problem:
 - * The microprocessor must be able to read and write data to any 16-bit location in addition to any 8-bit location.
 - * The data bus and memory are divided into banks:

 


8086 - 80386SX (16-bit) memory interface

\overline{BHE} and \overline{BLE} are used to select one or both:

\overline{BHE}	\overline{BLE}	Function
0	0	Both banks enabled for 16-bit transfer
0	1	High bank enabled for an 8-bit transfer
1	0	Low bank enabled for an 8-bit transfer
1	1	No banks selected

- * Bank selection can be accomplished in two ways:
 - * Separate write decoders for each bank (which drive \overline{CS}) OR
 - * A separate write signal (strobe) to each bank (which drive \overline{WE}).
 - * Note that 8-bit read requests in this scheme are handled by the microprocessor (it selects the bits it wants to read from the 16-bits on the bus).
- * Note in either method that A_0 does not connect to memory and bus wire A_1 connects to memory pin A_0 , A_2 to A_1 , etc.

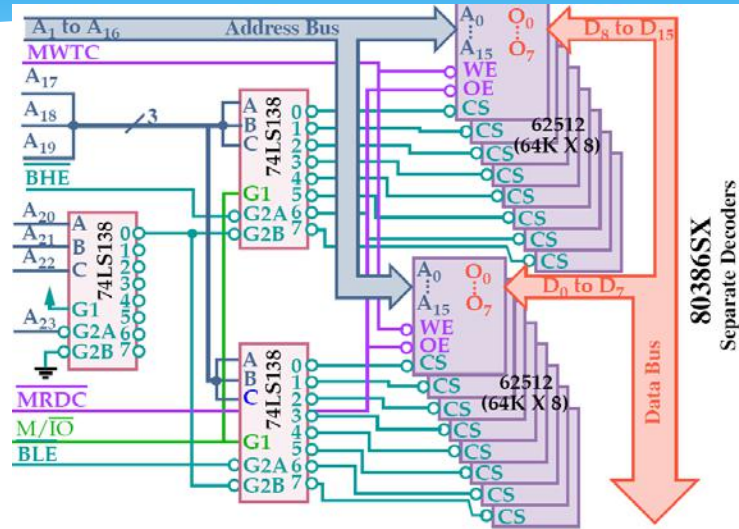
16-bit memory interface (separate decoders)



* 16 64K RAMs fill memory from 000000H through FFFFFFFH, for 1M bytes memory

16-bit memory interface (separate write strobe)

 - * A separate write strobe for each memory bank can be generated to handle bank selection by using a 74LS32 OR gate to combine A_0 or \overline{BHE} with \overline{WR}
 - * \overline{WR} is generated by using the \overline{MWTC}
 - * Only require 1 decoder to select a 16-bit wide memory




- * See text for *Separate Write Strobe* scheme plus some examples of the integration of EPROM and SRAM in a complete system.
 - * It is just an application of what we've been covering.

80386DX and 80486 (32-bit) memory interface

- * 80386DX and 80486 have 32-bit data buses and therefore 4 banks of memory.
- * 32-bit, 16-bit and 8-bit transfers are accomplished by different combinations of the bank selection signals \overline{BE}_3 , \overline{BE}_2 , \overline{BE}_1 , \overline{BE}_0 .
- * The Address bits A_0 and A_1 are used within the microprocessor to generate these signals.
 - * They are *don't cares* in the decoding of the 32-bit address outside the chip (using a PLD such as the **PAL 16L8**).
- * The high clock rates of these processors usually require **wait states** for memory access.

80386DX and 80486 (32-bit) memory interface

 
- ◆ Separate write strobes are developed, by using a simple 74LS32 OR gate




- ◆ A memory interface for 80386DX or 80486 **requires four bank write strobes for each memory bank** and decoding a 32-bit address.
- ◆ There are no integrated decoders, such as the 74LS138, that can easily accommodate a memory interface for the 80386DX or 80486
 - * **PLD is often used for bank write signal generation** because of its sizeable address bits

Pentium (64-bit) memory interface

- * The Pentium, Pentium Pro, Pentium II and III contain a 64-bit data bus.
- * Therefore, 8 decoders or 8 write strobes are needed as well as 8 memory banks.
- * The write strobes are obtained by combining the bank enable signals ($\overline{\text{BEx}}$) with the $\overline{\text{MWTC}}$ signal.
- * $\overline{\text{MWTC}}$ is generated by combining the $\overline{\text{M/IO}}$ and $\overline{\text{W/R}}$ signals.

 


Pentium (64-bit) memory interface

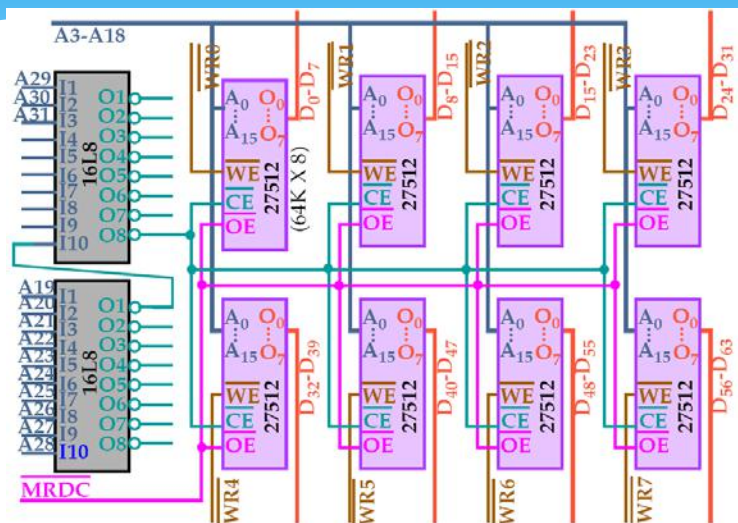

- * Select 512K RAM memory components (FFF80000-FFFFFFFF)

Pentium (64-bit) memory interface

 In order to map previous memory into addr. space $FFF80000H-FFFFFFFFH$



pins 1 2 3 4 5 6 7 8 9 10
A29 A30 A31 NC NC NC NC NC NC GND
pins 11 12 13 14 15 16 17 18 19 20
U2 CE NC NC NC NC NC NC NC VCC

Equations:

$$\overline{U2} = \overline{U2} * A29 * A30 * A31$$

pins 1 2 3 4 5 6 7 8 9 10
A19 A20 A21 A22 A23 A24 A25 A26 A27 GND
pins 11 12 13 14 15 16 17 18 19 20
A28 U2 NC NC NC NC NC NC VCC

Equations:

$$\overline{U2} = A19 * A20 * A21 * A22 * A23 * A24 * A25 * A26 * A27 * A28$$

- * Use a 16L8 to do the $\overline{WR0} - \overline{WR7}$ decoding using \overline{MWTC} and $\overline{BE0} - \overline{BE7}$.
- * See the text -- Figure 10-37.

Next Time

- * IO Interface

STOP