

CMPE 212

Principles of Digital Design

Lecture 9

Synthesis of Combinational Circuits

February 22, 2016

www.csee.umbc.edu/~younis/CMPE212/CMPE212.htm



Lecture's Overview

Previous Lecture:

- Canonical form of switching functions
(conversion from simplified to canonical form)
- Analyzing switching circuits using algebraic methods
(Truth table and Derivation of logic function)
- Analysis of timing diagram
- Effect of physical characteristics
(propagation delay and power dissipation)


This Lecture

- Synthesis of combinational logic circuits

Analysis of Combinational Circuits

- ❑ Digital circuits are designed by transforming a word description of a function into a switching equation and then a circuit
 - ➔ Digital circuit analysis is the opposite process
- ❑ A digital circuit can be described by:
 - 1) Switching function (algebraic method)
 - 2) Hardware design language module
 - 3) Truth tables
 - 4) Timing diagram
- ❑ Analysis of a logic circuit is used to:
 - determine that its behavior of matches specifications
 - transform the circuit to a different format to optimize the implementation

Example: Algebraic Method

 

$$f(a, b, c) = \overline{(a \oplus b)(b \oplus c) \cdot (\bar{a} + \bar{b} + a + c)}$$

Algebraic Simplification

$$\begin{aligned}f(a, b, c) &= \overline{(a \oplus b)(b \oplus c) \cdot (\bar{a} + \bar{b} + a + c)} \\&= \overline{(a \oplus b)(b \oplus c)} + \overline{(\bar{a} + \bar{b} + a + c)} \\&= (a \oplus b)(b \oplus c) + (\bar{a} + \bar{b})(a + c) \\&= (a\bar{b} + \bar{a}b)(b\bar{c} + \bar{b}c) + \bar{a}a + \bar{a}c + \bar{b}a + \bar{b}c \\&= a\bar{b}b\bar{c} + a\bar{b}\bar{b}c + \bar{a}bb\bar{c} + \bar{a}b\bar{b}c + 0 + \bar{a}c + \bar{b}a + \bar{b}c \\&= 0 + a\bar{b}c + \bar{a}b\bar{c} + \bar{a}c + \bar{b}a + \bar{b}c \\&= \bar{a}b\bar{c} + \bar{a}c + \bar{b}a + \bar{b}c \quad \text{Consensus} \\&= \bar{a}b\bar{c} + \bar{a}c + \bar{b}a = \bar{a}(b\bar{c} + c) + \bar{a}b \\&= \bar{a}(b + c) + a\bar{b} = \bar{a}b + \bar{a}c + a\bar{b} = (a \oplus b) + \bar{a}c\end{aligned}$$

Truth Table Method

❑ Build the truth table for the circuit and then derive a simplified switching function using SOP or POS

❑ Example:

to simplify
the previous
circuit

$\prod M(0,1,7)$

a	b	c	$\overline{(a \oplus b)(b \oplus c)} \cdot \overline{(\bar{a} + \bar{b} + \bar{a} + \bar{c})}$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

$$\begin{aligned}
 f(a, b, c) &= (a + b + c)(\bar{a} + \bar{b} + c)(\bar{a} + \bar{b} + \bar{c}) = (a + b + c)(\bar{a} + \bar{b}) \\
 &= a\bar{a} + a\bar{b} + b\bar{a} + b\bar{b} + \bar{a}c + \bar{b}c = a\bar{b} + b\bar{a} + \bar{a}c + \bar{b}c \\
 &= \mathbf{a\bar{b}} + \mathbf{b\bar{a}} + \mathbf{\bar{a}c} + \mathbf{\bar{b}c} = \mathbf{a\bar{b}} + \mathbf{b\bar{a}} + \mathbf{\bar{a}c} = \mathbf{(a \oplus b) + \bar{a}c}
 \end{aligned}$$


Timing Diagram

- ❑ Apply a sequence of input and observe corresponding output
- ❑ Useful for analyzing the propagation delay:

Time	Input (A, B, C)	Output	
		$f_1(A, B, C)$	$f_2(A, B, C)$
t_0	000	0	0
t_1	001	1	1
t_2	010	1	0
t_3	011	0	1
t_4	100	0	0
t_5	101	0	1
t_6	110	1	1
t_7	111	1	0



$$f_1(A, B, C) = \sum m(1, 2, 6, 7)$$

$$f_2(A, B, C) = \sum m(1, 3, 5, 6)$$


 


Propagation Delay

  - Propagation delay is time for the output to become ready after the input gets changed



  - Propagation delay depends on the microelectronics technology and size
- Rising and falling time may differ
- $t_{PD} = \frac{1}{2} (t_{PDH} + t_{PDL})$




Important Physical Characteristics

- Physical characteristics vary depending on the microelectronics technology used in the design and fabrication
- There is a trade-off between speed, power dissipation and cost


Logic family	Propagation Delay t_{PD} (ns)	Power Dissipation Per Gate (mW)	Technology
7400	10	10	Standard TTL
74H00	6	22	High-speed TTL
74L00	33	1	Low-power TTL
74LS00	9.5	2	Low-power Schottky TTL
74S00	3	19	Schottky TTL
74ALS00	3.5	1.3	Advanced low-power Schottky TTL
74AS00	3	8	Advanced Schottky TTL
74HC00	8	0.17	High-speed CMOS

Timing Diagram with Delay

 

ABC	$Y=f(A,B,C)$
000	0
001	1
010	0
011	0
100	1
101	1
110	1
111	0

$$f(A,B,C) = \sum m(1,4,5,6)$$

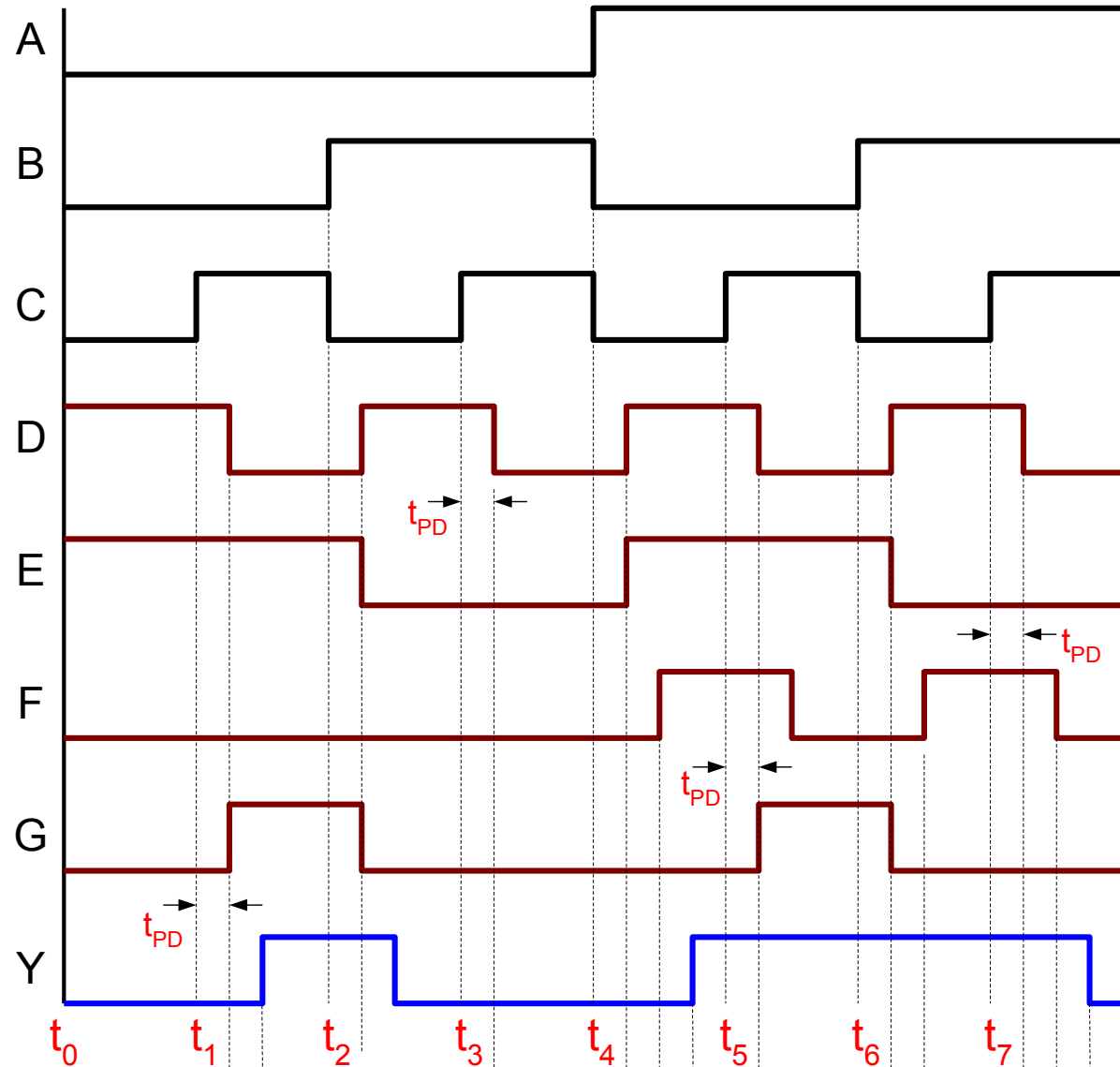


Logic Synthesis

Definition: To design a logic circuit such that it meets the specifications and can be economically manufactured:

- Performance – meets delay specification, or has minimum delay.
- Cost – uses minimum hardware, smallest chip area, smallest number of gates or transistors.
- Power – meets power specification, or consumes minimum power.
- Testability – has no redundant (untestable) logic and is easily testable.


Procedure:

 1. Minimization – Obtain MSOP or MPOS. This is also known as two-level minimization because the result can be implemented as a two-level AND-OR or NAND-NAND or NOR-NOR circuit.
2. Technology mapping – Considering design requirements, transform the minimized form into one of the technologically realizable forms:
 - Programmable logic array (PLA)
 - Field programmable gate array (FPGA)
 - Others . . .




Two-Level AND-OR Implementation

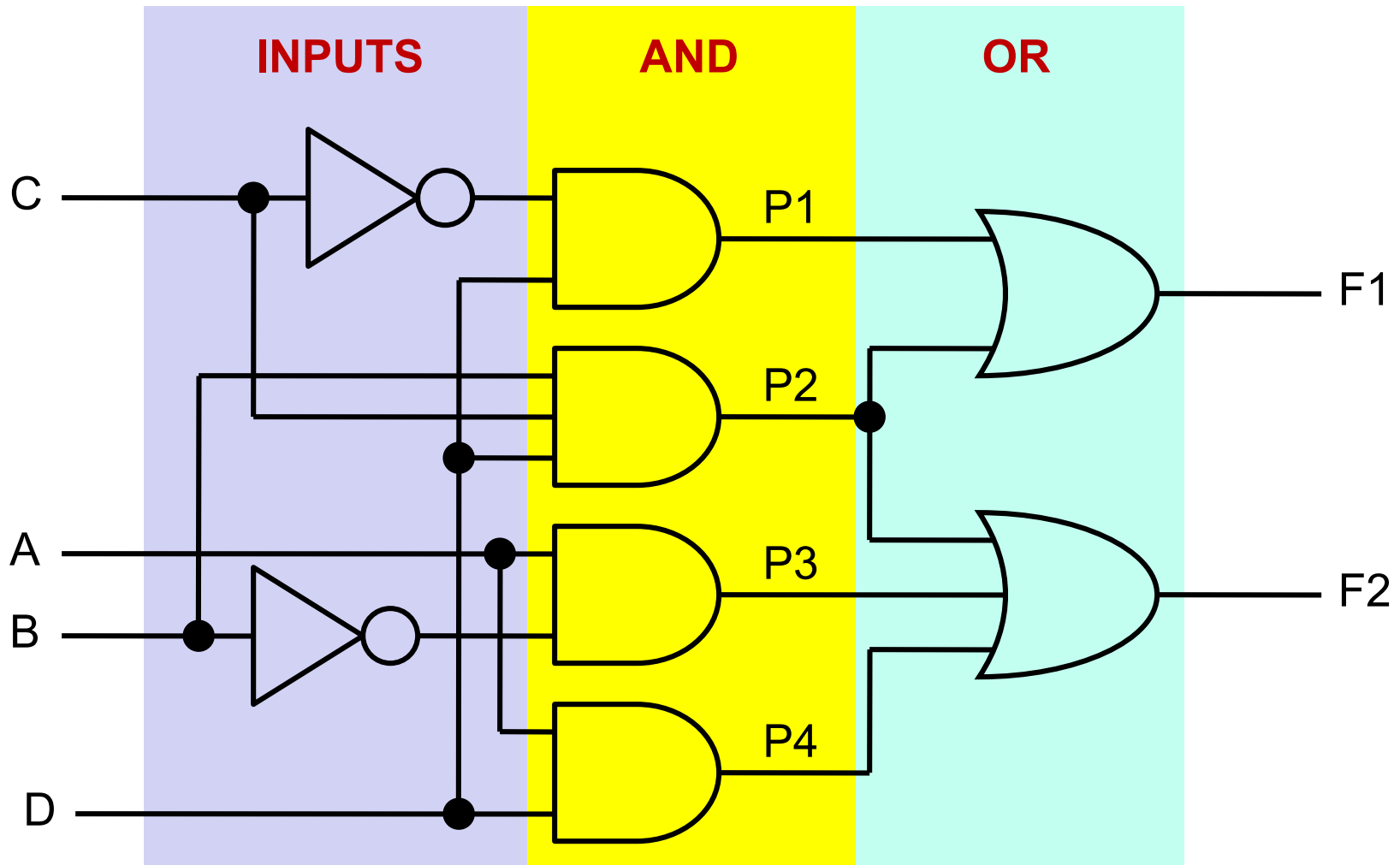- Also known as technology-independent circuit.




Slide contents are courtesy of Vishwani D. Agrawal

Bubbles Matching and Gate Conversion

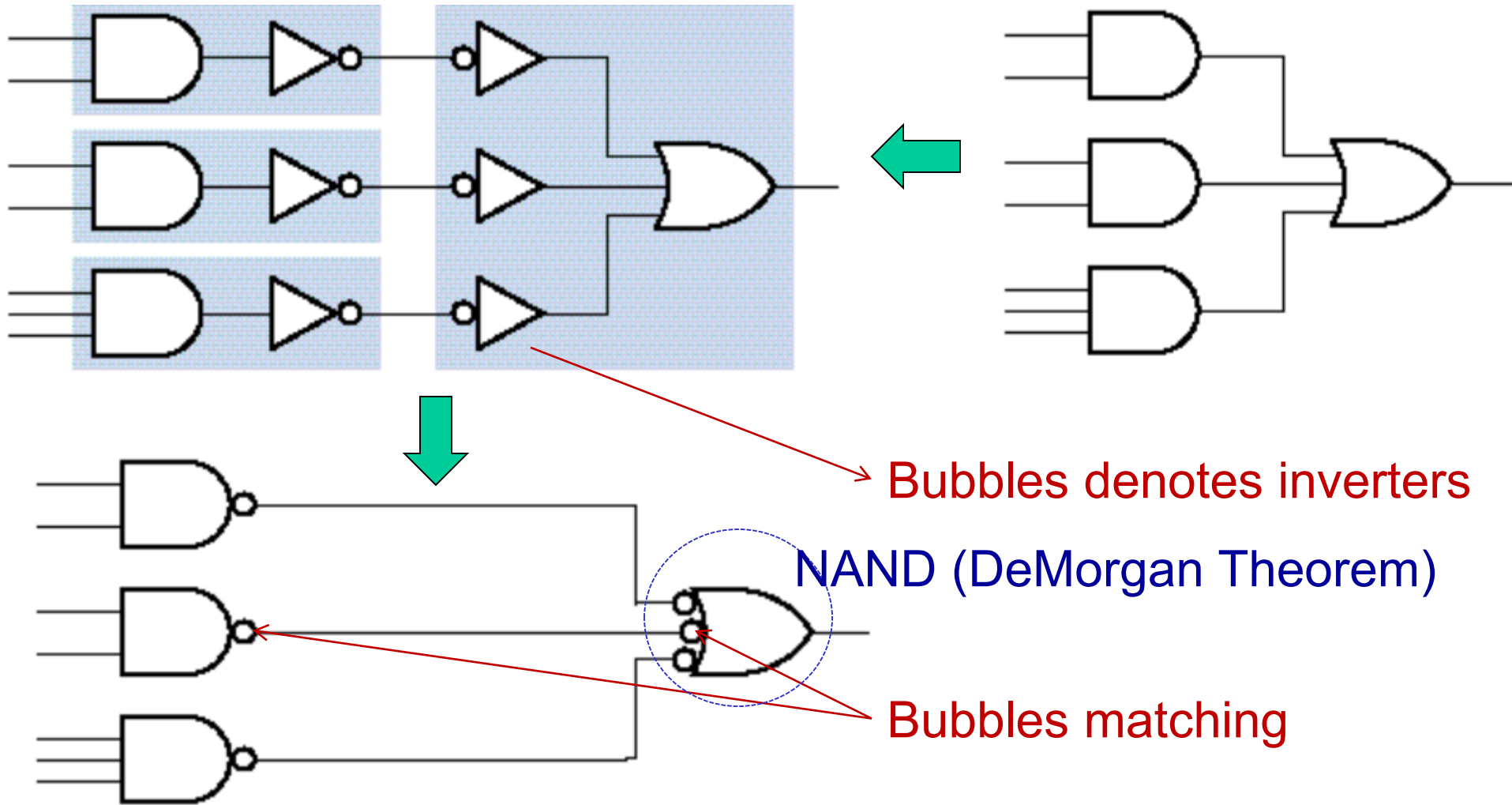


Implementing NAND (and NOR) gates requires fewer transistors than AND (and OR) gates → Convert AND-OR to NAND-NAND or NOR-NOR


OR-AND Conversion to NOR-NOR

 

Inverse Process

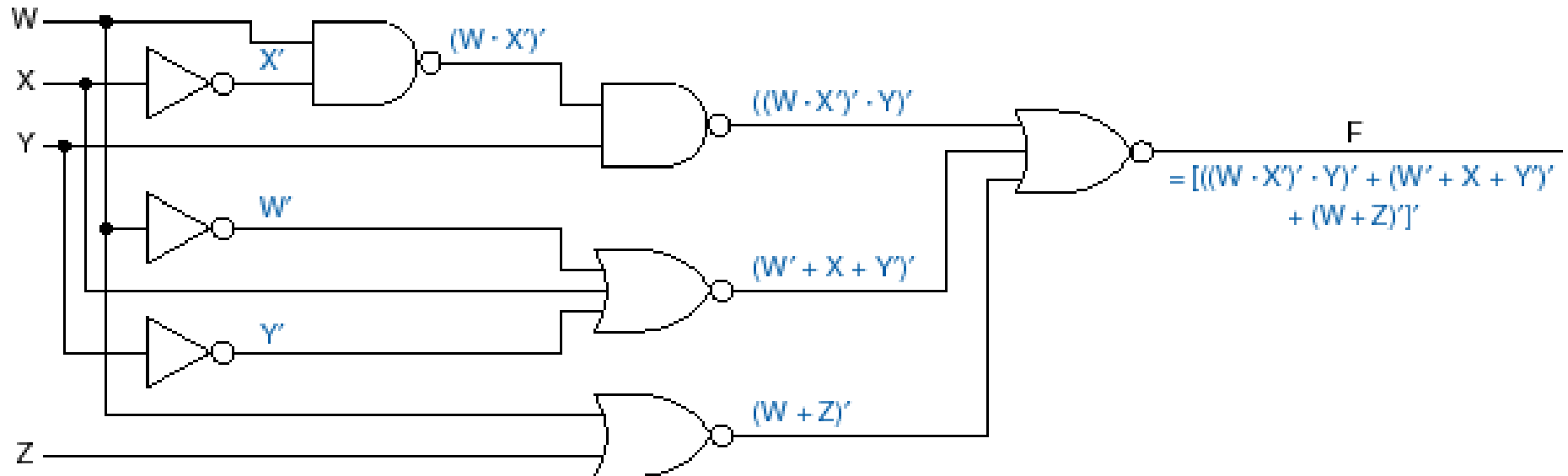


Push bubbles to obtain cancellations

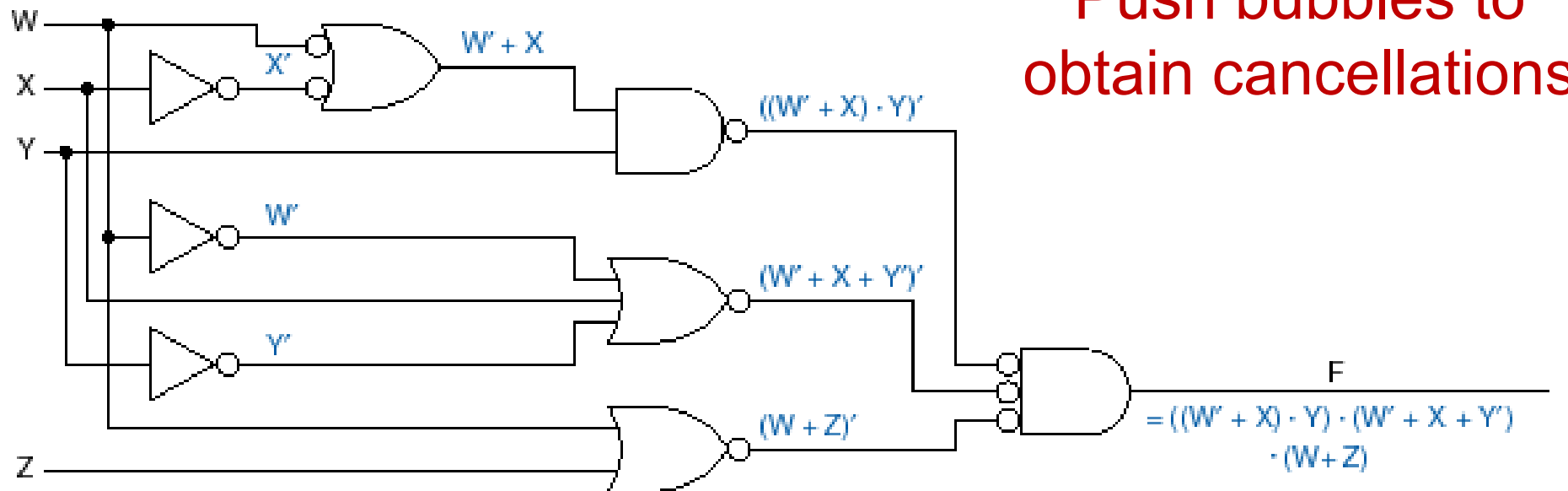


Two-Level AND-OR Implementation

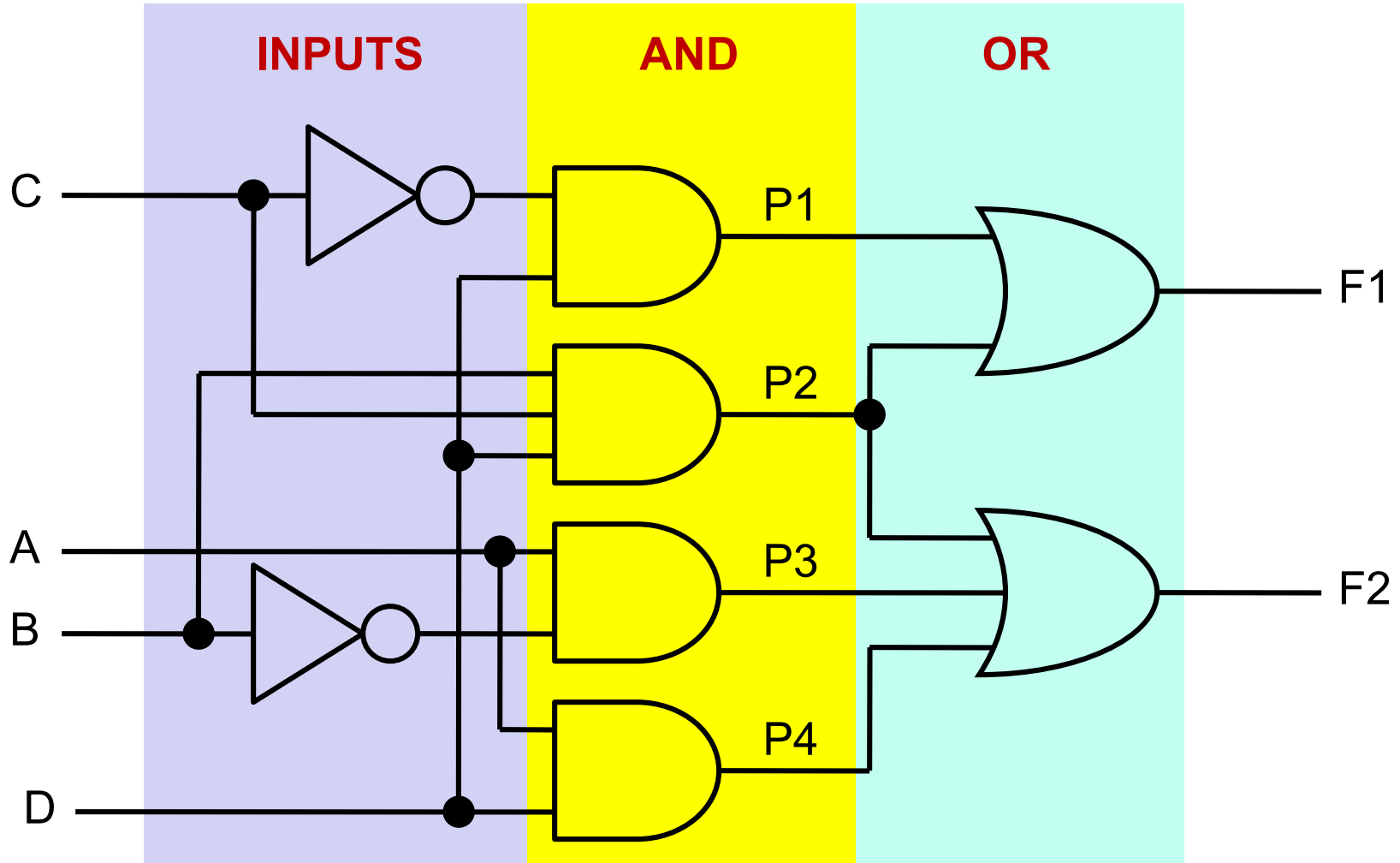- Also known as technology-independent circuit.




Slide contents are courtesy of Vishwani D. Agrawal



NAND-NAND Implementation

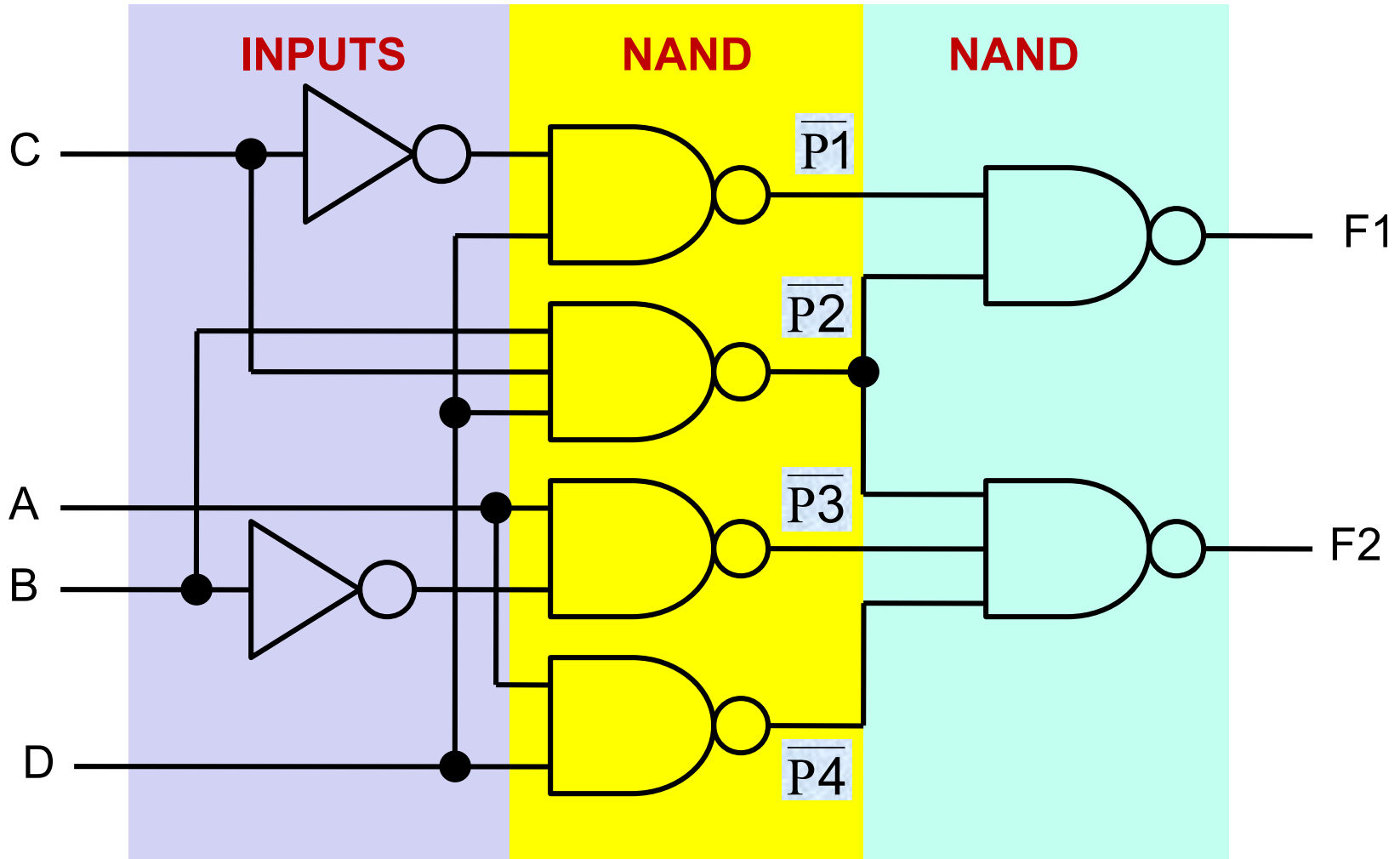

Popular Cells

 


**OR-AND-Inverter
Cell**

  


NAND3 Cell




Fan-in restrictions

 





4-Input NAND Cell

 


Fan-in
restrictions

   


AND-OR-Inverter Cell

    

Technology Mapping

 


XOR Cell

 


Procedure

- 1 Obtain SOP
- 2 Convert to two-level AND-OR circuit.
- 3 Transform to two-level NAND-NAND circuit.
- 4 Transform to two-input NAND and inverter tree network.
- 5 Perform an optimal pattern matching to obtain a minimum cost tree covering.

Example: 2 Level NAND Circuit

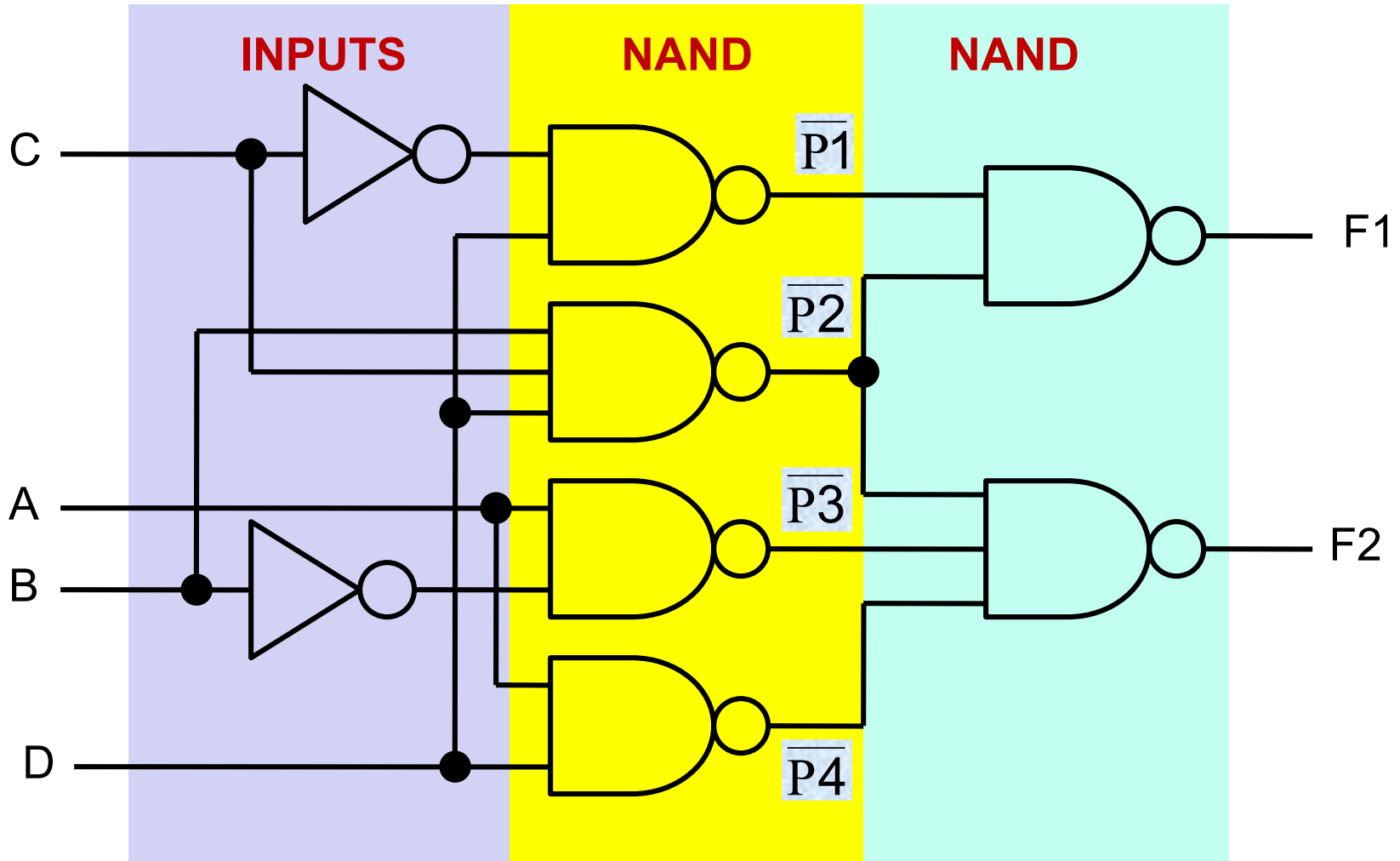


A Simple Technology Mapping



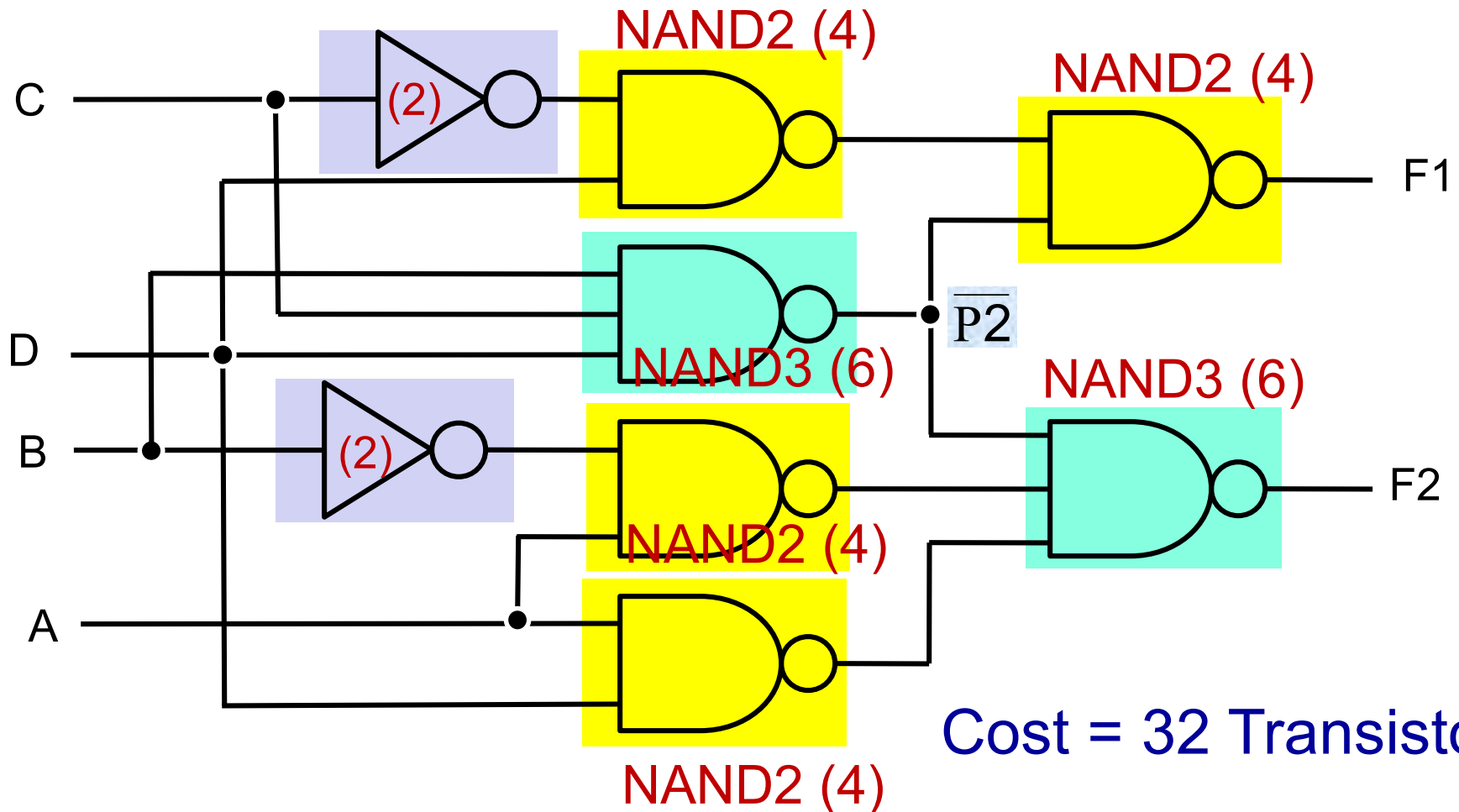


Cost = 32 Transistors

Splitting into a Forest of Trees

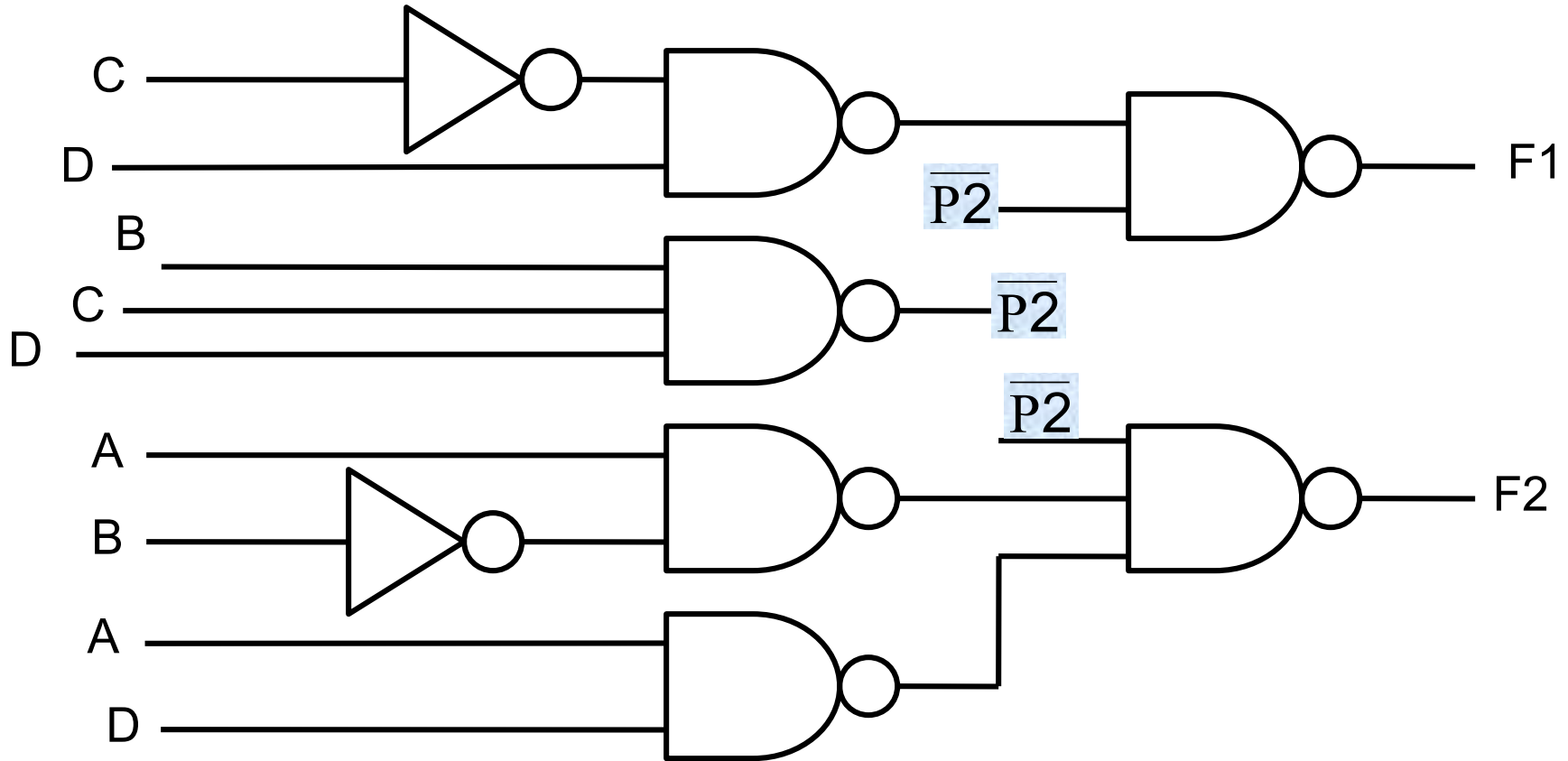


Two-Input NAND Trees

   

Factoring

 - Factoring is a technique to deal with fan-out constraints
- Can also minimize the required hardware
- Very difficult to perform in multi-level logic realization



Redundancy and duplicate logic may be unavoidable for complex fan-out issues, i.e. regenerate the same signal multiple times

Conclusion

□ Summary

- ➔ Logic Synthesis
(Definition, Procedure)
- ➔ Gate Type Conversion
(Role of DeMorgan Theorem, Bubble matching)
- ➔ Popular Cell Library
(AND-OR, AND-OR-INVERT, OR-AND, OR_AND_INVERT)
- ➔ Technology Mapping
(Splitting forest to trees, Fan-in constraints, Factoring)

□ Next Lecture

- ➔ Simplification of Switching Functions

Reading assignment: Section 2.5 in the textbook