

## CMPE 314 Midterm Exam 2


(April 19, 2011)

**Problem 1.** (15 points) - drawing & description

- What are the conditions for the cutoff, forward-active, and saturation modes for a pnp bipolar transistor? Show the structure, biasing connections.
- What are the charge carrier contributions to the emitter, collector and base currents (show directions)?


**Problem 2.** (20 points) - numerical answer

The transistor in the circuit has  $\beta=50$ ,  $V_{BE(on)}=0.7$  V and  $V_{CE(sat)}=0.2$  V. Determine  $I_B$ ,  $I_C$ , and the power dissipated in the transistor for  $V_I=3.6$  V. Is the transistor in the forward-active mode?

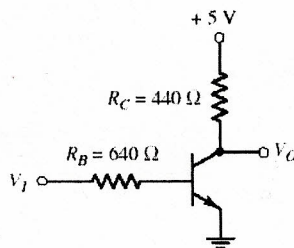


**Problem 3.** (25 points) - equations

Derive the equations for  $I_{CQ}$  and  $V_{CEQ}$ . Comment on the role of  $R_E$ . What is the maximum collector current under symmetric swing.

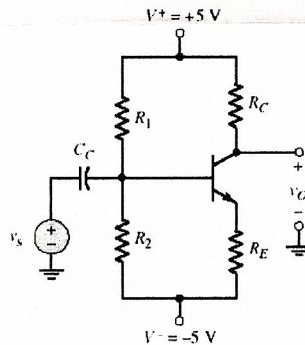

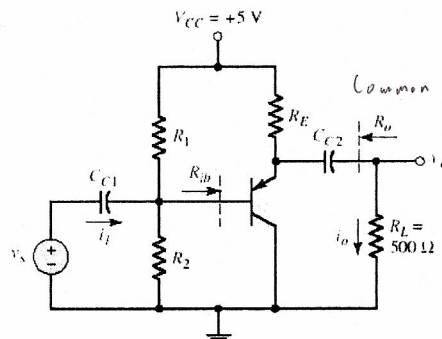**Problem 4.** (40 points) - equations

- Assume finite  $V_A$ . Draw the AC equivalent circuit, including the hybrid- $\pi$  model.
- Find the DC load-line slope and the AC load-line slope.
- Find the small-signal voltage gain and input resistance. Comment on the type of amplifier configuration and output resistance.






Common Em: HET  $A_v \gg 1$   
 $A_i \gg 1$   
 Input  $\rightarrow$  Moderate  
 Output  $\rightarrow$  Moderate  $\rightarrow$  High

# Solutions to Midterm Exam II

CMPE 314  
Spring 2011

## Problem 1

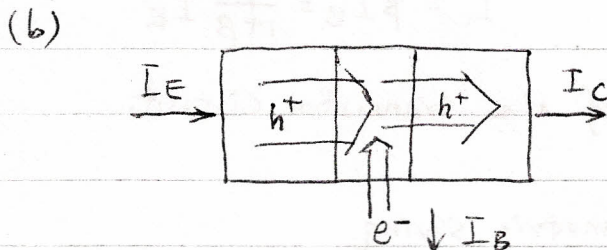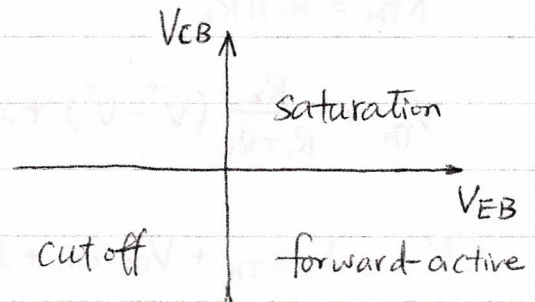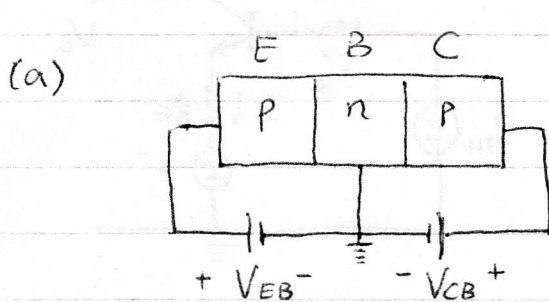

$I_E, I_C$ : Holes contribute most.  
 $I_B$ : Electrons contribute most.

## Problem 2

$$V_I = I_B R_B + V_{BE(on)} \quad (V_I = 3.6V) \rightarrow I_B = \frac{3.6 - 0.7}{640} = 4.53 \text{ mA}$$

$$\text{If } I_C = \beta I_B = 50 \times 4.53 \text{ mA} = 226.56 \text{ mA}$$

then

$$V_{CE} = V^+ - I_C R_C = 5 - 99.66 = -94.66 \text{ V} \quad \text{not possible.}$$

Transistor is in saturation




$$I_C = \frac{V^+ - V_{CE(sat)}}{R_C} = \frac{5 - 0.2}{440} = 10.91 \text{ mA}$$

$$P_{DC} = I_E V_{CE(sat)} + I_C V_{CE(sat)} = 3.01 + 3.18 = 6.19 \text{ mW}$$

# Solutions to Midterm Exam II

CMPE 314  
Spring 2011

## Problem 1

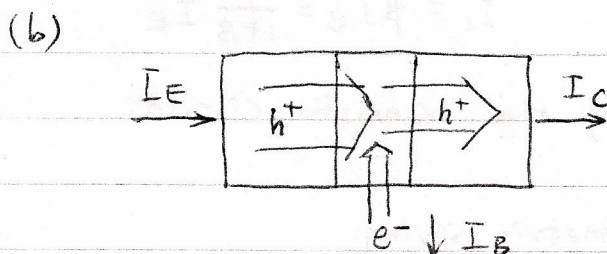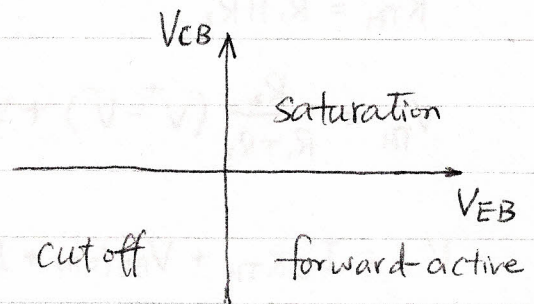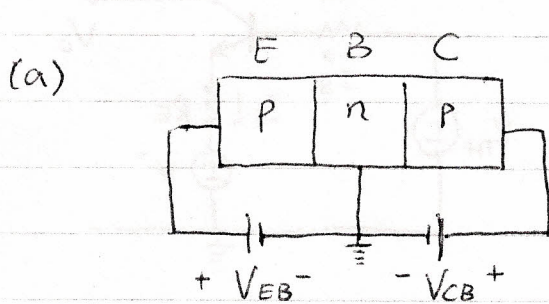

$I_E, I_C$ : Holes contribute most.

$I_B$ : Electrons contribute most.

## Problem 2

$$V_I = I_B R_B + V_{BE(on)} \quad (V_I = 3.6V) \rightarrow I_B = \frac{3.6 - 0.7}{640} = 4.53 \text{ mA}$$

If  $I_C = \beta I_B = 50 \times 4.53 \text{ mA} = 226.56 \text{ mA}$

then

$$V_{CE} = V^+ - I_C R_C = 5 - 99.66 = -94.66 \text{ V} \quad \text{not possible.}$$

Transistor is in saturation

$$I_C = \frac{V^+ - V_{CE(sat)}}{R_C} = \frac{5 - 0.2}{440} = 10.91 \text{ mA}$$

$$P_Q = I_B V_{BE(on)} + I_C V_{CE(sat)} = 3.71 + 2.182 = 5.353 \text{ mW}$$




### Problem 3

$$R_{TH} = R_1 \parallel R_2$$

$$V_{TH} = \frac{R_2}{R_1 + R_2} (V^+ - V^-) + V^-$$
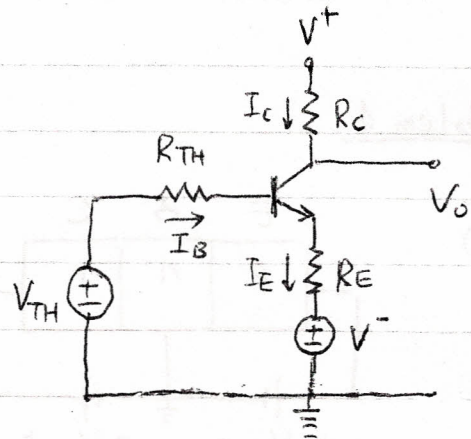
$$V_{TH} = I_B R_{TH} + V_{BE(on)} + I_E R_E + V^-$$



$$V^+ - V^- = I_C R_C + I_E R_E + V_{CE}$$


$$I_C = \beta I_B = \frac{\beta}{1 + \beta} I_E$$

$R_E$  is to stabilize the Q-pt of the transistor circuit.

$$\hat{I}_{C,max} = 2 I_{CQ} \quad \text{under symmetric swing}$$

### Problem 4

(a)

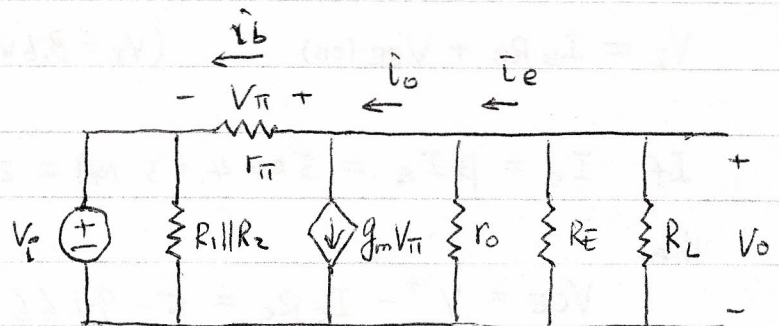

(b)

$$\text{DC: } V^+ = I_E R_E + V_{EC} = \frac{I_C}{\alpha} R_E + V_{EC}$$

$$\text{slope, DC} = - \frac{\alpha}{R_E}$$

$$\text{AC: slope, AC} = - \frac{\alpha}{r_o \parallel R_E \parallel R_L}$$

(c)

$$V_o = -I_o (r_o \parallel R_E \parallel R_L) = -(1 + \beta)(r_o \parallel R_E \parallel R_L) I_b \quad \beta I_b = g_m V_\pi$$

$$V_o = -V_\pi + V_o = -r_\pi I_b - (1 + \beta)(r_o \parallel R_E \parallel R_L) I_b$$

$$A_v = \frac{V_o}{V_\pi} = \frac{(1 + \beta)(r_o \parallel R_E \parallel R_L)}{r_\pi + (1 + \beta)(r_o \parallel R_E \parallel R_L)}$$

$$R_{i_b} = -\frac{V_\pi}{I_b} = r_\pi + (1 + \beta)(r_o \parallel R_E \parallel R_L)$$

It is an emitter-follower circuit.

$$A_v \approx +1 \quad R_o \text{ is small.}$$