

# CMPE 212

## Principles of Digital Design

### Lecture 21

## Counters Design

April 11, 2016

[www.csee.umbc.edu/~younis/CMPE212/CMPE212.htm](http://www.csee.umbc.edu/~younis/CMPE212/CMPE212.htm)



# Lecture's Overview

## □ Previous Lecture


- ➔ Register and Shift Registers  
(Design and example applications)
- ➔ Binary counters
  - Synchronous counters
  - Asynchronous counters
  - Down and up/down counters

## □ This Lecture

- ➔ Modulo-N Counters
- ➔ Synchronous and asynchronous BCD counters
- ➔ Ring counters (shift registers as counters)
- ➔ Fractional rate multipliers
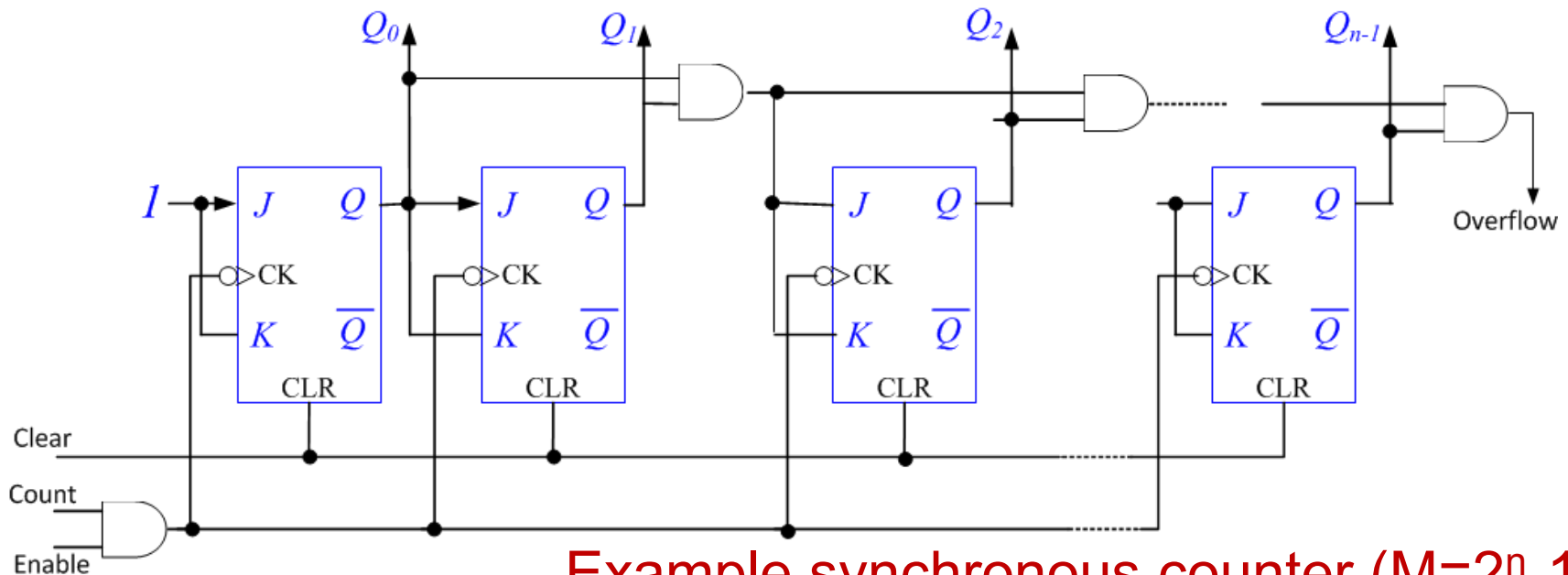
# Modulo-N Counters


- ❑ A counter circuit tracks the multiplicity of transitions is a signal up to an upper bound  $M$ , i.e., transitions between the states  $0, 1, \dots, M-1$
- ❑ A counter of an upper bound of  $M$  is called “Modulo  $M$  Counter”
- ❑ The number of flip flops,  $n$ , used in a counter imply  $M = 2^n - 1$
- ❑ In many applications a counter is needed with an upper bound  $N$  that is less than  $M$ , e.g., BCD counters
- ❑ Counters can be synchronous, i.e., operation is coordinated by a clock, and asynchronous that operates on the principle of “ready-go”.




Example synchronous counter ( $M=2^n-1$ )

# Synchronous BCD (Decade) Counter


Allows  $Q_3$  to be 1 only for 8 and 9

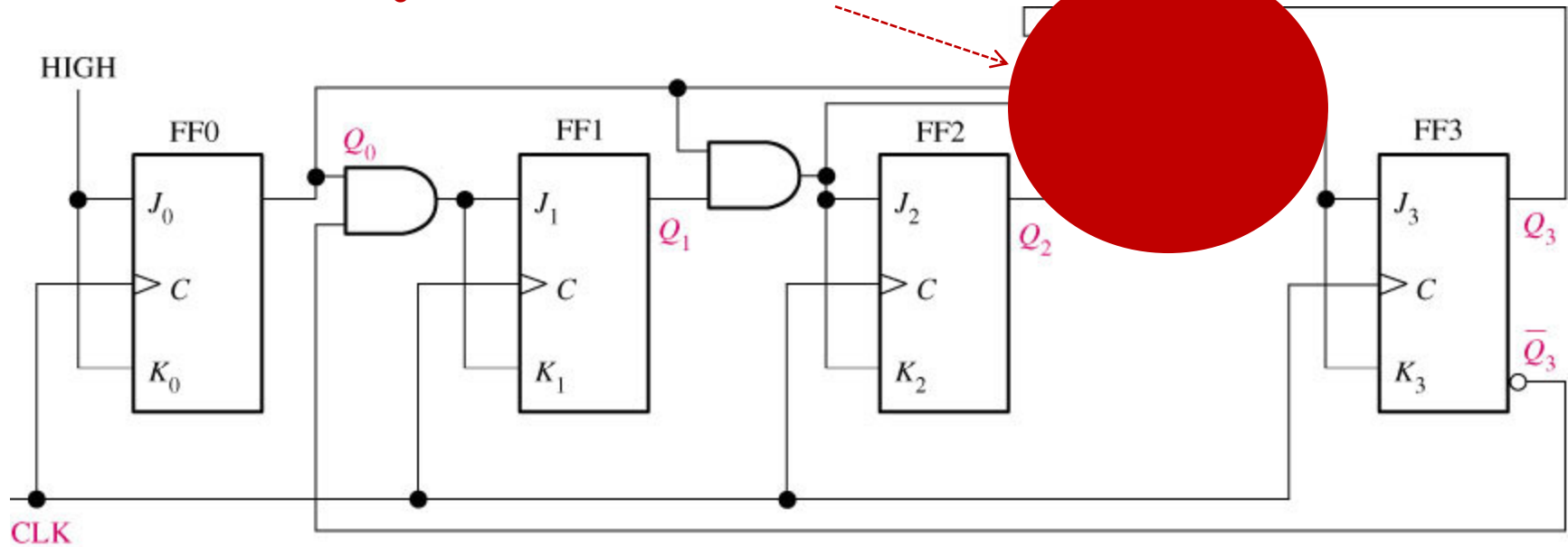

 - Idea: similar to  $2^n-1$  counters with logic that controls the next state
- Example: The 74LS160 Integrated Circuit




# Asynchronous Binary Counter

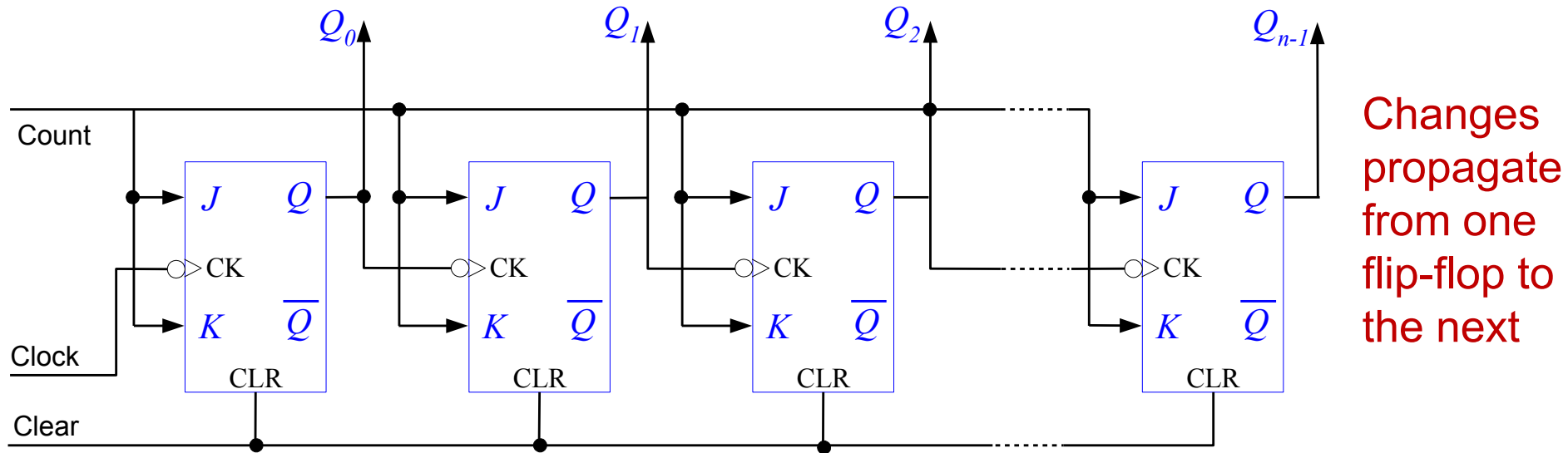


Asynchronous  $\rightarrow$  state change is not controlled by a synchronizing clock (ready-go operation)

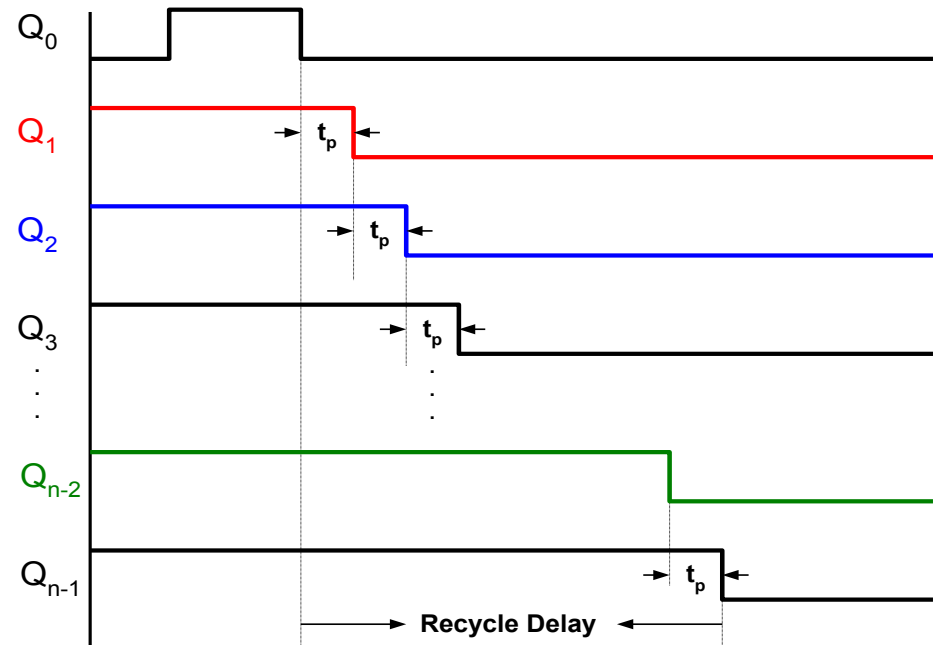- Delay is not homogenous and one has to determine the worst case delay to avoid reading the wrong output
- Recycling back to zero is not instantaneous,  $(n-1)t_p$




# Asynchronous BCD (Decade) Counter

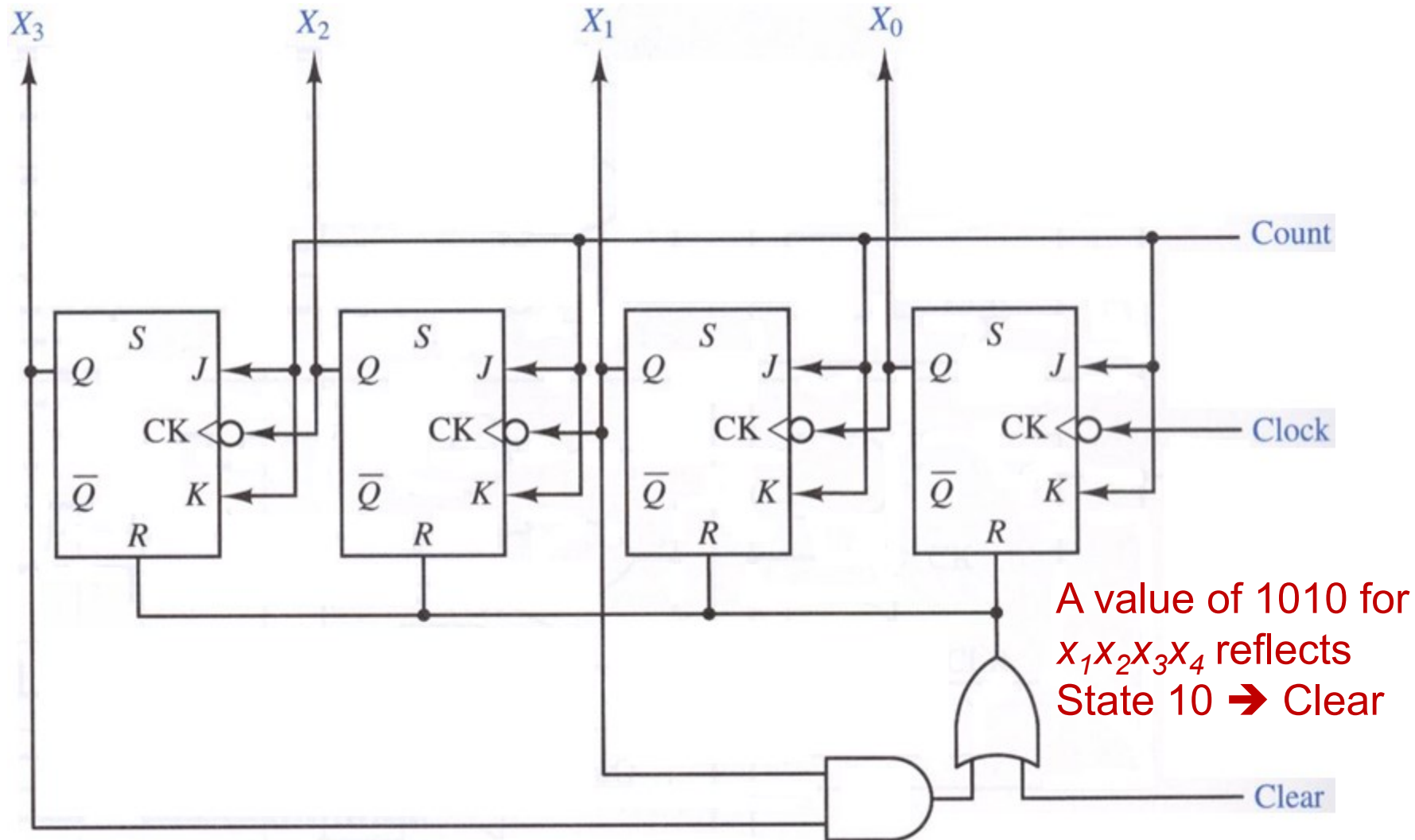


- Add combinational logic to detect number 9 (10<sup>th</sup> state) and reset the counter to zero (state 0)

# Asynchronous BCD counter

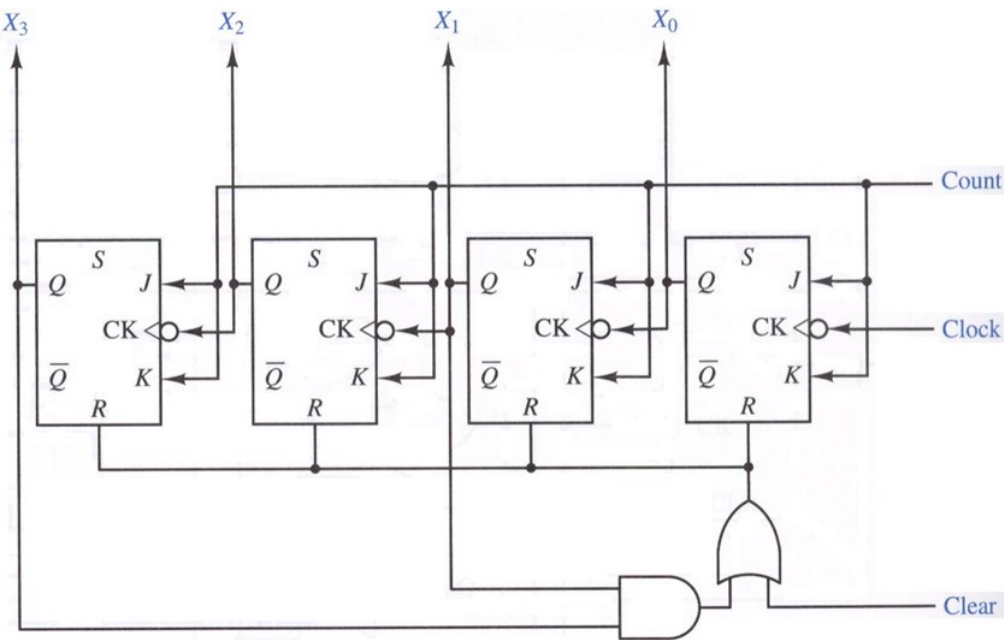


 Large circles denote steady states and small circles reflects intermediate states visited in transition



- Transition between two states may pass multiple intermediate states due to the ripple effect
- The most unstable output is in transition between 7 and 8.

# General Modulo-N Asynchronous Counter

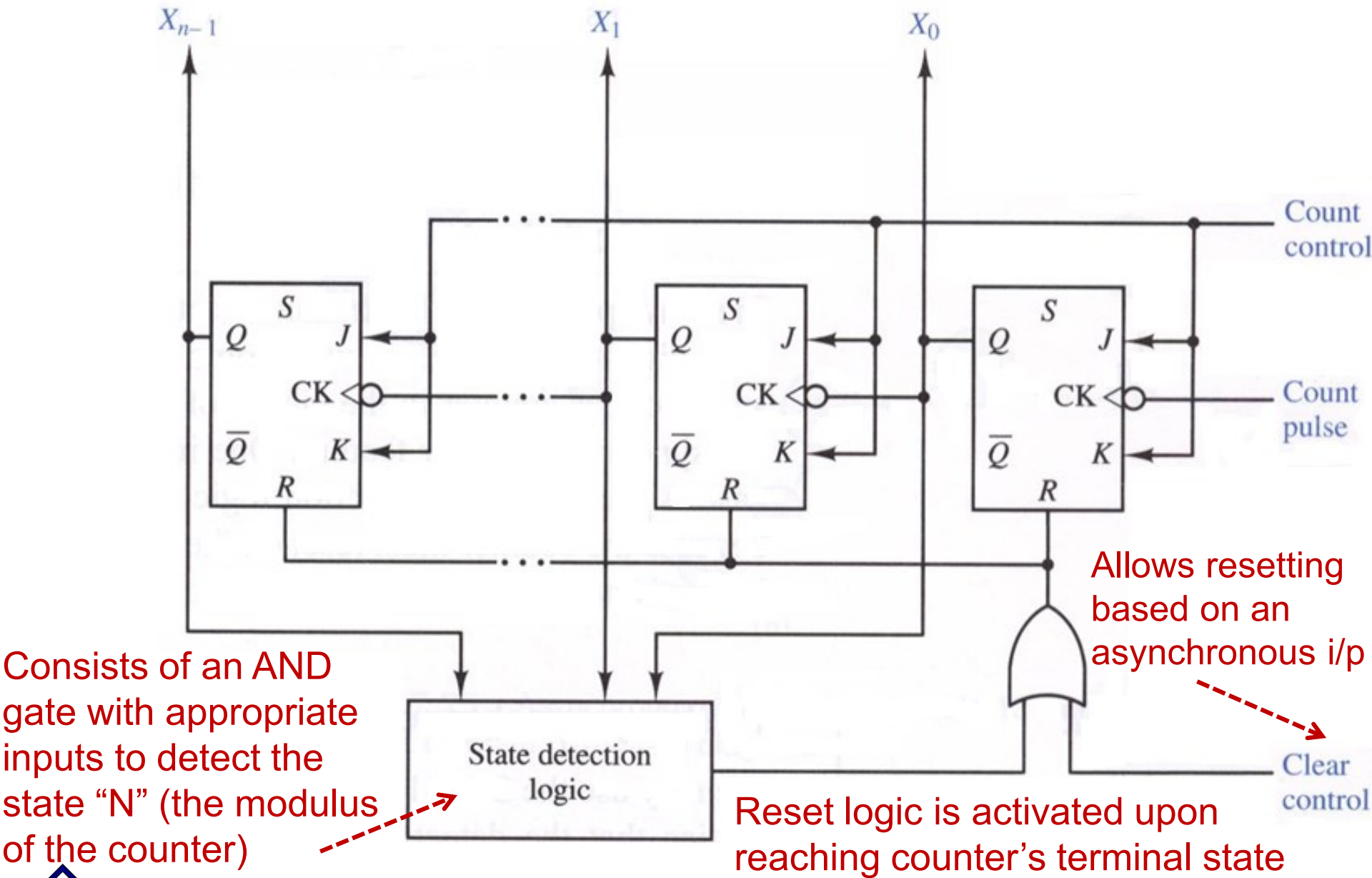





# Modulo-6 & Module-12 Counters

 Example: digital timer generator


Uses 60-hertz power line → divide by 60 (modulo 60)





# Ring Counters

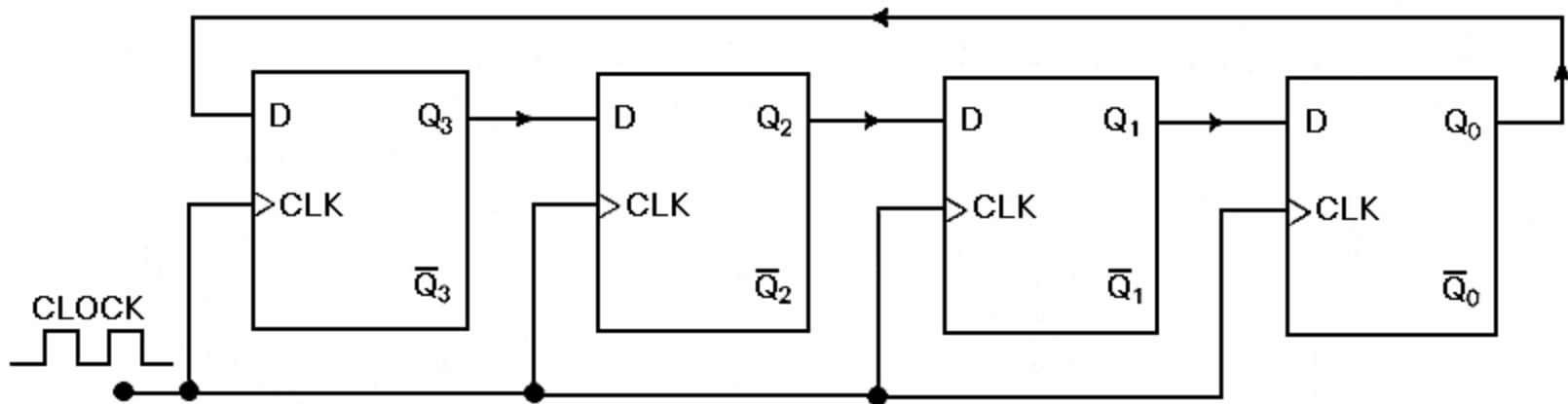

 - ❑ Shift registers can be considered as counters when the serial output is fed back as a serial input → ring
- ❑ A ring counter is a sequential circuits that has 1 flip flop per state
- ❑ If only bit is set to “1”, such “1” will circulate around the register (works like sequential decoder)




# Twisted-Ring Counters

 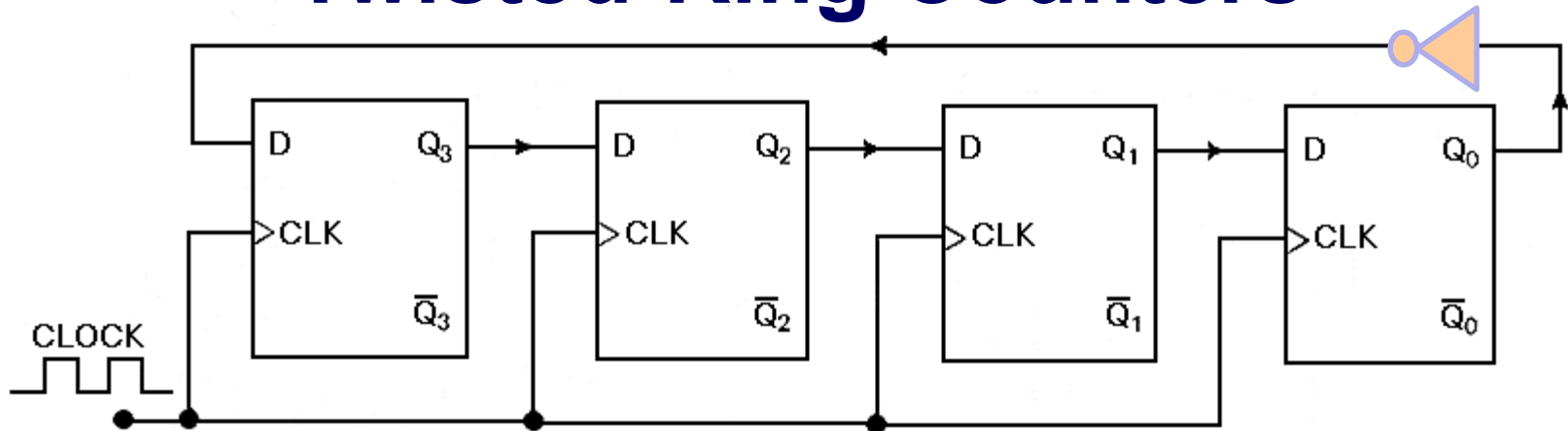


- ❑ *Twist-ring counter (or Johnson Counter):* a ring counter with an inverter in the feedback loop is called
- ❑ Number of states =  $2N$  (due to the inverter)
 
# Digital Fractional Rate Multipliers

- Transforms a stream of input clock pulses, e.g. clock, into controlled stream of output pulses



# Digital Fractional Rate Multipliers

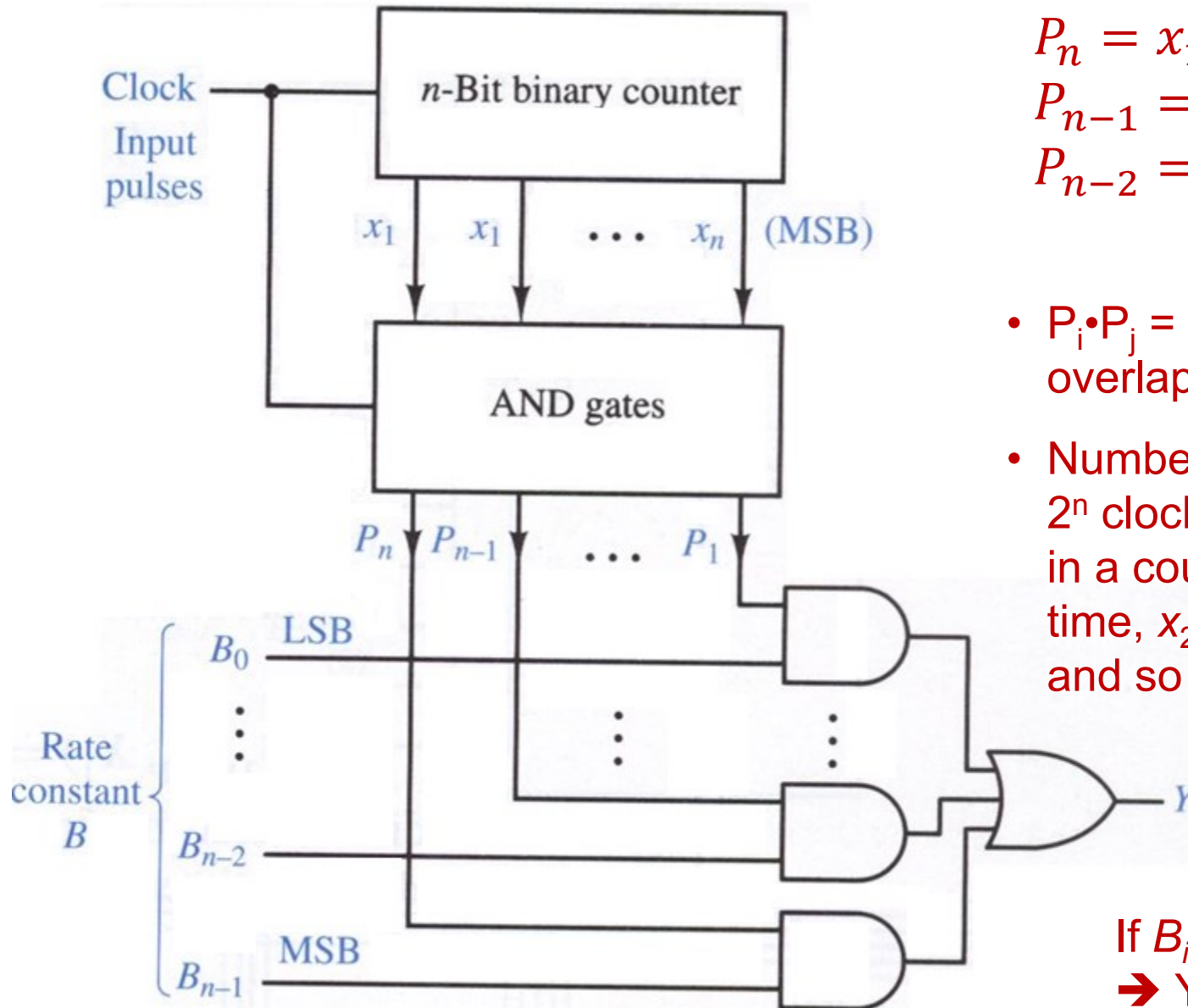

$$P_n = x_1 \cdot \text{Clock}$$

$$P_{n-1} = \overline{x_1} \cdot x_2 \cdot \text{Clock}$$

$$P_{n-2} = \overline{x_1} \cdot \overline{x_2} \cdot x_3 \cdot \text{Clock}$$

...

- $P_i \cdot P_j = 0 \rightarrow P_i$  and  $P_j$  do not overlap
- Number of pulses in  $P_i$  per  $2^n$  clock cycles is  $2^{i-1}$ , since in a counter  $x_1$  is on  $\frac{1}{2}$  of the time,  $x_2$  is on  $\frac{1}{4}$  of the time, and so

$$Y = \sum B_{i-1} \cdot P_i$$

If  $B_i = 1$  for  $i = 0, 1, \dots, n-1$   
 $\rightarrow Y = \text{clock}$

# Conclusion

## □ Summary

- ➔ Modulo-N Counters
- ➔ Synchronous and asynchronous BCD counters
- ➔ Counter resetting
- ➔ Ring counters (shift register as a counter)
- ➔ Fractional rate multipliers

## □ Next Lecture

- ➔ Synchronous sequential circuits models
- ➔ Sequential circuits analysis
- ➔ Synthesis of synchronous sequential circuits

Reading assignment: Sections 7.3 – 7.6 in the textbook