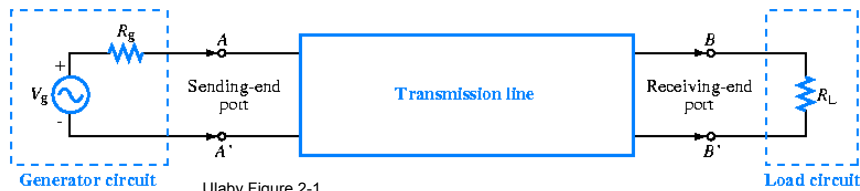


What is a transmission line?

The basic structure — a four port device that connects:

- (1) A Thévenin equivalent input or *generator circuit* with V_g and R_g , as the equivalent voltage source and resistance
- (2) A *load circuit* with a load resistance R_L as the equivalent resistance



More generally, with a-c inputs:


$$V_g \text{ and } R_g \rightarrow \tilde{V}_g \text{ and } Z_g$$

$$R_L \rightarrow Z_L$$

What is a transmission line?

The basic structure — a four port device that connects:

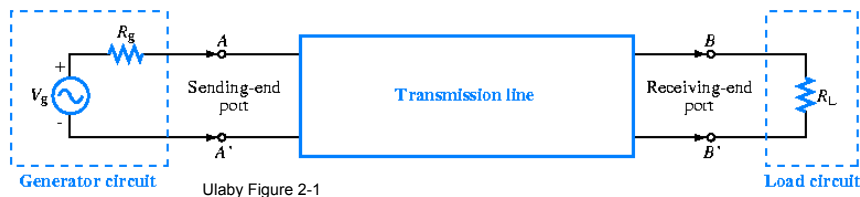
- (1) A Thévenin equivalent input or *generator circuit* with V_g and R_g , as the equivalent voltage source and resistance
- (2) A *load circuit* with a load resistance R_L as the equivalent resistance



*We take into account the finite transmission time
from A, A' to B, B'*

What is a transmission line?

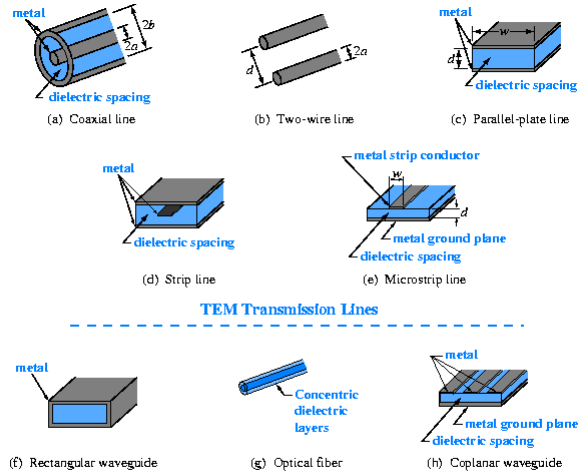There are two basic types of transmission line:



TEM Transmission Lines

Higher Order Transmission Lines


UMBC
AN HONORS
UNIVERSITY
IN MARYLAND

Ulabby
Figure 2-4

3.3

What is a transmission line?

A simple coaxial waveguide:

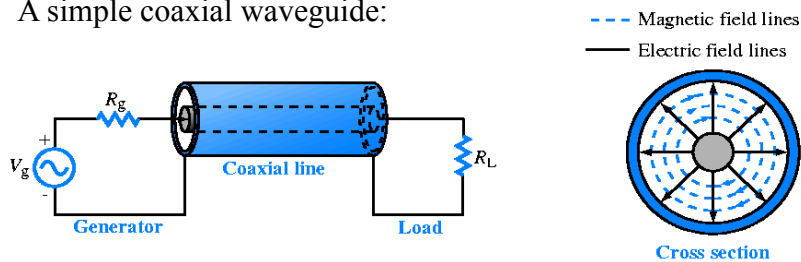

Ulabby Figure 2-5

- There is an electric field caused by charge separation from the inner and outer wires
- There is a magnetic field that is caused by the current flow, in opposite directions, along the inner and outer conductors

UMBC
AN HONORS
UNIVERSITY
IN MARYLAND

3.4

Lumped Element Model

We replace the detailed physics of the transmission line with lumped circuit parameters:


- R' : The combined resistance of both conductors (ohms/meter)
- L' : The combined inductance of both conductors (henrys/meter)
- G' : The conductance of the insulating medium between conductors (siemens/meter)
- C' : The capacitance between the two conductors (farads/meter)

- These parameters are all “per unit length.” Hence, we put primes.
- Their values are determined by the detailed physics.
- We will use this model to find a simple pair of coupled equations,

The telegrapher's equation
that describes propagation through the transmission line

Lumped Element Model

Transmission Line Model:

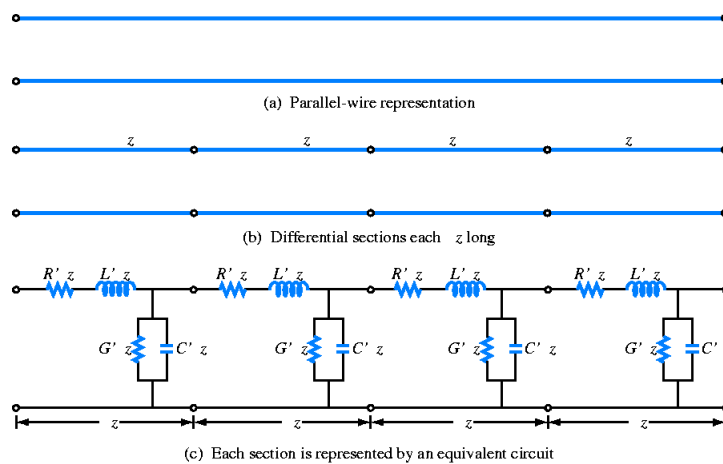

Lumped Element Model

Examples of parameter determination from the physics:

Parameter	Coaxial	Two wire	Parallel plane
R'	$\frac{R_S}{2\pi} \left(\frac{1}{a} + \frac{1}{b} \right)$	$\frac{2R_S}{\pi d}$	$\frac{2R_S}{w}$
L'	$\frac{\mu}{2\pi} \ln(b/a)$	$\frac{\mu}{\pi} \ln \left[(D/d) + \sqrt{(D/d)^2 - 1} \right]$	$\frac{\mu h}{w}$
G'	$\frac{2\pi\sigma}{\ln(b/a)}$	$\frac{\pi\sigma}{\ln \left[(D/d) + \sqrt{(D/d)^2 - 1} \right]}$	$\frac{\sigma w}{h}$
C'	$\frac{2\pi\epsilon}{\ln(b/a)}$	$\frac{\pi\epsilon}{\ln \left[(D/d) + \sqrt{(D/d)^2 - 1} \right]}$	$\frac{\epsilon w}{h}$



Ulaby Table 2-1 Slide 3.3 and the notes have definitions of a, b, d
 R_S = surface resistance = $(\pi f \mu_c / \sigma_c)^{1/2}$; μ_c, σ_c are conductor parameters
 μ, ϵ , and σ are insulator parameters

3.7

Microstrip Line

Real transmission lines can be complex

⇒ Curve fitting approximations are useful $s = w/h$
 w = strip width
 h = substrate thickness

$$\epsilon_{\text{eff}} = \frac{\epsilon_r + 1}{2} + \left(\frac{\epsilon_r - 1}{2} \right) \left(1 + \frac{10}{s} \right)^{-xy}$$



$$x = 0.56 \left(\frac{\epsilon_r - 0.9}{\epsilon_r + 3} \right)^{0.05}$$

$$y = 1 + 0.02 \ln \left(\frac{s^4 + 3.7 \times 10^{-4} s^2}{s^4 + 0.43} \right) + 0.05 \ln(1 + 1.7 \times 10^{-4} s^3)$$

$$Z_0 = \frac{60}{\sqrt{\epsilon_{\text{eff}}}} \ln \left[\frac{6 + (2\pi - 6) \exp(-t)}{s} + \left(1 + \frac{4}{s^2} \right)^{1/2} \right]; \quad t = \left(\frac{30.67}{s} \right)^{0.75}$$

$$R' = 0; \quad G' = 0$$
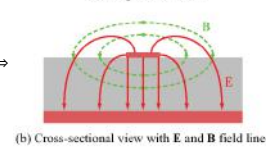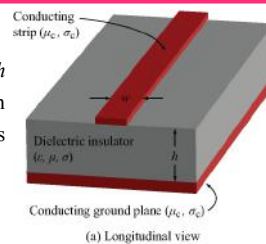
$$C' = \sqrt{\epsilon_{\text{eff}}} / Z_0 c; \quad L' = Z_0 \sqrt{\epsilon_{\text{eff}}} / c$$




(c) Microwave circuit

Ulaby and Ravaioli 2015, Figure 2-10 3.8

Transmission Line Equations

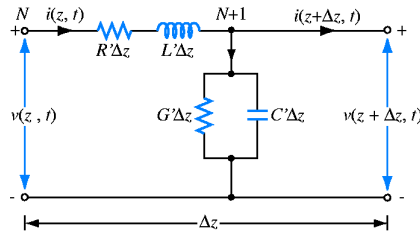Our starting point is one section of the transmission line



Note: We are taking a section that is small enough so that we can assume that the transmission through that section is instantaneous

Ulaby Figure 2-8

Kirchoff's voltage law: $v(z, t) - R' \Delta z i(z, t) - L' \Delta z \frac{\partial i(z, t)}{\partial t} - v(z + \Delta z, t) = 0$

Kirchoff's current law: (at node $N + 1$)

$$i(z, t) - G' \Delta z v(z + \Delta z, t) - C' \Delta z \frac{\partial v(z + \Delta z, t)}{\partial t} - i(z + \Delta z, t) = 0$$

Transmission Line Equations

Rearranging terms

$$-\frac{v(z + \Delta z, t) - v(z, t)}{\Delta z} = R' i(z, t) + L' \frac{\partial i(z, t)}{\partial t}$$

$$-\frac{i(z + \Delta z, t) - i(z, t)}{\Delta z} = G' v(z + \Delta z, t) + C' \frac{\partial v(z + \Delta z, t)}{\partial t}$$

Take the limit as $\Delta z \rightarrow 0$:

$$-\frac{\partial v(z, t)}{\partial z} = R' i(z, t) + L' \frac{\partial i(z, t)}{\partial t}$$

$$-\frac{\partial i(z, t)}{\partial z} = G' v(z, t) + C' \frac{\partial v(z, t)}{\partial t}$$

Telegrapher's Equations

Transmission Line Equations

Simplification

$$R' = (f\mu_c/\sigma_c)^{1/2} \rightarrow 0 \quad (\text{low frequency and high conductivity conductors})$$

$$G' \rightarrow 0 \quad (\text{low conductivity dielectric material})$$

The transmission equations become

$$-\frac{\partial v(z,t)}{\partial z} = L' \frac{\partial i(z,t)}{\partial t}, \quad -\frac{\partial i(z,t)}{\partial z} = C' \frac{\partial v(z,t)}{\partial t}$$

which imply


$$\frac{\partial^2 v(z,t)}{\partial z^2} = L'C' \frac{\partial^2 v(z,t)}{\partial t^2}, \quad \frac{\partial^2 i(z,t)}{\partial z^2} = L'C' \frac{\partial^2 i(z,t)}{\partial t^2}$$

Note: In Paul's notation: $v \rightarrow V$, $i \rightarrow I$, $L' \rightarrow l$, and $C' \rightarrow c$

$$\frac{\partial V(z,t)}{\partial z} = -l \frac{\partial I(z,t)}{\partial t}, \quad \frac{\partial I(z,t)}{\partial z} = -c \frac{\partial V(z,t)}{\partial t}$$

Transmission Line Equations

The circuit diagram also simplifies

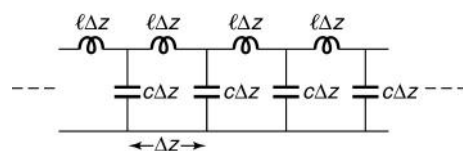


Paul Figure 6.1(c)

Note change in notation
from Ulaby

The second-order wave equations become in Paul's notation
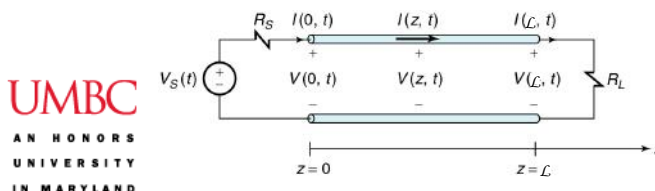
$$\frac{\partial^2 V(z,t)}{\partial z^2} = lc \frac{\partial^2 V(z,t)}{\partial t^2}, \quad \frac{\partial^2 I(z,t)}{\partial z^2} = lc \frac{\partial^2 I(z,t)}{\partial t^2}$$



V_S = source voltage
 R_S = source resistance
 R_L = load resistance
 L = total length of
transmission line

Time-Domain Evolution

The second-order voltage equation has the general solution

$$V(z,t) = \underbrace{V^+\left(t - \frac{z}{v}\right)}_{\text{forward propagation}} + \underbrace{V^-\left(t + \frac{z}{v}\right)}_{\text{backward propagation}}, \quad \text{with } v = 1/\sqrt{lc}$$

- $V^+(x)$ and $V^-(x)$ = two completely arbitrary functions
- v = the velocity of propagation

- (1) Arbitrarily shaped pulses propagate in the transmission line, both forward and backward, *without dispersing!*
- (2) The absence of dispersion is a special feature of TEM modes, which makes direct time-domain analysis possible.



Caveat: We are treating l and c as if they have no frequency dependence. This assumption is not generally true! It will often be approximately true over a limited frequency range

3.13

Time-Domain Evolution

The current is determined from the voltage

— After substitution into the transmission line equations

$$I(z,t) = \underbrace{\frac{V^+\left(t - \frac{z}{v}\right)}{Z_C}}_{\text{forward propagation}} - \underbrace{\frac{V^-\left(t + \frac{z}{v}\right)}{Z_C}}_{\text{backward propagation}}, \quad \text{with } Z_C = \sqrt{l/c}$$

- Z_C = the characteristic impedance of the transmission line
- Note that since $V(z, t)$ and $I(z, t)$ are real, so is Z_C
 - The characteristic impedance is purely resistive in this case.

We have $I^+(z,t) = V^+(z,t)/Z_C$ and $I^-(z,t) = -V^-(z,t)/Z_C$

BUT $|I(z,t)| \neq |V(z,t)|/Z_C$



There is no simple relationship between $V(z,t)$ and $I(z,t)$!

3.14

Time-Domain Evolution

Example: From Paul Quick Review Exercises 6.1 and 6.7

Question: What are the per unit length capacitance and inductance of a two-wire line whose wires have a radius of 7.5 mils and a separation of 50 mils? What is the characteristic impedance and the velocity of propagation? (These dimensions are typical for ribbon cables used to interconnect components.)

Answer: $7.5 \text{ mils} \times 2.54 \times 10^{-5} \text{ m/mil} = 1.91 \times 10^{-4} \text{ m}$,
 $50 \text{ mils} = 1.27 \times 10^{-3} \text{ m}$. $(D/d) = 50.0/15.0 = 3.33$, $[(D/d)^2 - 1] = 3.18$,
 $\ln(3.33 + 3.18) = 1.87$. $L' = (\mu_0 / \pi) \times 1.87 = 4 \times 10^{-7} \text{ H/m} \times 1.87 =$
 $7.46 \times 10^{-7} \text{ H/m}$. $C' = (\pi \epsilon_0 / 1.87) = (\pi / 1.87) \times 8.85 \times 10^{-12} \text{ F/m}$
 $= 1.49 \times 10^{-11} \text{ F/m}$. $Z_0 = (L' / C')^{1/2} = 224 \text{ ohms}$. $u_p = 1 / (7.46 \times 10^{-7} \text{ H/m} \times$
 $1.49 \times 10^{-11} \text{ F/m})^{1/2} = 3.00 \times 10^8 \text{ m/s}$. The velocity equals the speed of light in the vacuum.



NOTE: Paul uses a different notation for all quantities

3.15

Time-Domain Evolution

We now consider the behavior at the load

$$V(\mathcal{L}, t) = V^+(t - T) + V^-(t + T), \quad T = \mathcal{L}/v$$


= one-way time delay

$$I(\mathcal{L}, t) = \frac{V^+(t - T)}{Z_C} - \frac{V^-(t + T)}{Z_C}$$

From Ohm's Law: $V(\mathcal{L}, t) / I(\mathcal{L}, t) = R_L$

From the telegrapher's equations: $V^+(t - T) / I^+(t - T) = Z_C$

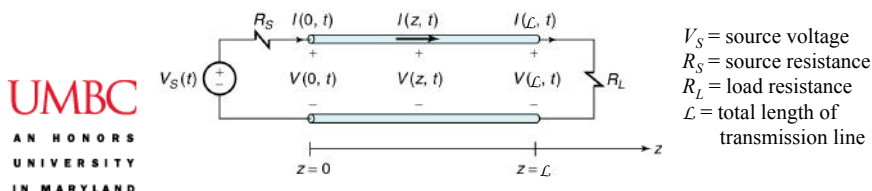Unless $R_L = Z_C$, there must be reflected waves!



3.16

Time-Domain Evolution

We now consider the behavior at the load

$$V(\mathcal{L}, t) = V^+(t - T) + V^-(t + T), \quad T = \mathcal{L}/v = \text{one-way time delay}$$

$$I(\mathcal{L}, t) = \frac{V^+(t - T)}{Z_C} - \frac{V^-(t + T)}{Z_C}$$

From Ohm's Law: $V(\mathcal{L}, t) / I(\mathcal{L}, t) = R_L$

From the telegrapher's equations: $V^+(t - T) / I^+(t - T) = Z_C$

Unless $R_L = Z_C$, there must be reflected waves!

When $R_L = Z_C$, we say that the line is *impedance matched*



The concept of impedance matching is one of the most important in this course.

Impedance matching is never perfect, giving rise to transients.

3.17

Time-Domain Evolution

Behavior at the load: Reflection Coefficient Γ_L

$$\Gamma_L = V^-(t + T) / V^+(t - T)$$

which implies

$$V(\mathcal{L}, t) = V^+(t - T)[1 + \Gamma_L], \quad I(\mathcal{L}, t) = \frac{V^+(t - T)}{Z_C}[1 - \Gamma_L]$$

from which

$$\frac{V(\mathcal{L}, t)}{I(\mathcal{L}, t)} = R_L = Z_C \frac{1 + \Gamma_L}{1 - \Gamma_L} \quad \text{and} \quad \Gamma_L = \frac{R_L - Z_C}{R_L + Z_C}$$


- Schematically, we may understand the behavior at the load as a combination of a forward-propagating wave and a backward-going wave that is a reflected copy of the first wave, multiplied by Γ_L .



3.18

Time-Domain Evolution

Behavior at the load

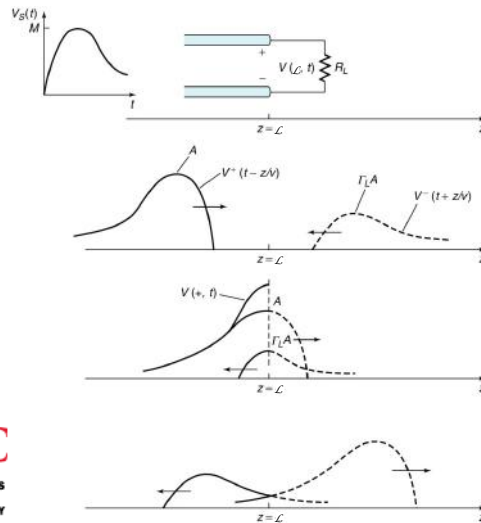

Paul Figure 6-9

Illustration of the reflection of voltage waves at the load of a transmission line.

Time-Domain Evolution

Behavior at the source $[0 < t < 2T]$


$$V_S(t) = 0 \text{ when } t < 0 \Rightarrow V^-(0,t) = 0 \text{ when } 0 < t < 2T$$

From Kirchhoff's voltage law:


$$V_S(t) = R_S I^+(t) + V^+(t) = [(R_S / Z_C) + 1] V^+(t)$$

$$V(0,t) = V^+(t) = \frac{Z_C}{R_S + Z_C} V_S(t)$$

$$I(0,t) = \frac{V_S(t)}{R_S + Z_C}$$

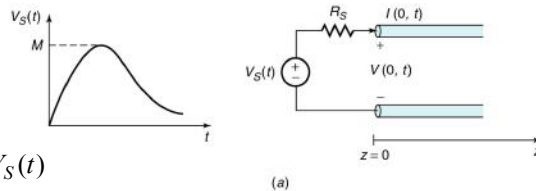

(a)

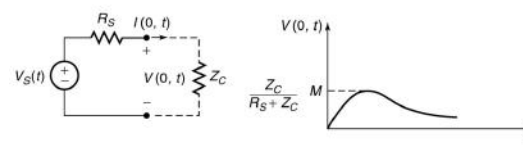

(b) $t < 2\frac{L}{v}$

Paul Figure 6-10

Time-Domain Evolution

Time evolution

$$V(0,t) = \frac{Z_C}{R_S + Z_C} \left[V_S(t) + (1 + \Gamma_S) \Gamma_L V_S(t - 2T) \right. \\ \left. + (1 + \Gamma_S)(\Gamma_S \Gamma_L) \Gamma_L V_S(t - 4T) + (1 + \Gamma_S)(\Gamma_S \Gamma_L)^2 \Gamma_L V_S(t - 6T) + \dots \right]$$

$$V(L,t) = \frac{Z_C}{R_S + Z_C} \left[(1 + \Gamma_L) V_S(t - T) + (1 + \Gamma_L)(\Gamma_S \Gamma_L) V_S(t - 3T) \right. \\ \left. + (1 + \Gamma_L)(\Gamma_S \Gamma_L)^2 V_S(t - 5T) + (1 + \Gamma_L)(\Gamma_S \Gamma_L)^3 V_S(t - 7T) + \dots \right]$$

NOTE: This series continues forever **IF**
we define $V_S(t) = 0$ when $t < 0$



3.23

Time-Domain Evolution

Geometric series:

$$1 + x + x^2 + \dots + x^m = \sum_{i=0}^m x^i = \frac{1 - x^{m+1}}{1 - x}$$

Summing all the bounces, we find

$$V(0,t) = \frac{V_S Z_C}{R_S + Z_C} \left[\frac{1 - (\Gamma_S \Gamma_L)^{m_S+1} + \Gamma_L [1 - (\Gamma_S \Gamma_L)^{m_S}]}{1 - \Gamma_S \Gamma_L} \right]$$

$$I(0,t) = \frac{V_S}{R_S + Z_C} \left[\frac{1 - (\Gamma_S \Gamma_L)^{m_S+1} - \Gamma_L [1 - (\Gamma_S \Gamma_L)^{m_S}]}{1 - \Gamma_S \Gamma_L} \right]$$

$$V(L,t) = \frac{V_S Z_C}{R_S + Z_C} \left[\frac{(1 + \Gamma_L) [1 - (\Gamma_S \Gamma_L)^{m_L}]}{1 - \Gamma_S \Gamma_L} \right]$$

$$I(L,t) = \frac{V_S}{R_S + Z_C} \left[\frac{(1 - \Gamma_L) [1 - (\Gamma_S \Gamma_L)^{m_L}]}{1 - \Gamma_S \Gamma_L} \right]$$



$$m_S = \lfloor t / 2T \rfloor, \quad m_L = \lfloor (t + T) / 2T \rfloor$$

3.24

Time-Domain Evolution

In Ulaby et al.'s notation, we find

$$V(0,t) = \frac{V_g Z_0}{R_g + Z_0} \left[\frac{1 - (\Gamma_g \Gamma_L)^{m_g+1} + \Gamma_L [1 - (\Gamma_g \Gamma_L)^{m_g}]}{1 - \Gamma_g \Gamma_L} \right]$$

$$I(0,t) = \frac{V_g}{R_g + Z_0} \left[\frac{1 - (\Gamma_g \Gamma_L)^{m_g+1} - \Gamma_L [1 - (\Gamma_g \Gamma_L)^{m_g}]}{1 - \Gamma_g \Gamma_L} \right]$$

$$V(l,t) = \frac{V_g Z_0}{R_g + Z_0} \left[\frac{(1 + \Gamma_L) [1 - (\Gamma_g \Gamma_L)^{m_L}]}{1 - \Gamma_g \Gamma_L} \right]$$

$$I(l,t) = \frac{V_g}{R_g + Z_0} \left[\frac{(1 - \Gamma_L) [1 - (\Gamma_g \Gamma_L)^{m_L}]}{1 - \Gamma_g \Gamma_L} \right]$$

$$m_g = \lfloor t / 2T \rfloor, \quad m_L = \lfloor (t + T) / 2T \rfloor$$

Time-Domain Evolution

When m_S and m_L become infinite, these become:

$$V(0,t) = \frac{V_S Z_C}{R_S + Z_C} \left[\frac{1 + \Gamma_L}{1 - \Gamma_S \Gamma_L} \right], \quad I(0,t) = \frac{V_S}{R_S + Z_C} \left[\frac{1 - \Gamma_L}{1 - \Gamma_S \Gamma_L} \right]$$

$$V(\mathcal{L},t) = \frac{V_S Z_C}{R_S + Z_C} \left[\frac{1 + \Gamma_L}{1 - \Gamma_S \Gamma_L} \right], \quad I(\mathcal{L},t) = \frac{V_S}{R_S + Z_C} \left[\frac{1 - \Gamma_L}{1 - \Gamma_S \Gamma_L} \right]$$

which is the same at both the source and the load

In Ulaby et al.'s notation, we have

$$V(0,t) = V(l,t) = \frac{V_g Z_0}{R_g + Z_0} \left[\frac{1 + \Gamma_L}{1 - \Gamma_g \Gamma_L} \right],$$

$$I(0,t) = I(l,t) = \frac{V_g}{R_g + Z_0} \left[\frac{1 - \Gamma_L}{1 - \Gamma_g \Gamma_L} \right]$$

Time-Domain Evolution

Example (Paul 6.1):


Question: A thirty volt battery is switched onto a line of length 400 m. The line has a characteristic impedance of 50Ω and a propagation velocity of 2.00×10^8 m/s. The source resistance is zero, and the load resistance is 100Ω . What is the current at the input and the voltage at the load as a function of time?

Answer: System Parameters:

$$\Gamma_S = \frac{0 - 50}{0 + 50} = -1$$

$$\Gamma_L = \frac{100 - 50}{100 + 50} = \frac{1}{3}$$

$$T = \frac{L}{v} = 2 \mu s$$

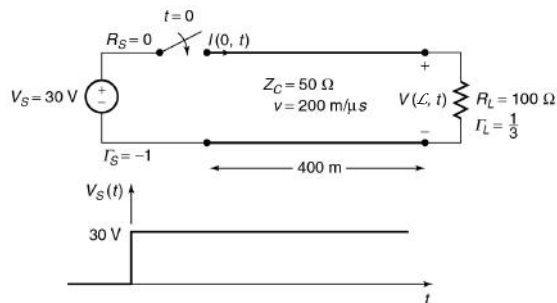

Paul Figure 6-12(a)

3.27

UMBC
AN HONORS
UNIVERSITY
IN MARYLAND

Time-Domain Evolution


Example (Paul 6.1):

Answer (continued): For $t = (0 \mu s, 2 \mu s)$, $V(L, t) = 0$. For $t = (2 \mu s, 6 \mu s)$, $V(L, t) = (\text{incoming voltage}) + (\text{reflected voltage}) = 30 \text{ V} + (1/3) \times 30 \text{ V} = 40 \text{ V}$. Since the reflected voltage is 10 V, we find that for $t = (4 \mu s, 8 \mu s)$, $V^+(t) = 30 \text{ V} - 10 \text{ V} = 20 \text{ V}$, and, for $t = (6 \mu s, 10 \mu s)$, $V(L, t) = (4/3) \times 20 \text{ V} = 26.67 \text{ V}$. And so on...

For $t = (0 \mu s, 4 \mu s)$, $I(0, t) = 30 \text{ V} / 50 \Omega = 0.6 \text{ A}$.

For $t = (4 \mu s, 8 \mu s)$,
 $I(0, t) = (20 \text{ V} - 10 \text{ V}) / 50 \Omega = 0.2 \text{ A}$.

And so on...

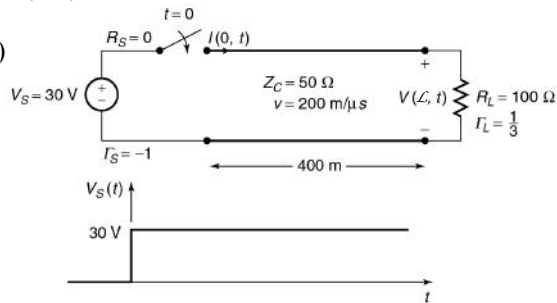

Paul Figure 6-12(a)


3.28

UMBC
AN HONORS
UNIVERSITY
IN MARYLAND

Time-Domain Evolution

Example (Paul 6.1):

MATLAB OUTPUT

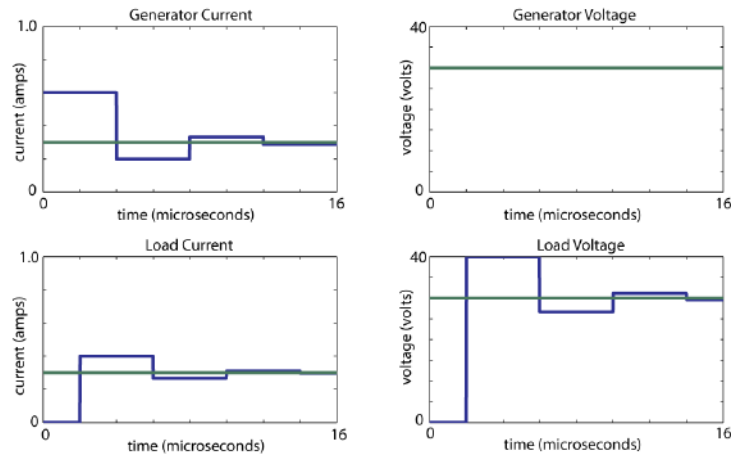

UMBC
AN HONORS
UNIVERSITY
IN MARYLAND


Key Point: Without good impedance matching, transients can exist for a long time, leading to poor system performance!

3.29

Time-Domain Evolution

Example (Paul 6.1):

MATLAB OUTPUT

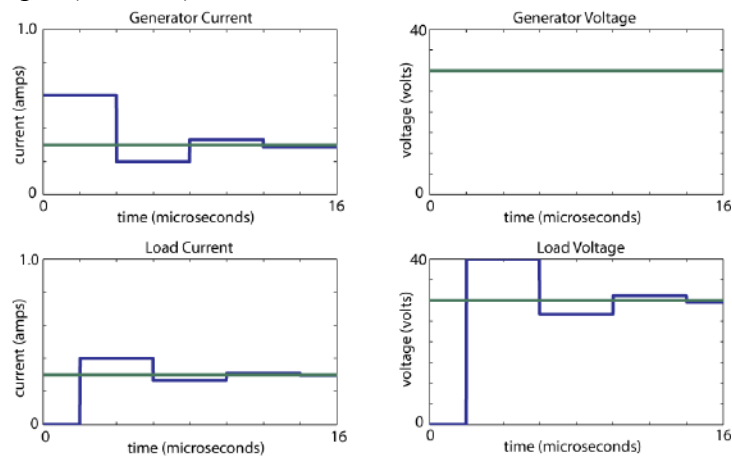


UMBC
AN HONORS
UNIVERSITY
IN MARYLAND

But transients can be useful for TDR in a matched line

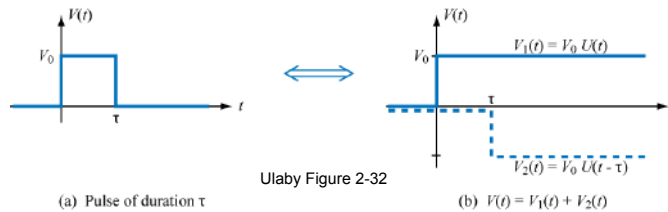3.30

Time-Domain Evolution

When a pulse is present, superpose two step functions



Time-Domain Evolution

Example (Paul 6.2):


Question: Consider a line of length 0.2 m. The source voltage is a pulse of 20 V amplitude and 1 ns duration t_D . The line has a characteristic impedance of 100 Ω and a velocity of propagation of 2×10^8 m/s. The source resistance is 300 Ω and the load is open-circuited. Find the source and generator currents and voltages.

Answer: System Parameters:

$$\Gamma_S = \frac{300 - 100}{300 + 100} = \frac{1}{2}$$

$$\Gamma_L = \frac{\infty - 100}{\infty + 100} = 1$$
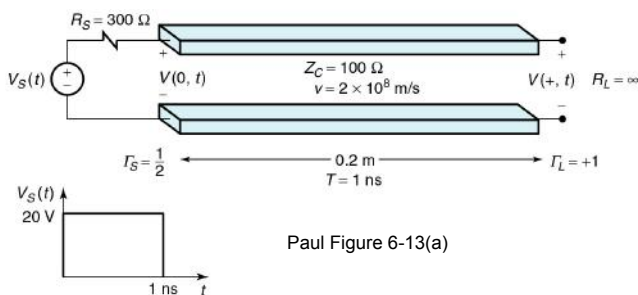
$$T = \frac{\mathcal{L}}{v} = 1 \text{ ns}; \quad t_D = 1 \text{ ns}$$



Time-Domain Evolution

Example (Paul 6.2):

Answer (continued): We use the formulae on slide 3.24, but we must subtract a negative contribution for the back end of the pulse

$$\begin{aligned}
 V(0,t) &= \frac{V_S Z_C}{R_S + Z_C} \left[\frac{1 - (\Gamma_S \Gamma_L)^{m_{S1}+1} + \Gamma_L [1 - (\Gamma_S \Gamma_L)^{m_{S1}}]}{1 - \Gamma_S \Gamma_L} - \frac{1 - (\Gamma_S \Gamma_L)^{m_{S2}+1} + \Gamma_L [1 - (\Gamma_S \Gamma_L)^{m_{S2}}]}{1 - \Gamma_S \Gamma_L} \right] \\
 I(0,t) &= \frac{V_S}{R_S + Z_C} \left[\frac{1 - (\Gamma_S \Gamma_L)^{m_{S1}+1} - \Gamma_L [1 - (\Gamma_S \Gamma_L)^{m_{S1}}]}{1 - \Gamma_S \Gamma_L} - \frac{1 - (\Gamma_S \Gamma_L)^{m_{S2}+1} - \Gamma_L [1 - (\Gamma_S \Gamma_L)^{m_{S2}}]}{1 - \Gamma_S \Gamma_L} \right] \\
 V(\mathcal{L},t) &= \frac{V_S Z_C}{R_S + Z_C} \left[\frac{(1 + \Gamma_L)[1 - (\Gamma_S \Gamma_L)^{m_{L1}}]}{1 - \Gamma_S \Gamma_L} - \frac{(1 + \Gamma_L)[1 - (\Gamma_S \Gamma_L)^{m_{L2}}]}{1 - \Gamma_S \Gamma_L} \right] \\
 I(\mathcal{L},t) &= \frac{V_S}{R_S + Z_C} \left[\frac{(1 - \Gamma_L)[1 - (\Gamma_S \Gamma_L)^{m_{L1}}]}{1 - \Gamma_S \Gamma_L} - \frac{(1 - \Gamma_L)[1 - (\Gamma_S \Gamma_L)^{m_{L2}}]}{1 - \Gamma_S \Gamma_L} \right]
 \end{aligned}$$



$$\begin{aligned}
 m_{g1} &= \lfloor t / 2T \rfloor, & m_{g2} &= \lfloor (t - t_D) / 2T \rfloor, \\
 m_{L1} &= \lfloor (t + T) / 2T \rfloor, & m_{L2} &= \lfloor (t + T - t_D) / 2T \rfloor, \quad t > t_D
 \end{aligned}$$

You only subtract for $t > t_D$

3.33

Time-Domain Evolution

Example (Paul 6.2):

Answer (continued): In Ulaby's notation, this is

$$\begin{aligned}
 V(0,t) &= \frac{V_g Z_0}{R_g + Z_0} \left[\frac{1 - (\Gamma_g \Gamma_L)^{m_{g1}+1} + \Gamma_L [1 - (\Gamma_g \Gamma_L)^{m_{g1}}]}{1 - \Gamma_g \Gamma_L} - \frac{1 - (\Gamma_g \Gamma_L)^{m_{g2}+1} + \Gamma_L [1 - (\Gamma_g \Gamma_L)^{m_{g2}}]}{1 - \Gamma_g \Gamma_L} \right] \\
 I(0,t) &= \frac{V_g}{R_g + Z_0} \left[\frac{1 - (\Gamma_g \Gamma_L)^{m_{g1}+1} - \Gamma_L [1 - (\Gamma_g \Gamma_L)^{m_{g1}}]}{1 - \Gamma_g \Gamma_L} - \frac{1 - (\Gamma_g \Gamma_L)^{m_{g2}+1} - \Gamma_L [1 - (\Gamma_g \Gamma_L)^{m_{g2}}]}{1 - \Gamma_g \Gamma_L} \right] \\
 V(l,t) &= \frac{V_g Z_0}{R_g + Z_0} \left[\frac{(1 + \Gamma_L)[1 - (\Gamma_g \Gamma_L)^{m_{L1}}]}{1 - \Gamma_g \Gamma_L} - \frac{(1 + \Gamma_L)[1 - (\Gamma_g \Gamma_L)^{m_{L2}}]}{1 - \Gamma_g \Gamma_L} \right] \\
 I(l,t) &= \frac{V_g}{R_g + Z_0} \left[\frac{(1 - \Gamma_L)[1 - (\Gamma_g \Gamma_L)^{m_{L1}}]}{1 - \Gamma_g \Gamma_L} - \frac{(1 - \Gamma_L)[1 - (\Gamma_g \Gamma_L)^{m_{L2}}]}{1 - \Gamma_g \Gamma_L} \right]
 \end{aligned}$$



$$\begin{aligned}
 m_{S1} &= \lfloor t / 2T \rfloor, & m_{S2} &= \lfloor (t - t_D) / 2T \rfloor, \\
 m_{L1} &= \lfloor (t + T) / 2T \rfloor, & m_{L2} &= \lfloor (t + T - t_D) / 2T \rfloor, \quad t > t_D
 \end{aligned}$$


You only subtract for $t > t_D$

3.34

Time-Domain Evolution

Example (Paul 6.2):

MATLAB OUTPUT

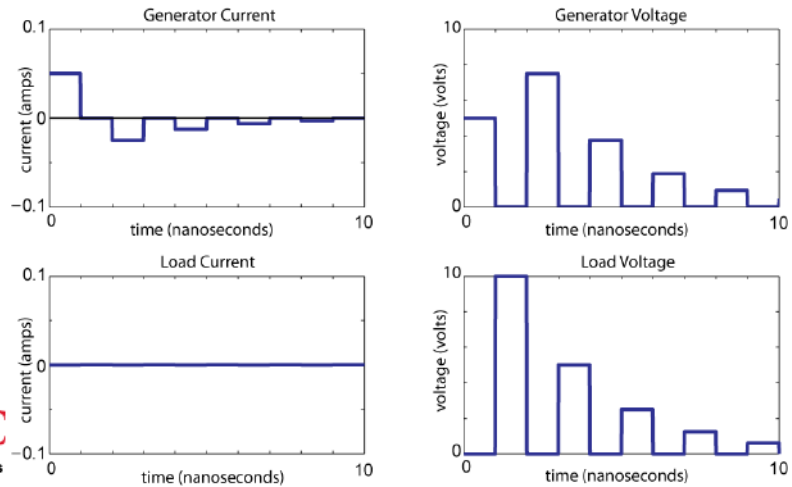

UMBC
AN HONORS
UNIVERSITY
IN MARYLAND

3.35

Assignment

Problem Set 2: Some notes

- There are 6 problems. Many of the answers to these problems have been provided by either Ulaby and Ravaoli or by me. YOU MUST SHOW YOUR WORK TO GET FULL CREDIT!
- Watch significant figures. Report the number that I ask for.
- These problems are difficult. GET STARTED EARLY!

UMBC
AN HONORS
UNIVERSITY
IN MARYLAND

3.36