

CMPE 212

Spring, 2016

Project 2 Report

Sabbir Ahmed
Teaching assistant:
Ahmed Shahin


1. Project description:

The goal of this project is to design and implement a finite state machine through combinational and sequential circuits. With one 1-bit input corresponding to 25 ¢ or 10 ¢, the machine is to behave similarly to a vending machine dispensing an output after an amount of 70 ¢ or higher has been accumulated, except when the excess is either 5 ¢ or 15 ¢, in which case a change of 5 ¢ will also be outputted leaving the remaining as credit for the next simulation.

2. Process:

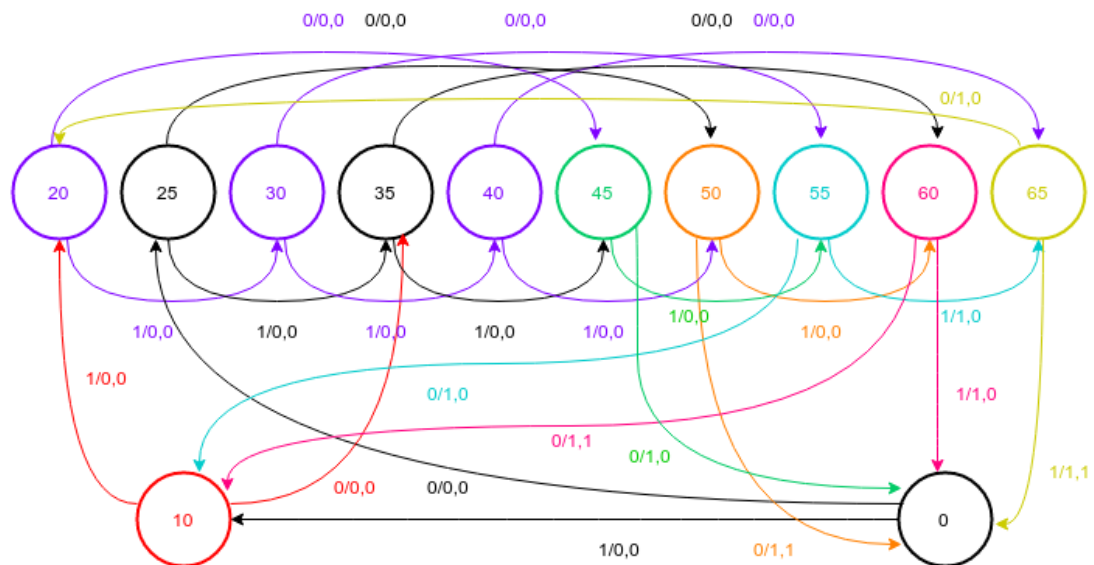a. State diagram:

The following state diagram was derived from the description:



State diagram for a vending machine finite state machine with outputs y0, y1

The states were verified by an executable Python script, `vending_machine_fsm.py` attached to the report in the `src` directory. The script is written in Python 2.7 syntax.

Usage:

Systems with a python2 compiler as default:

```
python vending_machine_fsm.py
```

Systems with a newer Python compiler:

```
python2.x vending_machine_fsm.py
```

The script generates the following outputs:

```
Switch = 0
A 0000 -> D 0010 (0, 0)
C 0011 -> H 0110 (0, 0)
B 0001 -> F 0101 (0, 0)
E 0100 -> J 1101 (0, 0)
D 0010 -> I 1100 (0, 0)
G 0111 -> L 1110 (0, 0)
F 0101 -> K 1111 (0, 0)
I 1100 -> A 0000 (1, 1)
H 0110 -> A 0000 (1, 0)
K 1111 -> B 0001 (1, 1)
J 1101 -> B 0001 (1, 0)
L 1110 -> C 0011 (1, 0)
```

```
Switch = 1
A 0000 -> B 0001 (0, 0)
C 0011 -> E 0100 (0, 0)
B 0001 -> C 0011 (0, 0)
E 0100 -> G 0111 (0, 0)
D 0010 -> F 0101 (0, 0)
G 0111 -> I 1100 (0, 0)
F 0101 -> H 0110 (0, 0)
I 1100 -> K 1111 (0, 0)
H 0110 -> J 1101 (0, 0)
K 1111 -> A 0000 (1, 0)
J 1101 -> L 1110 (0, 0)
L 1110 -> A 0000 (1, 1)
```

12 states with their corresponding code assignments

b. Functions:

The script was also used to determine the minterms for each of the Boolean functions for the 4 flip flops and 2 outputs:

```
Default don't cares: [8, 9, 11, 10, 24, 25, 27, 26]
J0 [2, 4, 5, 7, 22, 23]
J0_D [12, 13, 14, 15, 28, 29, 30, 31]
J1 [1, 2, 3, 18, 19]
J1_D [4, 5, 6, 7, 12, 13, 14, 15, 20, 21, 22, 23, 28, 29, 30, 31]
J2 [0, 5, 17, 20, 21, 28, 29]
J2_D [2, 3, 6, 7, 14, 15, 18, 19, 22, 23, 30, 31]
J3 [4, 14, 16, 18, 20, 22, 28]
J3_D [1, 3, 5, 7, 13, 15, 17, 19, 21, 23, 29, 31]
K0 [12, 13, 14, 15, 30, 31]
K0_D [0, 1, 2, 3, 4, 5, 6, 7, 16, 17, 18, 19, 20, 21, 22, 23]
K1 [6, 12, 13, 14, 15, 30, 31]
K1_D [0, 1, 2, 3, 16, 17, 18, 19]
K2 [2, 6, 15, 18, 19, 22, 23, 30, 31]
K2_D [0, 1, 4, 5, 12, 13, 16, 17, 20, 21, 28, 29]
K3 [3, 7, 19, 21, 23, 29, 31]
K3_D [0, 2, 4, 6, 12, 14, 16, 18, 20, 22, 28, 30]
z0 [6, 12, 13, 14, 15, 30, 31]
z1 [12, 15, 30]
```

Minterms for all the functions generated by simulating the state machine
(variables with '_D' represent don't cares)

The minterms were then used to reduce functions through use of Karnaugh maps:

| | $\bar{D}\bar{E}$ | $\bar{D}E$ | DE | $D\bar{E}$ |
|-------------------------|------------------|------------|------|------------|
| $\bar{A}\bar{B}\bar{C}$ | 0 | 0 | 0 | 1 |
| $\bar{A}\bar{B}C$ | 1 | 1 | 1 | 0 |
| $\bar{A}B\bar{C}$ | x | x | x | x |
| $\bar{A}BC$ | x | x | x | x |
| $A\bar{B}\bar{C}$ | 0 | 0 | 0 | 0 |
| $A\bar{B}C$ | 0 | 0 | 1 | 1 |
| $AB\bar{C}$ | x | x | x | x |
| ABC | x | x | x | x |

$$j0 = \bar{A}\bar{C}\bar{D} + \bar{A}CE + ACD + \bar{A}CDE$$

| | $\bar{D}\bar{E}$ | $\bar{D}E$ | DE | $D\bar{E}$ |
|-------------------------|------------------|------------|------|------------|
| $\bar{A}\bar{B}\bar{C}$ | x | x | x | x |
| $\bar{A}\bar{B}C$ | x | x | x | x |
| $\bar{A}B\bar{C}$ | 1 | 1 | 1 | 1 |
| $\bar{A}BC$ | x | x | x | x |
| $A\bar{B}\bar{C}$ | x | x | x | x |
| $A\bar{B}C$ | x | x | x | x |
| $AB\bar{C}$ | 0 | 0 | 1 | 1 |
| ABC | x | x | x | x |

$$k0 = \bar{A} + D$$

| | $\bar{D}\bar{E}$ | $\bar{D}E$ | $D\bar{E}$ | DE |
|-------------------------|------------------|------------|------------|------|
| $\bar{A}\bar{B}\bar{C}$ | 0 | 1 | 1 | 1 |
| $\bar{A}\bar{B}C$ | x | x | x | x |
| $\bar{A}B\bar{C}$ | x | x | x | x |
| $\bar{A}BC$ | x | x | x | x |
| $A\bar{B}\bar{C}$ | 0 | 0 | 1 | 1 |
| $A\bar{B}C$ | x | x | x | x |
| $AB\bar{C}$ | x | x | x | x |
| ABC | x | x | x | x |

$$j1 = \bar{A}E + D$$

| | $\bar{D}\bar{E}$ | $\bar{D}E$ | $D\bar{E}$ | DE |
|-------------------------|------------------|------------|------------|------|
| $\bar{A}\bar{B}\bar{C}$ | x | x | x | x |
| $\bar{A}\bar{B}C$ | 0 | 0 | 0 | 1 |
| $\bar{A}B\bar{C}$ | 1 | 1 | 1 | 1 |
| $\bar{A}BC$ | x | x | x | x |
| $A\bar{B}\bar{C}$ | x | x | x | x |
| $A\bar{B}C$ | 0 | 0 | 0 | 0 |
| $AB\bar{C}$ | 0 | 0 | 1 | 1 |
| ABC | x | x | x | x |

$$k1 = \bar{A}B + BD + \bar{A}D\bar{E}$$

| | $\bar{D}\bar{E}$ | $\bar{D}E$ | $D\bar{E}$ | DE |
|-------------------------|------------------|------------|------------|------|
| $\bar{A}\bar{B}\bar{C}$ | 1 | 0 | x | x |
| $\bar{A}\bar{B}C$ | 0 | 1 | x | x |
| $\bar{A}B\bar{C}$ | 0 | 0 | x | x |
| $\bar{A}BC$ | x | x | x | x |
| $A\bar{B}\bar{C}$ | 0 | 1 | x | x |
| $A\bar{B}C$ | 1 | 0 | x | x |
| $AB\bar{C}$ | 1 | 1 | x | x |
| ABC | x | x | x | x |

$$j2 = AE + AC + \bar{A}\bar{C}\bar{E} + \bar{B}CE$$

| | $\bar{D}\bar{E}$ | $\bar{D}E$ | $D\bar{E}$ | DE |
|-------------------------|------------------|------------|------------|------|
| $\bar{A}\bar{B}\bar{C}$ | x | x | 0 | 1 |
| $\bar{A}\bar{B}C$ | x | x | 0 | 1 |
| $\bar{A}B\bar{C}$ | x | x | 1 | 0 |
| $\bar{A}BC$ | x | x | x | x |
| $A\bar{B}\bar{C}$ | x | x | 1 | 1 |
| $A\bar{B}C$ | x | x | 1 | 1 |
| $AB\bar{C}$ | x | x | 1 | 1 |
| ABC | x | x | x | x |

$$k2 = A + \bar{B}\bar{E} + BE$$

| | $\bar{D}\bar{E}$ | $\bar{D}E$ | $D\bar{E}$ | DE |
|-------------------------|------------------|------------|------------|------|
| $\bar{A}\bar{B}\bar{C}$ | 0 | x | x | 0 |
| $\bar{A}\bar{B}C$ | 1 | x | x | 0 |
| $\bar{A}B\bar{C}$ | 0 | x | x | 1 |
| $\bar{A}BC$ | x | x | x | x |
| $A\bar{B}\bar{C}$ | 1 | x | x | 1 |
| $A\bar{B}C$ | 1 | x | x | 1 |
| $AB\bar{C}$ | 1 | x | x | 0 |
| ABC | x | x | x | x |

$$j3 = A\bar{B} + A\bar{D} + \bar{B}C\bar{D} + \bar{A}BD$$

| | $\bar{D}\bar{E}$ | $\bar{D}E$ | $D\bar{E}$ | DE |
|-------------------------|------------------|------------|------------|------|
| $\bar{A}\bar{B}\bar{C}$ | x | 0 | 1 | x |
| $\bar{A}\bar{B}C$ | x | 0 | 1 | x |
| $\bar{A}B\bar{C}$ | x | 0 | 0 | x |
| $\bar{A}BC$ | x | x | x | x |
| $A\bar{B}\bar{C}$ | x | 0 | 1 | x |
| $A\bar{B}C$ | x | 1 | 1 | x |
| $AB\bar{C}$ | x | 1 | 1 | x |
| ABC | x | x | x | x |

$$k3 = \bar{B}D + AC$$

| | $\overline{D.E}$ | $\overline{D.E}$ | $D.E$ | $D.E$ |
|--------------------|------------------|------------------|-------|-------|
| $\overline{A.B.C}$ | 0 | 0 | 0 | 0 |
| $\overline{A.B.C}$ | 0 | 0 | 0 | 1 |
| $\overline{A.B.C}$ | 1 | 1 | 1 | 1 |
| $\overline{A.B.C}$ | x | x | x | x |
| <hr/> | | | | |
| $A.B.C$ | 0 | 0 | 0 | 0 |
| $A.B.C$ | 0 | 0 | 0 | 0 |
| $A.B.C$ | 0 | 0 | 1 | 1 |
| $A.B.C$ | x | x | x | x |


$$y_0 = \overline{A}B + BD + \overline{A}\overline{C}D\overline{E}$$

| | $\overline{D.E}$ | $\overline{D.E}$ | $D.E$ | $D.E$ |
|--------------------|------------------|------------------|-------|-------|
| $\overline{A.B.C}$ | 0 | 0 | 0 | 0 |
| $\overline{A.B.C}$ | 0 | 0 | 0 | 0 |
| $\overline{A.B.C}$ | 1 | 0 | 1 | 0 |
| $\overline{A.B.C}$ | x | x | x | x |
| <hr/> | | | | |
| $A.B.C$ | 0 | 0 | 0 | 0 |
| $A.B.C$ | 0 | 0 | 0 | 0 |
| $A.B.C$ | 0 | 0 | 0 | 1 |
| $A.B.C$ | x | x | x | x |

$$y_1 = \overline{A}B\overline{D}\overline{E} + \overline{A}BDE + \overline{A}BD\overline{E}$$

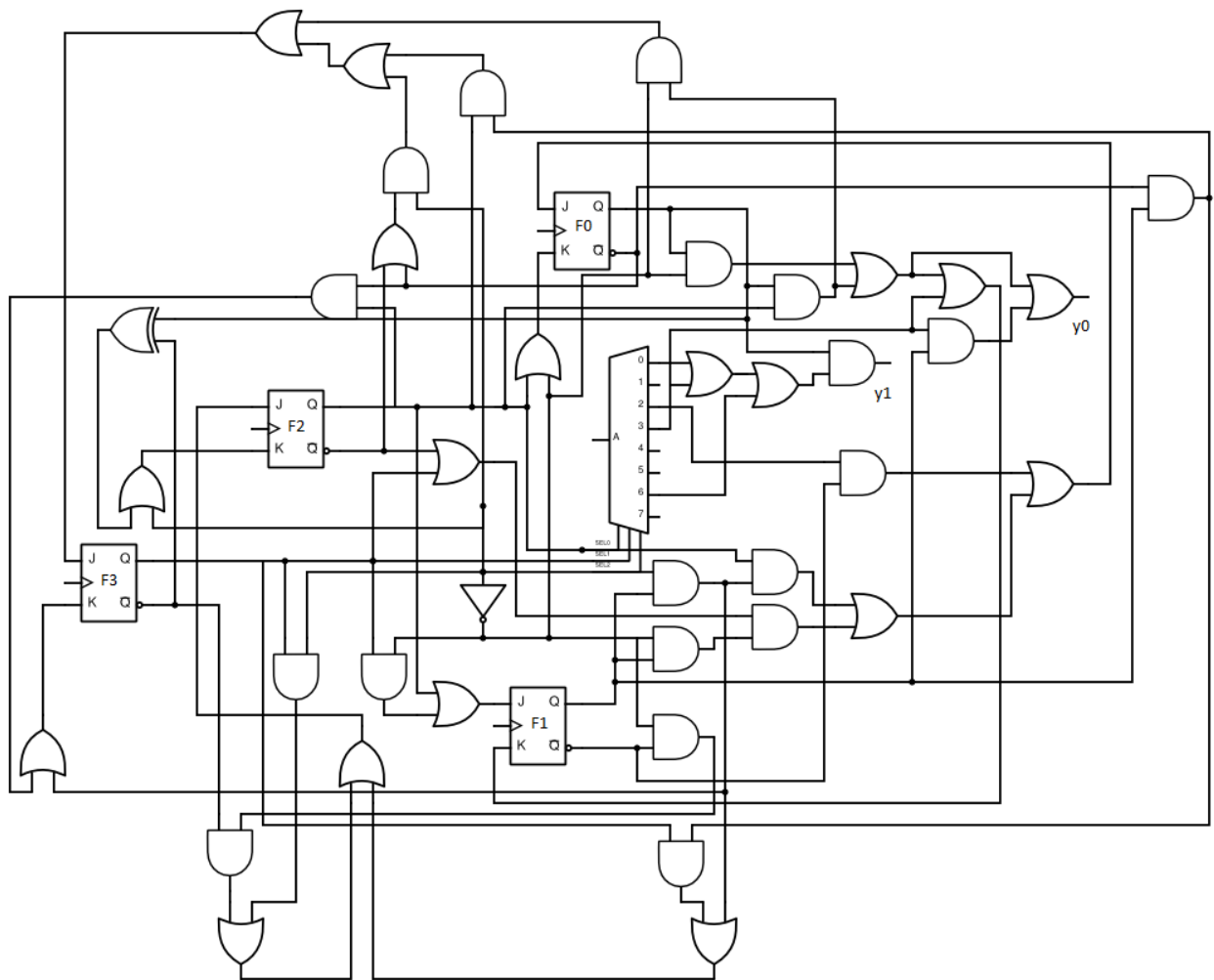c. Design:

After several Boolean function manipulation, a design for the circuit was realized. Since the number of flip flops can be found by computing $\lceil \log_2(states) \rceil$, 4 JK flip flops were used. A decoder was used as well to generate 4 3-bit minterms that were used multiple times. The following schematic was designed and used as the working blueprint during the implementation:



Circuit design of the vending machine finite state machine

d. Verification:

The logic of the entire circuit was verified using Verilog. Several testbenches have been included along with a makefile for convenience. The scripts were compiled using Icarus Verilog (iverilog) successfully, and ncverilog on GL, where it showed occasional runtime errors.

Usage:

Testbench for JK flip flop module:

make jk

Testbench for the machine with inputs of only 0:

make quarters

Testbench for the machine with inputs of only 1:

make dimes

Testbench for the machine with inputs of both 0 and 1:

make

3. Conclusion:

After the designing processes were completed, the circuit was constructed on a breadboard, and the logic above was verified again. Due to possible pin mapping errors and/or flawed logic, the state machine was not able to be implemented correctly and debugging the entire machine was not possible.