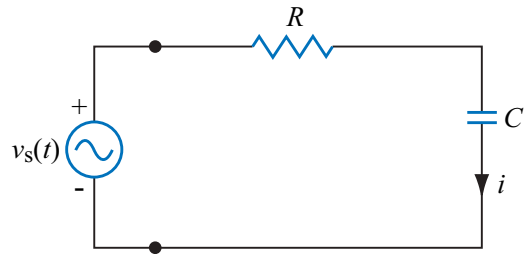



(Each problem is worth 10 points)

1. A wave in a lossy transmission line has a frequency of $f = 5$ GHz and $\epsilon_r = 2.25$.
 - a. What are ω , λ , β , and u_p ?
 - b. The wave has an initial amplitude of 125 V. After propagating 300 m, its amplitude is 1 V. What is its amplitude at 100 m and 200 m?

2. For a simple RC circuit like the one shown on the right [Ulaby et al., Fig. 1-20], operating at a frequency f with a source voltage whose phasor is expressed \tilde{V}_s , give expressions for the phasors of the voltage and the current across the resistor and the capacitor as a function of \tilde{V}_s , R , C , and f . What fraction of the power is dissipated in the resistor and what fraction is dissipated in the capacitor?



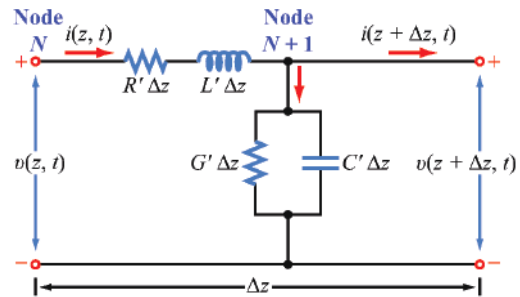3. Show how to obtain the telegrapher's equations for a transmission line using the equivalent circuit shown to the right [Ulaby et al., Fig. 2-8] in the limit where Δz becomes small. Write the corresponding phasor domain equations.



4. In a parallel plate transmission line, we have $Z_0 = 100 \Omega$ and $u_p = 2 \times 10^8$ m/s. What are L' and C' ? Recall that in a parallel plate transmission line, we have $L' = \mu h/w$ and $C' = \epsilon w/h$, where w is the width of the plates and h is the separation between the plates. Estimate w/h to two significant figures.
5. Consider a $50\text{-}\Omega$ transmission line with a load impedance of 100Ω and a generator impedance of 50Ω . At $t = 0$, we turn on a generator voltage of 100 V, and at $t = 1$ ns, the transient voltage reaches the load. Give the voltage and current as a function of time at both the generator and the load.