

Problem Set #3 Solutions

1. We first note from Ulaby et al.'s equation (2.29),

$$Z_0 = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}} = \sqrt{\frac{L'}{C'}} \sqrt{\frac{R'/L' + j\omega}{G'/C' + j\omega}} = \sqrt{L'/C'},$$

where we note that for a distortionless line, we have $R'/L' = G'/C'$. We also have the general expression for γ ,

$$\gamma = [(R' + j\omega L')(G' + j\omega C')]^{1/2} = [R'G' + j\omega(L'G' + R'C') - \omega^2 L'C']^{1/2}.$$

For a distortionless line, we have $L'G' + R'C' = 2R'C' = 2L'G' = 2\sqrt{L'G'}\sqrt{R'C'}$. Substituting this last relation into the expression for γ , we have

$$\alpha + j\beta = \gamma = [R'G' + 2j\omega\sqrt{R'G'}\sqrt{L'C'} + L'C']^{1/2} = \sqrt{R'G'} + j\omega\sqrt{L'C'}.$$

We now conclude $\alpha = \sqrt{R'G'} = R'\sqrt{C'/L'}$ and $\beta = \omega\sqrt{L'C'}$.

2. According to Ulaby et al.'s Eq. 2.73, we have

$$S = \frac{1 + |\Gamma|}{1 - |\Gamma|}, \quad \text{which implies} \quad |\Gamma| = \frac{S - 1}{S + 1}.$$

In our case, $S = 1.5/0.8 = 1.875$, so that $|\Gamma| = 0.7/2.3 = 0.304$.

3. All the answers, with the exception of part (e) can be found in Ulaby's module 2.1B – 2.4B in the 2001–2007 editions. They can also be obtained using module 2.4 in the 2010 edition.

- a. We have $\omega = 2\pi f = 3\pi \times 10^9 \text{ s}^{-1} = 9.42 \times 10^9 \text{ s}^{-1}$. Since we are assuming $\mu = \mu_0$, we have $\epsilon_r = c^2/v_p^2 = (3 \times 10^8/1.5 \times 10^8)^2 = 4$. We have $z_L = Z_L/Z_0 = (25 - 25j)/50 = 0.5 - 0.5j$.
- b. We have $\Gamma = (Z_L - Z_0)/(Z_L + Z_0) = -0.2 - 0.4j = 0.447 \exp(-j2.034)$. Hence, we have $|\Gamma| = 0.447$ and $\theta_r = -2.034 \text{ rads} = -117^\circ$. We also have $S = (1 + |\Gamma|)/(1 - |\Gamma|) = 2.62$.

To calculate l_{\max} and l_{\min} , we first note that $\lambda = v_p/f = 1.5 \times 10^8/1.5 \times 10^9 = 0.1 \text{ m} = 10 \text{ cm}$. We also note, for future reference that $\beta = 2\pi/\lambda = 20\pi \text{ m}^{-1}$. Maxima occur when $-z = (\theta_r\lambda/4\pi) + (n\lambda/2) > 0$, or when $(-0.162 + 0.5n)\lambda > 0$. The first maximum occurs when $n = 1$, at which point $l_{\max} = 3.38 \text{ cm}$. Since $l_{\max} > 0.25\lambda = 2.50 \text{ cm}$, we have $l_{\min} = l_{\max} - \lambda/4 = 0.88 \text{ cm}$.

- c. To determine V_{\max} and V_{\min} , we first find $\beta l = 2\pi/\lambda = 2\pi \times 24/10 = 15.1$. We must calculate Z_{in} using Ulaby's Eq. (2.61),

$$Z_{\text{in}} = Z_0 \frac{\exp(j\beta l) + \Gamma \exp(-j\beta l)}{\exp(j\beta l) - \Gamma \exp(-j\beta l)}.$$

We find $Z_{\text{in}} = 71.1 - j55.8$. We then calculate V_0^+ using Ulaby's Eq. (2.66)

$$V_0^+ = \left(\frac{\tilde{V}_g Z_{\text{in}}}{Z_g + Z_{\text{in}}} \right) \left(\frac{1}{\exp(j\beta l) + \Gamma \exp(-j\beta l)} \right) = -4.05 - j2.94 \text{ V}.$$

We then find that $|V_0^+| = 5.00$ and that $\theta_r = -144^\circ$. From here, we find $V_{\max} = |V_0^+|(1 + |\Gamma|) = 7.24 \text{ V}$ and $V_{\min} = |V_0^+|(1 - |\Gamma|) = 2.74 \text{ V}$.


- d. The general expression for $v(z, t)$ has the form

$$v(z, t) = A \cos(\omega t - \beta z + \pi_1) + B \cos(\omega t + \beta z + \phi_2),$$

and we already showed that $\omega = 3\pi \times 10^9 \text{ s}^{-1}$ and that $\beta = 20\pi \text{ m}^{-1}$. Since we must have $A = |V_0^+|$ and $\phi_1 = \theta_r$, we have $A = 5 \text{ V}$ and $\phi_1 = -144^\circ$. We have $V_0^- = \Gamma V_0^+ = -0.367 + j2.21 = 2.24 \exp(j1.74) = 2.24 \angle 99.4^\circ$, from which we conclude that $B = 2.24$ and $\phi_2 = 99.4^\circ$.

- e. The output from Ulaby et al.'s module 2.4 follows:

ULABY CD MODULE OUTPUT:

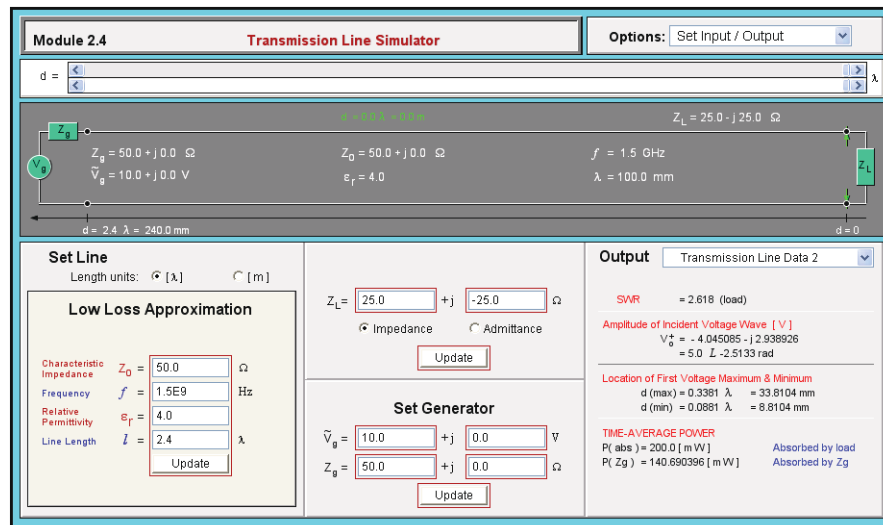

- f. Writing $V_0^+ = |V_0^+| \exp(j\phi^+)$, we find

$$\tilde{V}(z) = |V_0^+| [\exp(-j\beta z + \phi^+) + |\Gamma| \exp(j\beta z + \theta_r + \phi^+)].$$

Writing $\tilde{V}(z) = |\tilde{V}(z)| \exp[j\phi(z)]$, we find first

$$\begin{aligned} |V(z)| &= \left\{ \left[\exp(-j\beta z + \phi^+) + |\Gamma| \exp(j\beta z + \theta_r + \phi^+) \right] \right. \\ &\quad \left. \times \left[\exp(+j\beta z - \phi^+) + |\Gamma| \exp(-j\beta z - \theta_r - \phi^+) \right] \right\}^{1/2} \\ &= \left[1 + |\Gamma|^2 + \exp(2j\beta z + \theta_r) + \exp(-2j\beta z - \theta_r) \right]^{1/2} \\ &= \left[1 + |\Gamma|^2 + 2|\Gamma| \cos(2\beta z + \theta_r) \right]^{1/2} \end{aligned}$$

We also have

$$\phi(z) = \tan^{-1} \left\{ \frac{\text{Im}[\tilde{V}(z)]}{\text{Re}[\tilde{V}(z)]} \right\} = \tan^{-1} \left\{ -\frac{\sin(\beta z - \phi^+) - |\Gamma| \sin(\beta z + \theta_r + \phi^+)}{\cos(\beta z - \phi^+) + |\Gamma| \cos(\beta z + \theta_r + \phi^+)} \right\}.$$


We finally have

$$v(z, t) = \text{Re} \left\{ |\tilde{V}(z)| \exp[j\phi(z)] \exp(j\omega t) \right\} = |\tilde{V}(z)| \cos[j\omega t + \phi(z)],$$

which is the result on slide 4.14.


4. The load impedance is given by $Z_L = R + j\omega L = 600 + j6.28 \times (5.00 \times 10^6) \times (2.00 \times 10^{-5}) = 600 + j628 \Omega$. We also have $\lambda = c/f = (3.00 \times 10^8)/(5.00 \times 10^6) = 60.0 \text{ m}$. We now find (a) $\Gamma = (Z_L - Z_0)/(Z_L + Z_0) = 0.55 + j0.31 = 0.63 \exp(j0.52)$ and (b) $S = (1 + |\Gamma|)/(1 - |\Gamma|) = 4.5$. (c) Since $\theta_r > 0$, the first voltage maximum is given by $d_{\max} = \theta_r \lambda / 4\pi = (0.516 \times 60.0)/12.6 = 2.5 \text{ m}$. (d) The first current maximum is given by the first voltage minimum, which is given by $d_{\min} = d_{\max} + \lambda/4 = 17 \text{ m}$. The output from Ulaby et al.'s module 2.5 follows:

ULABY CD MODULE OUTPUT:

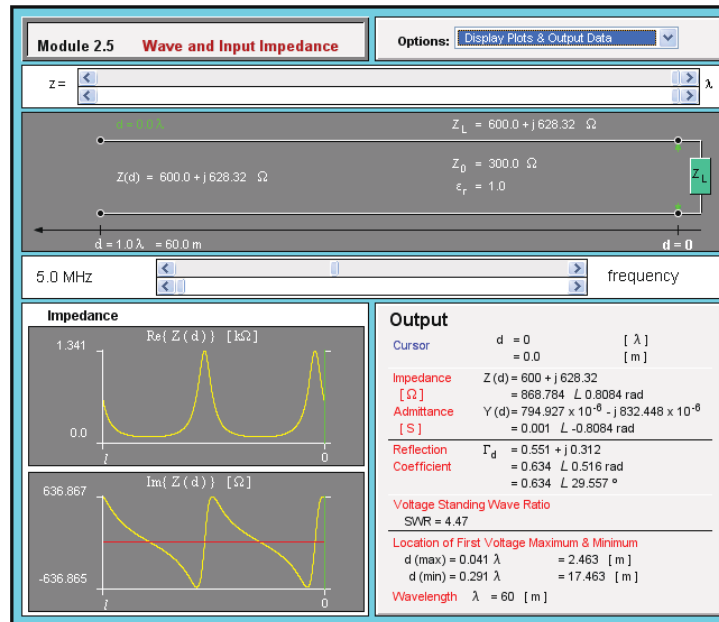

5. For a short-circuited line, we have $Z_{\text{in}}^{\text{sc}} = jZ_0 \tan \beta l$. (See Ulaby et al., Eq. 2.84.) Since $Z_0 = 50 \, \Omega$, to obtain a reactance of $40 \, \Omega$, we must have $\tan \beta l = 0.800$, which implies that $\beta l = 0.675$. With 300 MHz and a velocity of $2.25 \times 10^8 \text{ m/s}$, we find $\beta = 2\pi f/u_p = 6.28 \times (3.00 \times 10^8)/(2.25 \times 10^8) = 8.38 \text{ m}^{-1}$. It follows that $l = 0.675/8.38 = 0.080 \text{ m}$ or 8.0 cm . The output from Ulaby's module 2.5 follows:

ULABY CD MODULE OUTPUT:

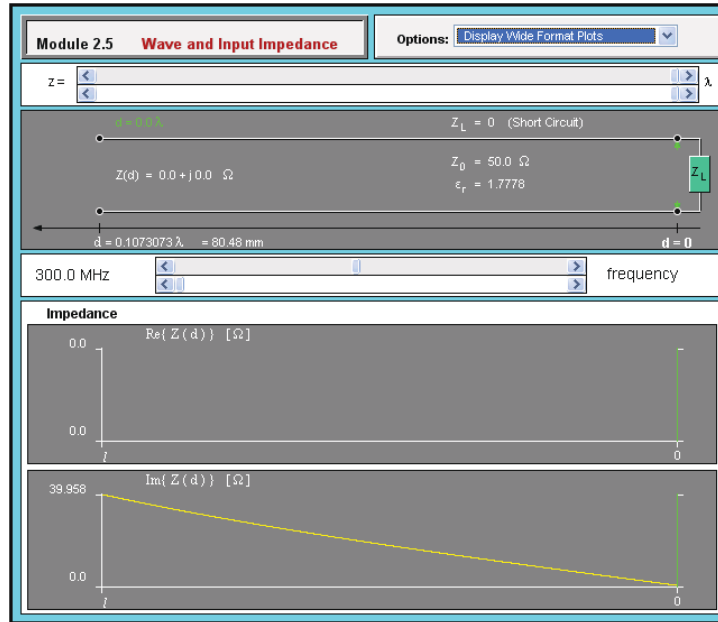

6. We begin by recalling that

$$V_i(t) = \text{Re}[\tilde{V}_i \exp(j\omega t)] = \frac{1}{2} [\tilde{V}_i \exp(j\omega t) + \tilde{V}_i^* \exp(-j\omega t)]$$

and

$$I_i(t) = \text{Re}[\tilde{I}_i \exp(j\omega t)] = \frac{1}{2} [\tilde{I}_i \exp(j\omega t) + \tilde{I}_i^* \exp(-j\omega t)]$$

It follows that

$$V_i(t)I_i(t) = \frac{1}{4} [\tilde{V}_i \tilde{I}_i \exp(2j\omega t) + \tilde{V}_i \tilde{I}_i^* + \tilde{V}_i^* \tilde{I}_i + \tilde{V}_i^* \tilde{I}_i^* \exp(-2j\omega t)].$$

We now calculate

$$\begin{aligned} P_{\text{av}}^i &= \frac{\omega}{2\pi} \int_0^{2\pi/\omega} V_i(t)I_i(t) dt \\ &= \frac{\omega}{2\pi} \int_0^{2\pi/\omega} \frac{1}{4} [\tilde{V}_i \tilde{I}_i \exp(2j\omega t) + \tilde{V}_i \tilde{I}_i^* + \tilde{V}_i^* \tilde{I}_i + \tilde{V}_i^* \tilde{I}_i^* \exp(-2j\omega t)] dt \\ &= \frac{1}{4} [\tilde{V}_i \tilde{I}_i^* + \tilde{V}_i^* \tilde{I}_i] = \frac{1}{2} \text{Re}(\tilde{V}_i \tilde{I}_i^*). \end{aligned}$$

The proof for the reflected power is identical.

7. We begin by calculating the voltage reflection coefficient, $\Gamma = (Z_L - Z_0)/(Z_L + Z_0) = 25/125 = 0.200$. We also have $\exp(j\beta l) = \exp(j2\pi \times 0.15) = 0.588 + j0.809$.

a. We now find

$$Z_{\text{in}} = Z_0 \frac{\exp(j\beta l) + \Gamma \exp(-j\beta l)}{\exp(j\beta l) - \Gamma \exp(-j\beta l)} = 41.3 - j16.3 = 44.4\angle -21.2^\circ$$

b. We have

$$\tilde{V}_i = \left(\frac{\tilde{V}_g Z_{\text{in}}}{Z_g + Z_{\text{in}}} \right) = 46.9 - j9.51 = 47.8 \exp(-j0.200) = 47.8\angle -11.5^\circ \text{ V},$$

$$\text{and } \tilde{I}_i = \tilde{V}_i / Z_{\text{in}} = 1.06 + j0.190 = 1.08 \exp(j0.177) = 1.08\angle 10.2^\circ \text{ A}.$$

c. We have $P_{\text{in}} = 0.5 \operatorname{Re}(\tilde{V}_i \tilde{I}_i^*) = 24.0 \text{ W}$.

d. We have

$$\begin{aligned} V_0^+ &= V_i \left(\frac{1}{\exp(j\beta l) + \Gamma \exp(-j\beta l)} \right) \\ &= 29.4 - j40.5 = 50.0 \exp(-j0.942) = 50.0\angle -54.0^\circ \end{aligned}$$

and $V_0^- = \Gamma V_0^+ = 0.200 V_0^+ = 10.0 \exp(-j0.942)$, so that $\tilde{V}_L = 60.0 \exp(-j0.942)$. We have $\tilde{I}_L = \tilde{V}_L / Z_L = 0.800 \exp(-j0.942)$. It follows that $P_L = 0.5 \operatorname{Re}(\tilde{V}_L \tilde{I}_L^*) = 24.0 \text{ W}$. This value is the same as P_{in} and indicates that all the incoming power is dissipated in the load.

e. The power delivered by the generator is $P_g = 0.5 \operatorname{Re}(\tilde{V}_g \tilde{I}_i^*) = 53.1 \text{ W}$. The power that is dissipated in Z_g equals $0.5 \operatorname{Re}(Z_g \tilde{I}_i \tilde{I}_i^*) = 29.1 \text{ W}$. The power that is dissipated in Z_g and the power that is dissipated in the load equals the power that is supplied by the generator.