

# UMBC

AN HONORS UNIVERSITY IN MARYLAND

Department of Computer Science and Electrical Engineering

## CMPE 415

# Synthesis of Loops

Prof. Ryan  
Robucci

# Single Assignment Code

---

- Consider the following code:

```
a=b+1;  
a=a*3;
```

- This is the same as

```
a = (b+1)*3;
```

- This only assigning a, and there is a single assignment to it.
- It can be implemented in hardware with

[register b] → (+1) → (x3) → [register a]

# Conversion to Single Assignment

---

- A technique uses variable creation and renaming to create single assignments in section of code:

```
a1=b+1;  
a2=a1*a3;
```

# MERGE

---

We'll first motivate with another example:

```
a=b;
for(i=1;i<6;i++){
    a=a+i
}
```

Attempt:

```
a1=b;
for(i=1;i<6;i++){
    a2= a? + i; //what to use?
                //for first iteration need a1, thereafter need a2
}
```

**Solution is to use introduce the concept of a MERGE.  
A MERGE maps to a mux in HW, typically creating a loop or feedback.**

**Still must ensure that no combinatorial loops are formed, adding registers and multiple clock cycles as needed (below a2 may be implemented a register to ensure this).**

```
a1=b;  
for(i=1;i<6;i++){  
    a3=MERGE(if i==1 use a1; else if i>1 use a2);  
                                     //now a1 and a2 will be registers  
    a2=a3+1;  
}
```

# Unrolling and Simplification

- Unrolling can be used to create single assignment code

```
a1=b;  
a2=a1+1;  
a3=a3+2;  
a4=a4+3;  
a5=a5+4;  
a6=a6+5;
```

This can be implemented in one clock cycle with HW and 5 adders.

- Simplification can trim unnecessary complexity from run time

```
a = b+15;
```

a single adder in one clock cycle

# Example


## Original Code

```
int gcd(int a , int b) {  
    while (a!= b) {  
        if (a> b)  
            a = a-b;  
        else  
            b=b-a;  
        }  
    return a;  
}
```

## Single Assignment

```
int gcd(int a1 , int b1) {  
    while (MERGE(a1,a2)!=MERGE(b1,b2)){  
        a3 = MERGE(a1,a2);  
        b3 = MERGE(b1,b2);  
        if (a3> b3)  
            a2 = a3-b3;  
        else  
            B2 = b3-a3;  
        }  
    return a2;  
}
```
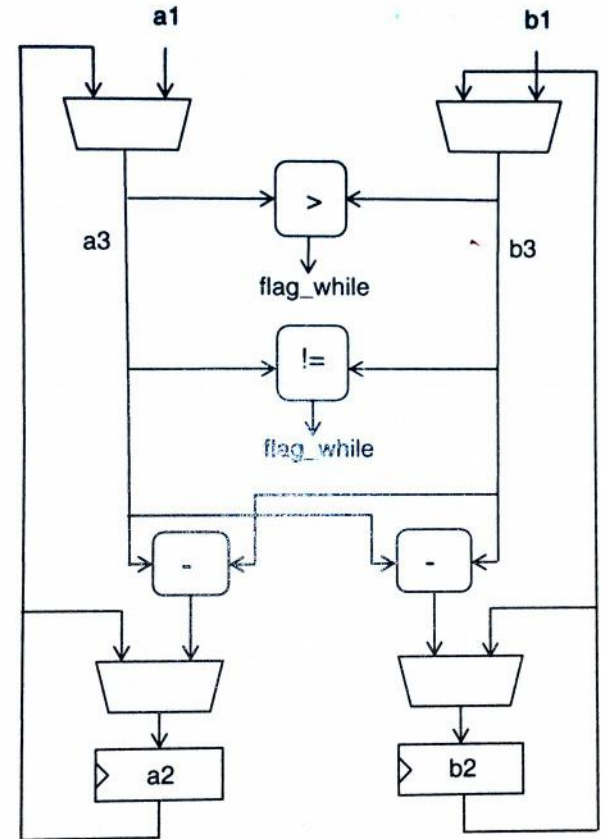
## Single Assignment Code Hardware Implementation



**Single Assignment Code** allows examination of data dependencies and hardware resources such as what can be done in a single clock cycle (combinatorial) and where a register is required. These concepts are also important when writing behavioral HDL code in Verilog or VHDL.



# Synthesizeable Combinatorial Code with attention to Loops


---

- Today we'll discuss a few constructs which involve a concern of **Control** Loops and **Data** (dependency) Loops in procedural HDL
- We'll first concern ourselves with combinatorial behavior and then allow additional flexibility with sequential
- Should not attempt to synthesize any code that implements unresolvable dependency loops as combinatorial HW (executes in one clock cycle)
 
# Single Assignment Code (1)

- Think of each statement as a node on a graph with the edges denoting dependencies. Nodes can be producers and consumers of values. A graph with loops cannot be directly resolved as a combinatorial circuit. The inputs not generated from within the code are also nodes – they represent an assignment elsewhere.

```
y1 = a+b;  
y2 = y1+c;  
y3 = y1+y2*y2;
```




# Single Assignment Code (2)

- Branches can be thought of as multiplexors that depend on the evaluation of conditional expression.

A new flag variable based on the condition evaluation may be introduced to make this clear.


```
y1 = a+b;  
if (y1 < 0)  
    y2 = 0;  
else  
    y2 = y1;
```
 
```
y1 = a+b;  
flag = (y1 < 0);  
y2 = flag?0:y1;
```


 
# Single Assignment Code (3)

- To achieve the status of single assignment code, every variable may only be assigned once.
- We may need to convert code to an equivalent single-assignment code to understand its underlying structure. To do this introduce additional variables when variables are assignment more than once.



# Verilog Synthesis: Feedback (data dependency loops)

```
always @ (a,b) begin
```

```
  y = 0;
```

```
  y = y&a;
```

```
  y = y&b;
```

```
end
```

No feedback after substitutions

```
always @ (a,y) begin
```

```
  y = ~(y&a);
```

```
end
```

Feedback


```
always @ (a,b,yA,yB)  
begin
```

```
  yA = ~(yB&a);
```

```
  yB = ~(yA&b);
```

```
end
```

Feedback

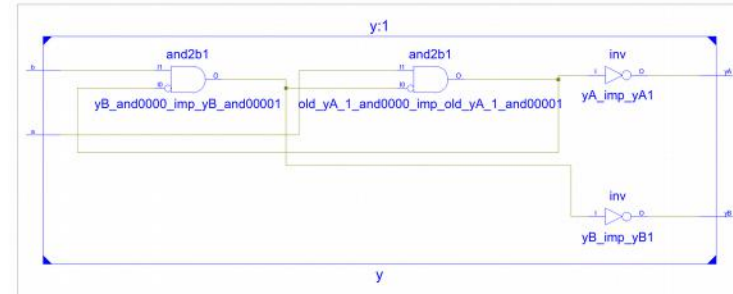

```
always @ (posedge clk)  
begin  
  y = ~(y&a);  
end
```

This clearly does not attempt to describe combinatorial hardware it is edge-triggered describing sequential hardware. A register y is inserted.

# Combinatorial Synthesis: Loops

- Static Loops: Number of iterations defined at compile time. Can directly perform finite unrolling  
Often synthesizers cannot convert non-static loops to combinatorial circuit.
- In the example below, the condition that is checked before every iteration is dependent on assignments within the body of the loop.
- Furthermore, the multiple data movements are problematic

```
// "while loop"
temp = data_in;
count = 0;
for (index = 0; | temp; index = index + 1)
begin
    if temp[0] == 1 (count = count + 1)
        temp >> 1;
end
```

# Combinatorial Synthesis: Loops

---

- Should rewrite to have static loop count and no implied data movement:

```
// "while loop"  
count = 0;  
for(index=0; index<8; index=index+1) begin  
    if temp[index]==1 (count=count +1);  
end
```

# Synthesis: Feedback (data dependency loops)

Registered logic (mix comb and seq.) should be separated to understand the dependencies. New variables may be introduced to denote the difference in signals before and after a register.

```
always @ (posedge clk) begin  
  if (counter == CNT_MAX)  
    counter <= 0;  
  else  
    counter <= counter +1;  
end
```

Feedback is perhaps unclear here. See rewrite below.

```
always @ (posedge clk) begin  
  counter <= counter_comb;  
end
```

Feedback across clock cycles is OK.

```
always @ * begin  
  flag = counter == CNT_MAX;  
  counter_comb = flag?0:counter+1;  
end
```

No feedback in comb. part.



# Synthesis: keyword **disable**

---

- The keyword **disable** may be used to implement a “break” from a loop. Consider this not yet covered and avoid for now.

# Sequential Synthesis: Loops

- Note you may be able describe a **sequential** circuit with non-static loops, but this is commonly NOT SUPPORTED by synthesizers.


```
// "while loop" with iterations sync. to clock  
count = 0;  
for(index=0; !temp; index=index+1) begin  
    @(posedge clk);  
    if temp[0]==1 (count=count +1)  
        temp>>1;  
end
```

# Synthesis: Multicycle Operation

Typical to employ multi-cycle operations to reduce hardware through resource sharing (reuse of hardware in difference clock cycles) and reduce the critical path lengths.

```
always @ (posedge clk)
begin
    temp=a*b;
    @(posege clk)
    y=temp*c;
end
```

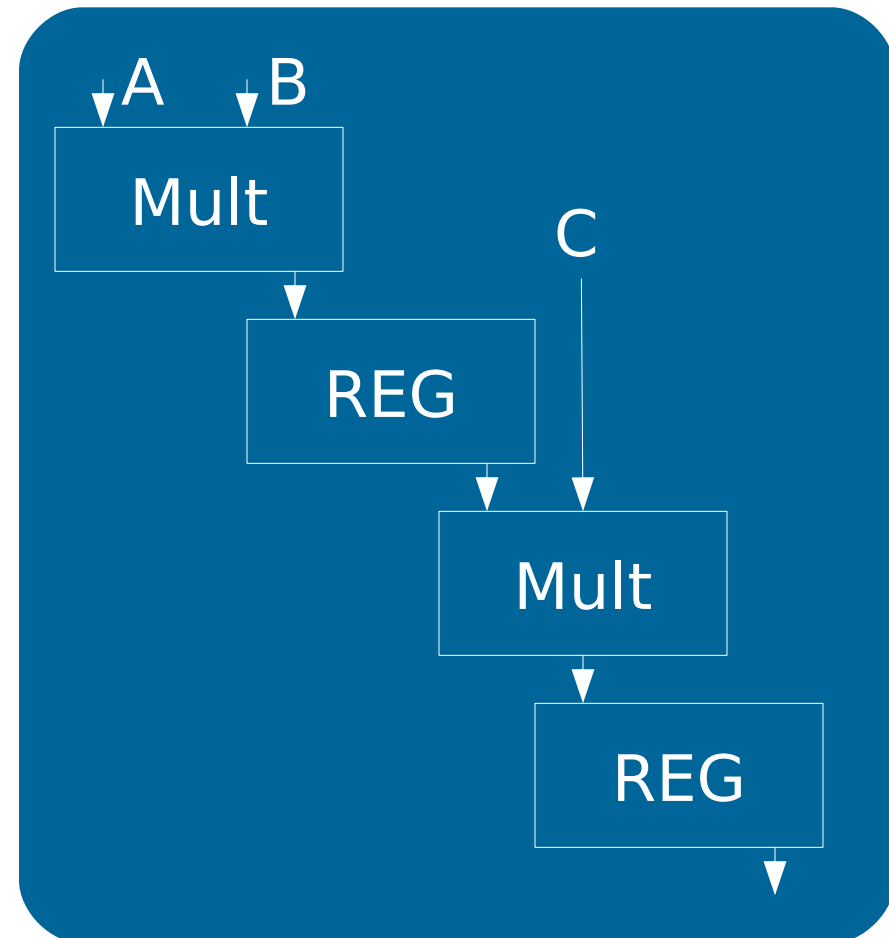- We'll want to understand how to implement multi-cycle operations using state machines



# Key Points

---

- Combinatorial data dependency loops cannot be synthesized
- Static for loops can be synthesized by being unrolled
- Dynamic for Loops may not be understood by the synthesizer
- Dynamic for Loops with timing control may be synthesized as a “multicycle operation” or a state machine.
- We'll want to formalize multi-cycle operations as state machines.

# A structural “for loop”: For Generate

- Uses a special indexing variable. Use for repetitive structural instantiations

```
genvar index;
generate
for (index=0; index < 8; index=index+1)
begin: gen_code_label
    BUFR BUFR_inst (
        .O(clk_o(index)), // Clock buffer output
        .CE(ce), // Clock enable input
        .CLR(clear), // Clock buffer reset input
        .I(clk_i(index)) // Clock buffer input
    );
end
endgenerate
```

- In class example adder

# For Generate

- Uses a special indexing variable. Use for repetitive instantiations

```
genvar index;
generate
for (index=0; index < 8; index=index+1)
begin: gen_code_label
    adder adder_inst (
        .cin(c[index]),
        .a(a[index]),
        .b(b[index]),
        .cout(c[index+1]),
        .y(u[index])
    );
end
endgenerate
```

# Concluding Points

---

- Combinatorial dependency loops cannot be synthesized
- Static for loops can be synthesized by being unrolled
- Dynamic for Loops may not be synthesizable
- Dynamic for Loops with timing control may be synthesized as a “multicycle operation” or a state machine.
- Repetative/Patterned Structural Instantiations may be done with for...generate loops
- We'll want to formalize multi-cycle operations as state machines.